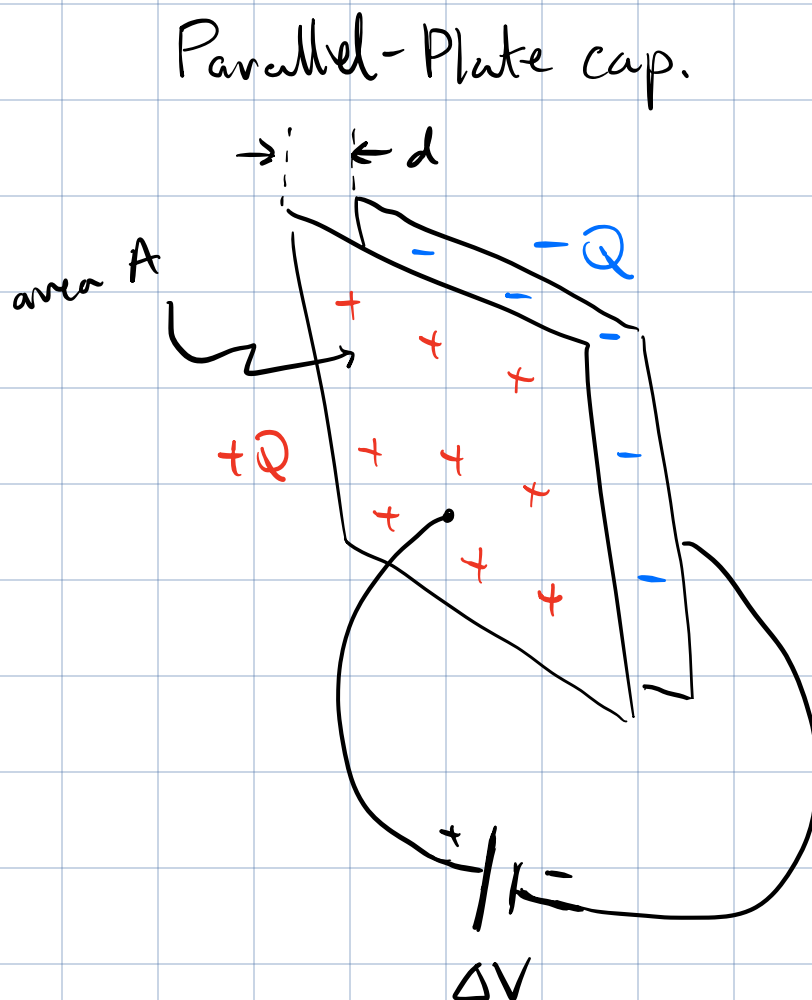


- To do:
- ✓ Complete HW 7 by 23:59 on Friday
 - ✓ Complete Pre-Lab # 4 before Lab # 4
 - ✓ Midterm Wed. Feb. 28 (in person ^{EME} 0050)
 - ✓ No tutorials this week

Before the break:



$$C = \epsilon_0 \frac{A}{d}$$


$$C = \frac{Q}{\Delta V}$$

Energy stored by a charged capacitor

$$U = \frac{Q^2}{2C} = \frac{1}{2} Q |\Delta V| = \frac{1}{2} C |\Delta V|^2$$

Lab #4

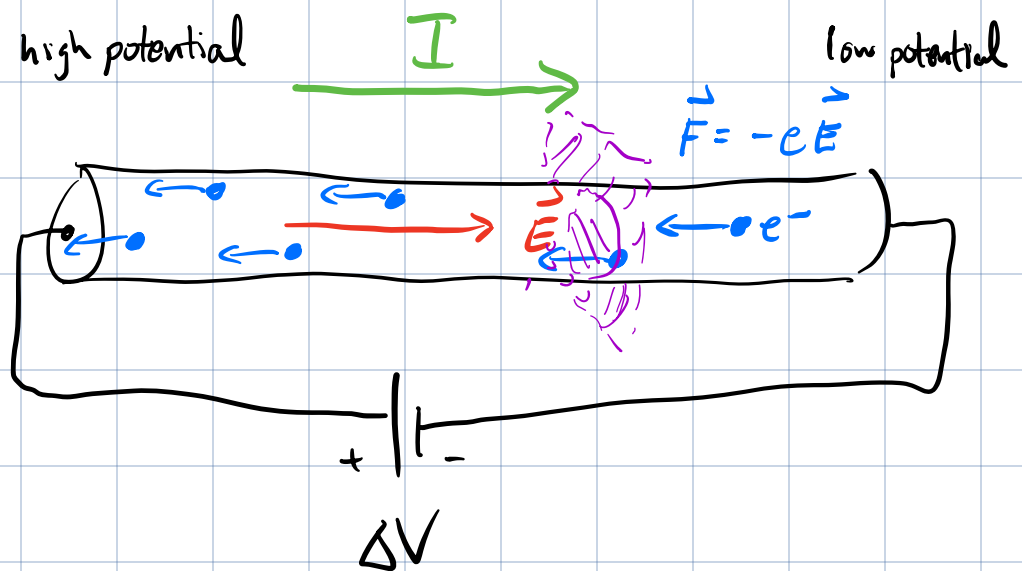Imagine connecting a battery across a cylindrical conductor or wire.



Recall that \vec{E} -fields point from high-to-low potential. Since $\vec{E} \neq 0$ in conductor, this is a non-equil. situation. \rightarrow Can have a net flow of charge.

\vec{E} -field in conductor exerts forces on mobile e^- causing a flow of charge or a current.

Imagine keeping track of amount of charge Δq that crosses a surface intersecting the wire during time interval Δt .

Define average current as

$$\text{current} \rightarrow I_{\text{avg}} = \frac{\Delta q}{\Delta t} \quad [I] = \frac{[\Delta q]}{[\Delta t]} = \frac{C}{S}$$

$$[I] = \frac{C}{S} \equiv A$$

$$1 \text{ amp} = \frac{1 \text{ Coulomb}}{1 \text{ sec.}}$$

If we shrink $\Delta t \rightarrow 0$, get the instantaneous current I :

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

In circuits, current is the dir'n of pos. charge flow. For a conductor it is electrons (neg) that flow. \therefore the current is in the opp. dir'n of the electron flow.

Suppose we connect the same battery to different wires (diff. types of material, or diff. length, diff. diameters ...)

Will find that for the same voltage, get a different current.

The resistance R of a wire is defined as

$$R = \frac{\Delta V}{I} \quad [R] = \frac{V}{A} = \Omega$$


↑
"ohm"

$$1\Omega = \frac{1V}{1A}$$

Circuit symbol for a resistor is :



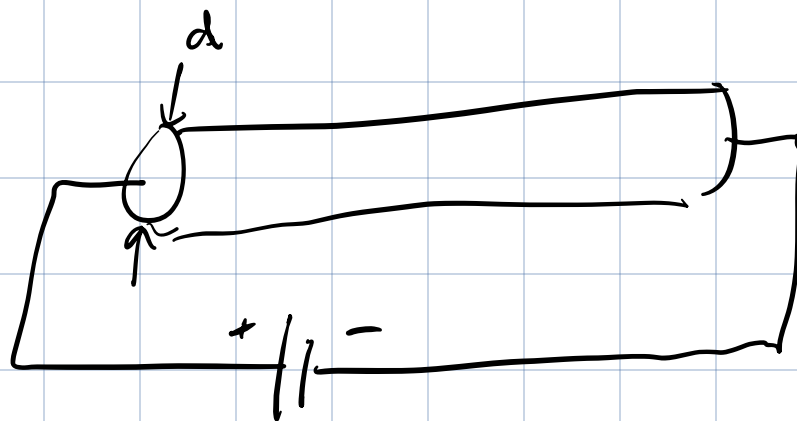
Circuit diagram for our wire connected to a battery is :



ΔV

R

$$R = \frac{\Delta V}{I}$$

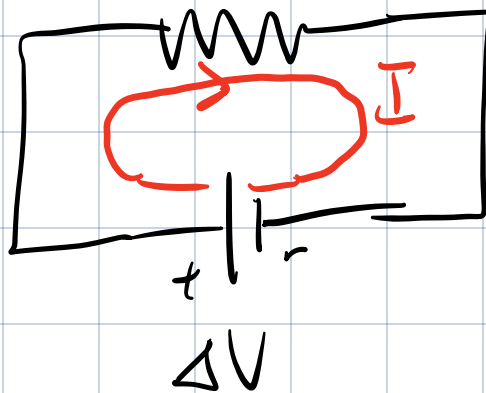


In Lab #4, you will investigate how the resistance of a wire depends on its diameter d .


Back to capacitors.

Combinations of Capacitors.

Parallel Combinations

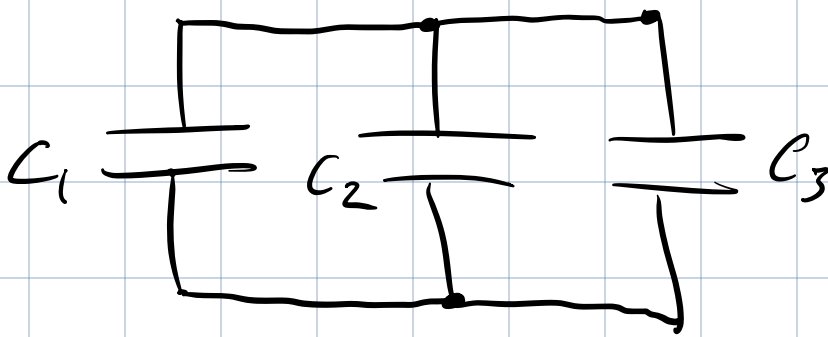

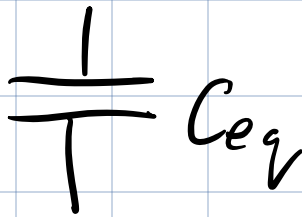Connect together
all top plates
& all btm plates.





Want to represent
the parallel combo as
a single "equivalent"
capacitor C_{eq} .

Result:

$$C_{eq} = C_1 + C_2 + C_3$$

C_{eq} is given by
sum of each of
parallel capacitances.

Series combination

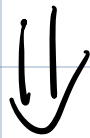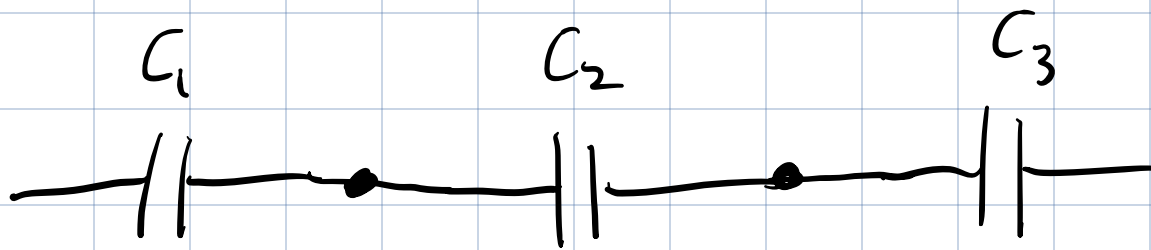

In a series combination, line up capacitors & connect nearest plates to one another.


In this case, we will find

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Inverses of individual capacitances add to give the inverse of C_{eq} .

In series combination, it will always be true
case that $C_{eq} < C_1, C_2, C_3$

Parallel combination of capacitors.

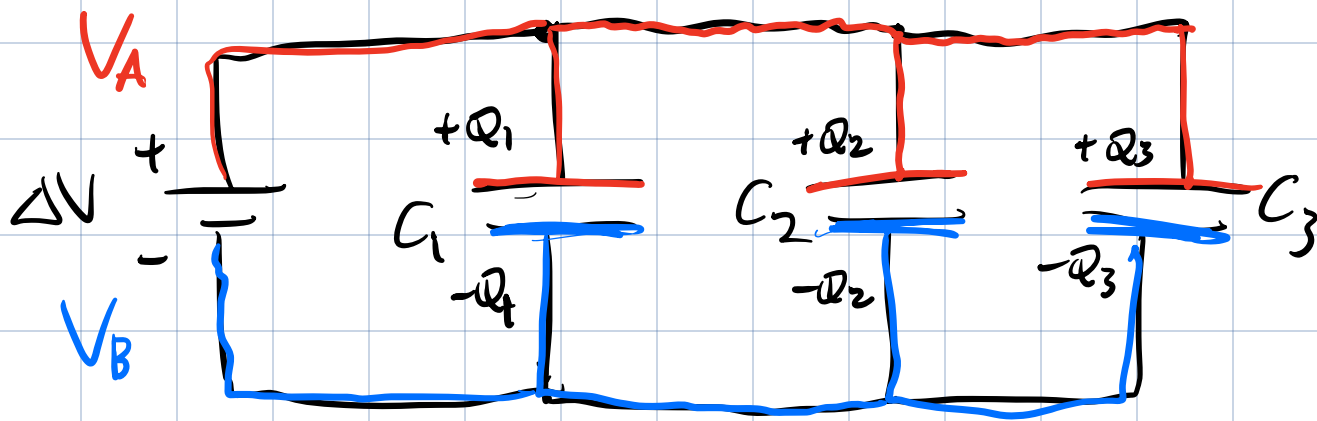

— one single conductor

— another single conductor

After the capacitors charge up, there is
no more flow charge \Rightarrow conductors are
in equil.

\Rightarrow Each conductor is at a uniform
or constant potential.

∴ top plates of each capacitor is at same potential V_A

bottom plates are all @ pot. V_B .

∴ Potential difference across each parallel cap is the same:

$$\Delta V_1 = \Delta V_2 = \Delta V_3 = V_A - V_B \equiv \Delta V$$

Recall, by definition, $C = \frac{Q}{\Delta V} \Rightarrow Q = C \Delta V$

$$Q_1 = C_1 \Delta V$$

$$Q_2 = C_2 \Delta V$$



$$Q_3 = C_3 \Delta V$$

∴ total charge Q stored by the parallel combination is

$$Q = Q_1 + Q_2 + Q_3$$

$$\therefore Q = C_1 \Delta V + C_2 \Delta V + C_3 \Delta V$$
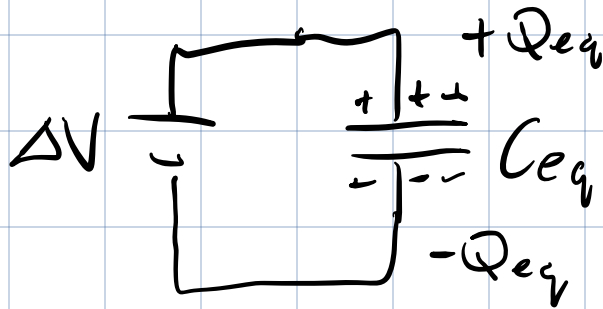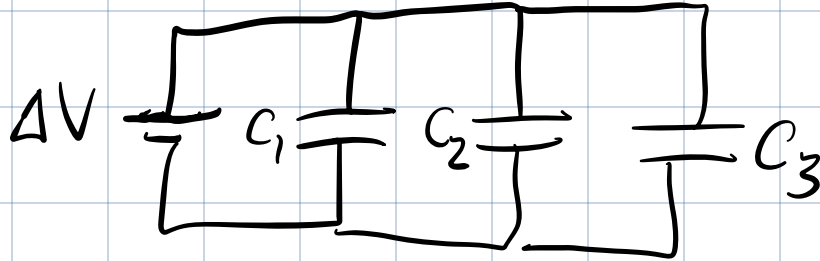
$$Q = (C_1 + C_2 + C_3) \Delta V \quad (1)$$



For C_{eq} , the stored charge is

$$Q_{eq} = C_{eq} \Delta V$$

C_{eq} must stored same total charge

\therefore

$$Q_{eq} = Q = C_{eq} \Delta V \quad (2)$$

Eqs. ① & ② each calculate the stored charge Q & must be equal.

$$\textcircled{1} = \textcircled{2}$$

$$(C_1 + C_2 + C_3) \cancel{\Delta V} = C_{eq} \cancel{\Delta V}$$

$$\therefore C_{eq} = C_1 + C_2 + C_3$$

Parallel capacitors.