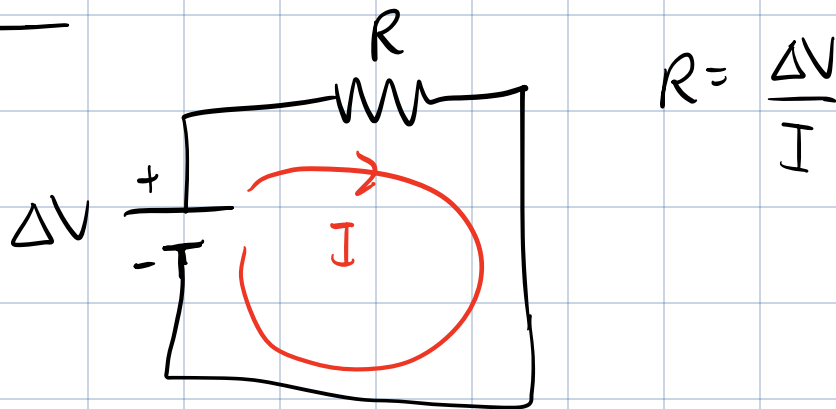



- To do:
- Complete HW 7 by 23:59 today
 - No Pre-Lab # 5
 - Tutorials resume next week.

Last Time:




$$R = \frac{\Delta V}{I}$$

Capacitors in Parallel:

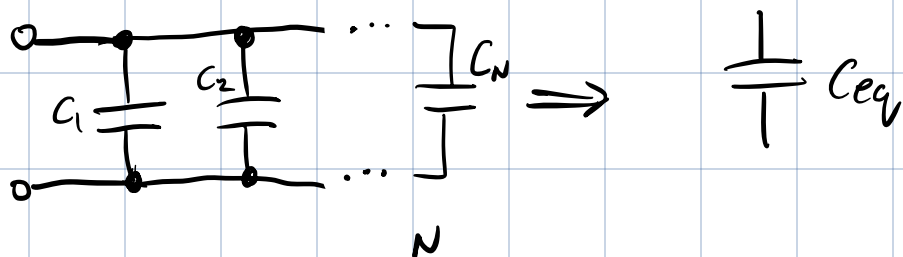


$$C_{eq} = \sum_{i=1}^N C_i = C_1 + C_2 + \dots + C_N$$

Capacitors in Series :

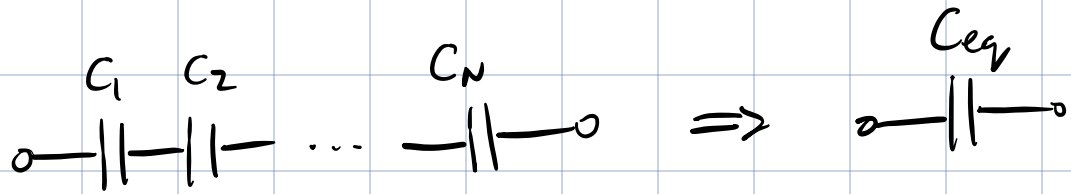

$$\frac{1}{C_{eq}} = \sum_{i=1}^N \frac{1}{C_i} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

Proof: Capacitors in Series.

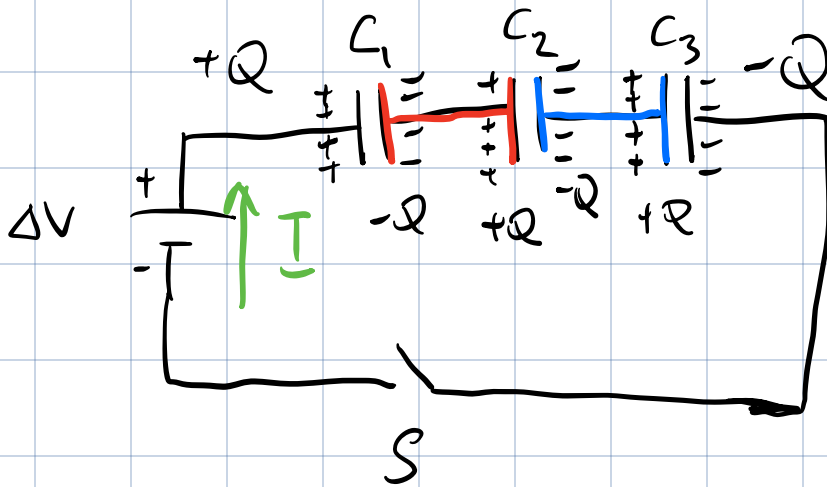


- Start w/ uncharged capacitors & switch S open.
- Conductors highlighted red & blue are neutral & isolated from rest of circuit. So, when switch S is closed, the red & blue conductors must remain overall neutral.

- When switch is closed, battery causes charge to transfer from right plate of C_3 to left plate of C_1


- The neutral conductors (red & blue) become polarized (separation of charge),

\Rightarrow Each of the series capacitors carry the same charge:

$$Q_1 = Q_2 = Q_3 \equiv Q$$

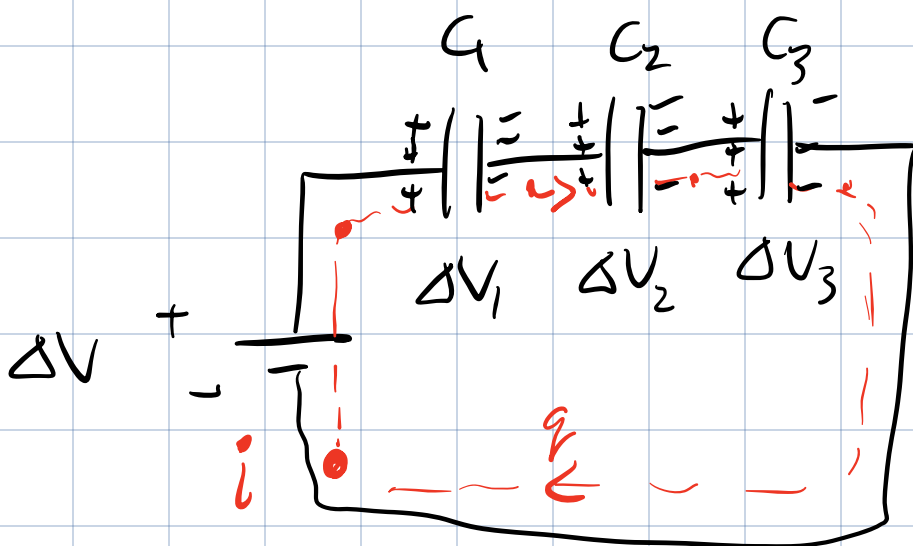

Aside: Gravitational P.E.

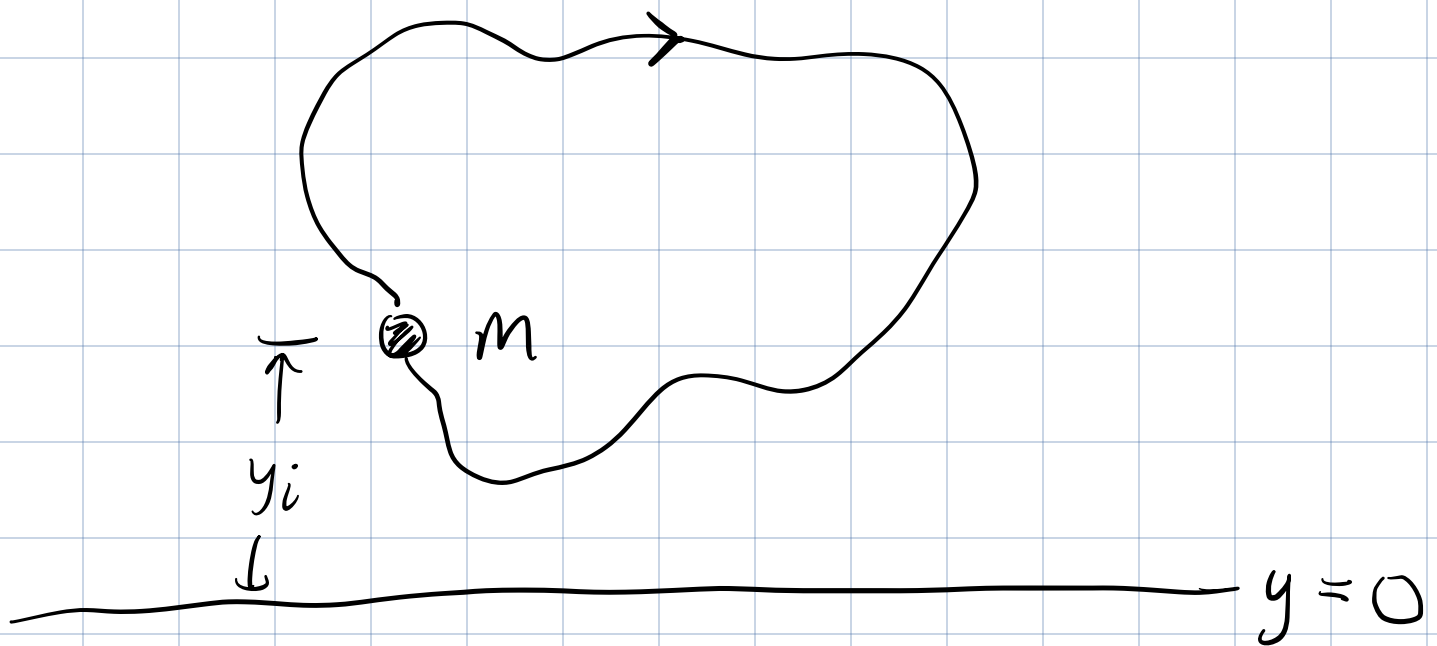

If we move mass m through a loop in a constant gravitational field, then net change in gravitational P.E. is zero.

$$\Delta U_g = mg \Delta y$$

For a loop, $\Delta y = 0 \therefore \Delta U_g = 0$

Now consider a charge q moving around a circuit.

Every time the circuit has a change in potential/voltage ΔV , the corresponding change in P.E. of the charge is $\Delta U = q\Delta V$.

If we start in lower-left corner of circuit & go around clockwise, track the changes in P.E. of q :

1. Cross battery from neg to pos. terminal.
Gain voltage ΔV & P.E. $q\Delta V$.

2. Cross C_1 from pos. to neg. plate & loss
voltage $-\Delta V_1$ & P.E. $-q\Delta V_1$

3. Cross C_2 loss P.E. $-q\Delta V_2$
" C_3 " " $-q\Delta V_3$

4. We're now back @ starting point.
Net change in P.E. of q must be zero (conservation of energy).

$$\Delta U_{\text{net}} = \underbrace{q \Delta V}_{\text{battery}} - \underbrace{q \Delta V_1}_{C_1} - \underbrace{q \Delta V_2}_{C_2} - \underbrace{q \Delta V_3}_{C_3} = 0$$

Divide by q :

$$\Delta V - \Delta V_1 - \Delta V_2 - \Delta V_3 = 0$$

In general, for any closed loop in a circuit, the net change in voltage around the loop must be zero.

Kirchhoff Voltage Loop Rule

$$\textcircled{1} \quad \Delta V = \Delta V_1 + \Delta V_2 + \Delta V_3$$

For series cap. example.

For capacitors, we know $C = \frac{Q}{\Delta V}$



$$\Delta V = \frac{Q}{C} \text{ for a cap.}$$

$$\Delta V_1 = \frac{Q_1}{C_1}$$



$$\Delta V_2 = \frac{Q_2}{C_2}$$

$$\Delta V_3 = \frac{Q_3}{C_3}$$

Subbing into ①:

$$\Delta V = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3}$$

Equivalent Capacitor

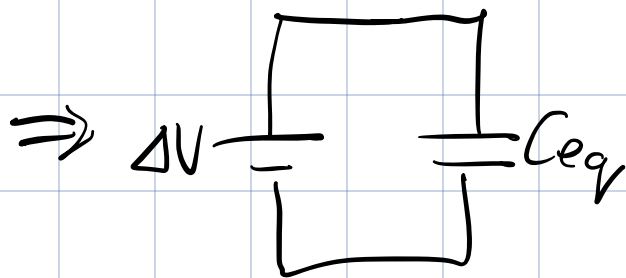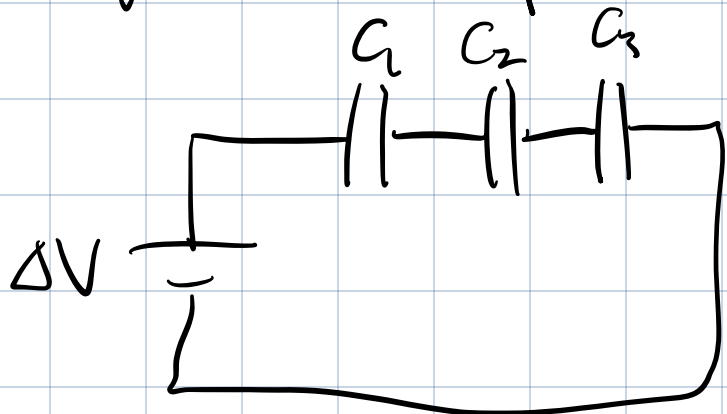

Require $Q_{eq} = Q_1 = Q_2 = Q_3 = Q$

$$\sim Q_{eq} = C_{eq} \Delta V$$


$$\Delta V = \frac{Q_{eq}}{C_{eq}}$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

Series combination of capacitors

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

RC Circuit: battery, cap, resistor

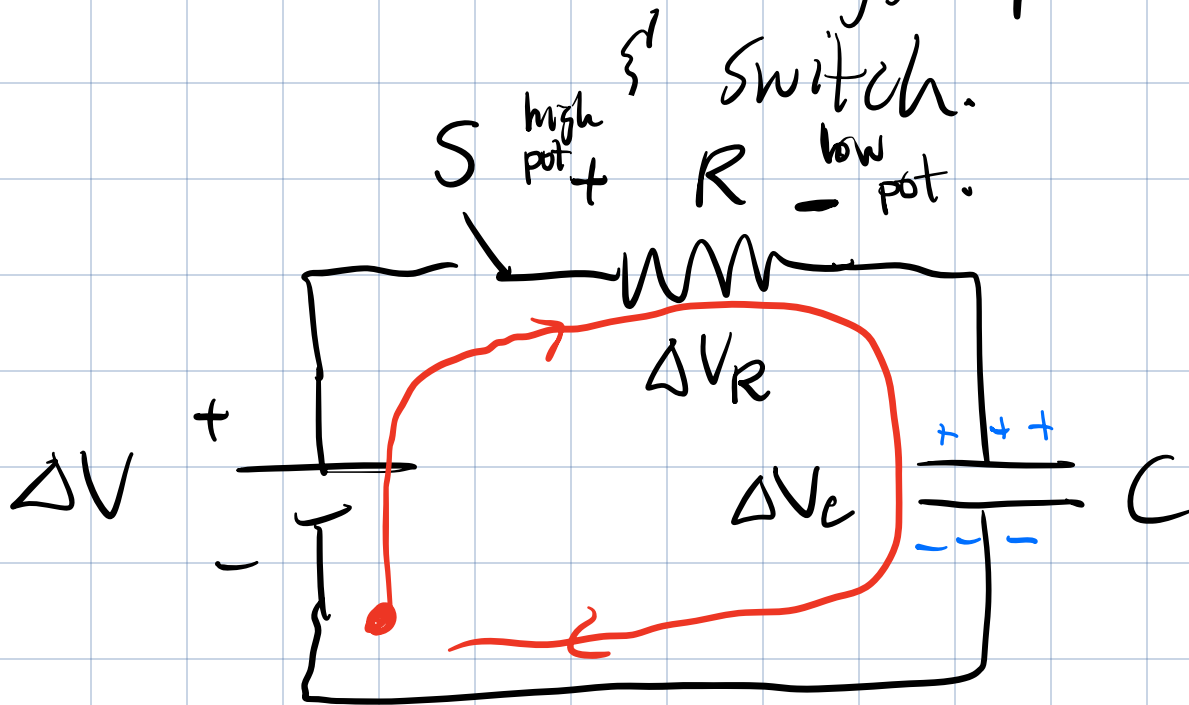

If C is initially uncharged & switch S is closed at time $t = 0$.

How do the current $I(t)$ & charge on the cap $Q(t)$ evolve with time?

Kirchhoff Loop Rule requires:

$$\underbrace{\Delta V}_{\text{battery}} - \underbrace{\Delta V_R}_{\text{resistor}} - \underbrace{\Delta V_C}_{\text{cap.}} = 0$$

$$\Delta V_R = IR$$


$$\Delta V_C = \frac{Q}{C}$$

$$\Delta V - IR - \frac{Q}{C} = 0$$

Recall $I = \frac{\Delta Q}{\Delta t}$

$$\therefore \Delta V = R \frac{\Delta Q}{\Delta t} + \frac{Q}{C}$$

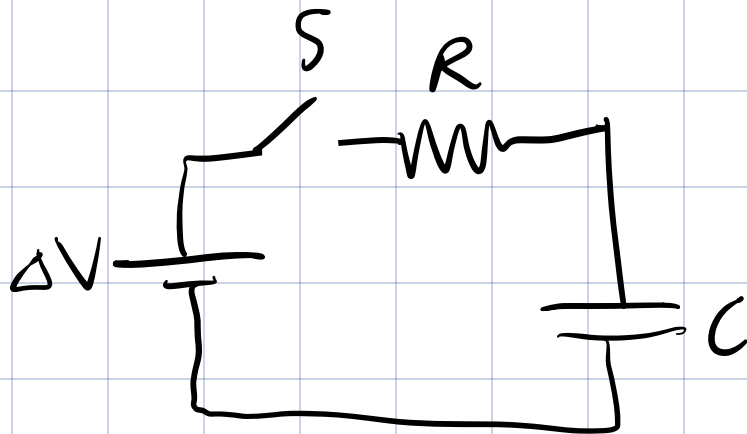This expression can be used to determine ~~the~~ how charge changes w/ time.





If S is just closed $\Delta V_C = 0$ (initially uncharged)

Initially, $\Delta V_R = \Delta V$ (at $t=0$)

$$\therefore IR = \Delta V$$
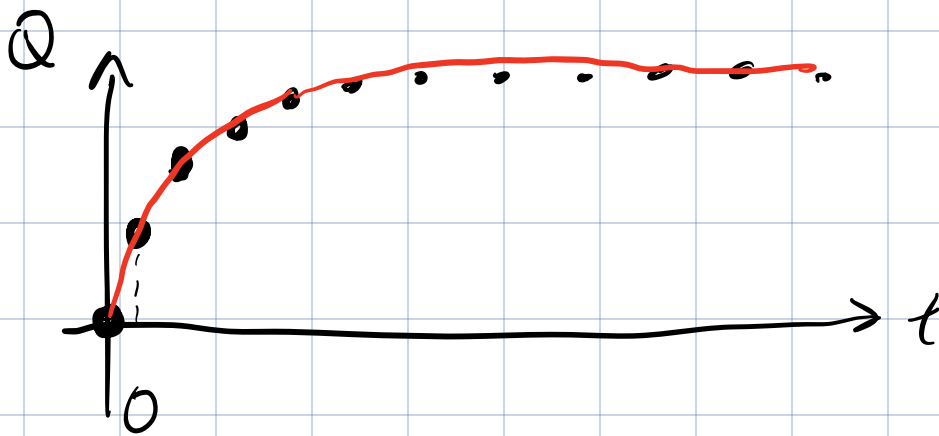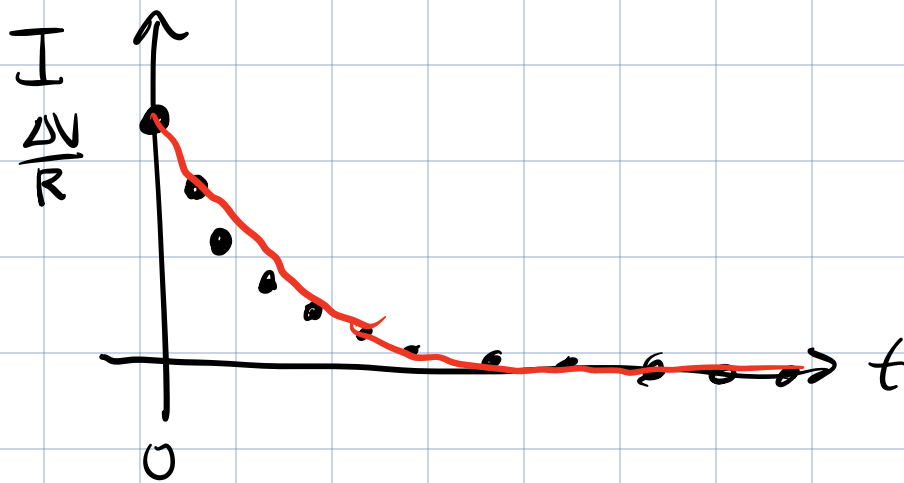
$$I = \frac{\Delta V}{R} \quad (\text{large current})$$



After a short time Δt , capacitor accumulates some charge $\Delta Q = I \Delta t$

Now, voltage ΔV_C across capacitor is non-zero.
 \therefore Voltage across resistor & the current decrease.