
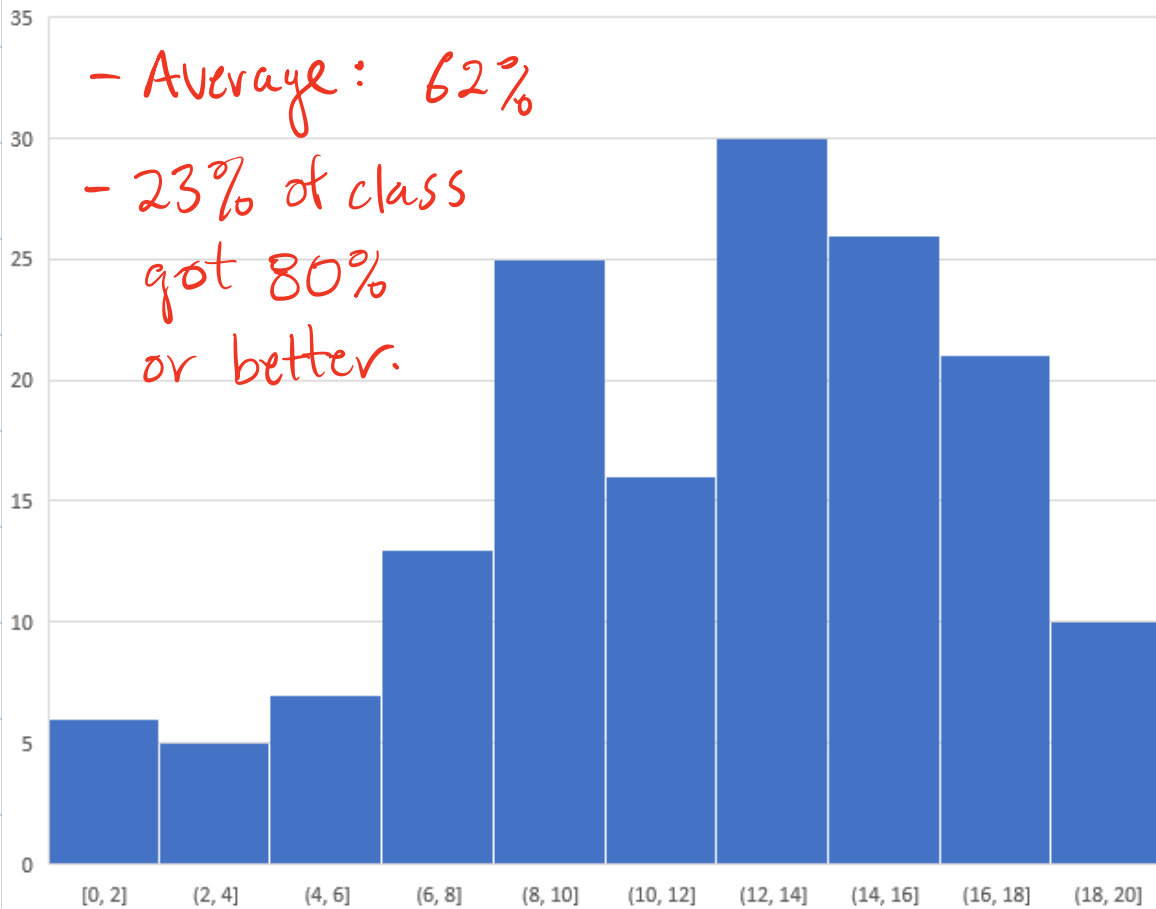


- Complete Prairie Learn HW by Friday @ 23:59
- No Pre-Lab # 5
- Tutorials resume this week.

Midterm dist'n

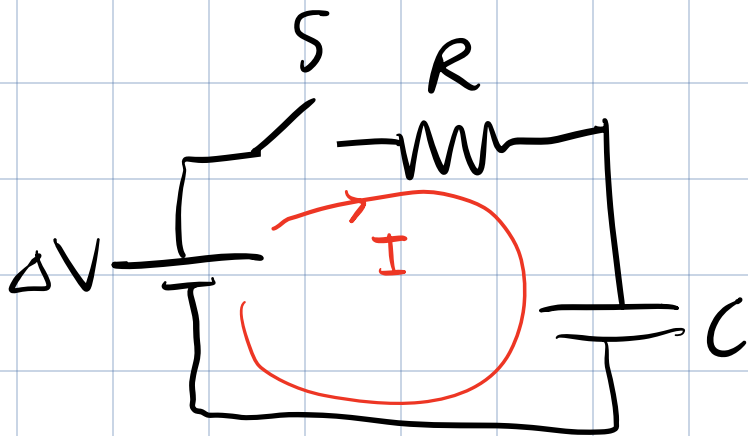

Last Time: RC Circuit.



$$C = \frac{Q}{\Delta V_c}$$

$$\Delta V_c = \frac{Q}{C}$$

Loop Rule $\Delta V - IR - \frac{Q}{C} = 0$ *

Eq'n (0).

Solve Eq (0) for current I.

$$I = \frac{\Delta V}{R} - \frac{Q}{RC} \} \equiv \tau$$

(tau)
time constant.

$\equiv I_0$
↑

current at $t=0$ when
the switch is closed & capacitor volt.
is zero.

Define $I_0 = \frac{\Delta V}{R}$ $\tau = RC$

∴ the current at any time in our RC circuit is given by:

$$I = I_0 - \frac{Q}{\tau} \quad (1)$$

Since $I = \frac{\Delta Q}{\Delta t}$, we can calc. how much charge is added to the cap. in time Δt

using: $\Delta Q = I \Delta t \quad (2)$

After finding ΔQ , know that new charge on the cap is the original value of Q plus ΔQ

$$Q \rightarrow Q + \Delta Q$$

Likewise $t \rightarrow t + \Delta t$

Strategy:

Start w/ known values of
 $\Delta V, R, C \Rightarrow$ constants.

Pick a value for time interval Δt
 \Uparrow

Calc. $I_0 = \frac{\Delta V}{R}$ $\tau = RC \Leftarrow$ constants

Start w/ $Q=0$ at $t=0$

1. Use Eq. (1) to find I .
2. Use Eq. (2) to find ΔQ (change in cap. charge during time interval Δt).
3. Update the value of $Q \Rightarrow Q + \Delta Q$
4. Update the time $t \Rightarrow t + \Delta t$
5. Return to step 1. $\{$ iterate until Q reaches its max. value $\& I \rightarrow 0$.

See course website for an example implementation.

Exact solution

$$I = I_0 - \frac{Q}{L} \quad (1)$$

$$I = \frac{dQ}{dt}$$

$$\frac{dQ}{dt} = I_0 - \frac{Q}{L}$$

$$dQ = \left(I_0 - \frac{Q}{L} \right) dt$$

$$\frac{dQ}{I_0 - \frac{Q}{L}} = dt$$

Integrate

$$\int_{Q=0}^Q \frac{dQ}{I_0 - \frac{Q}{L}} = \int_{t=0}^t dt$$

substitution

$$u = I_0 - \frac{Q}{L}$$

$$du = -\frac{1}{L} dQ$$

$$dQ = -L du$$

$$\text{when } Q=0, \quad u = I_0$$

$$Q=Q, \quad u = I_0 - \frac{Q}{\tau}$$

$$\int_{u=I_0}^{I_0 - \frac{Q}{\tau}} \frac{-\tau du}{u} = t$$

$$\int_{u=I_0}^{I_0 - \frac{Q}{\tau}} \frac{du}{u} = -\frac{t}{\tau}$$

$$\ln u \Big|_{I_0}^{I_0 - \frac{Q}{\tau}} = -\frac{t}{\tau}$$

$$\Rightarrow \ln\left(I_0 - \frac{Q}{\tau}\right) - \ln(I_0) = -\frac{t}{\tau}$$

$$\therefore \ln\left(\frac{I_0 - \frac{Q}{\tau}}{I_0}\right) = -\frac{t}{\tau}$$

$$\ln\left(1 - \frac{Q}{\tau I_0}\right) = -\frac{t}{\tau}$$


solve for Q .

$$1 - \frac{Q}{\tau I_0} = e^{-t/\tau}$$

$$\therefore \frac{Q}{\tau I_0} = 1 - e^{-t/\tau}$$

$$\begin{aligned} \text{Finally } Q &= \tau I_0 (1 - e^{-t/\tau}) \\ &= \cancel{(RC)} \frac{\Delta V}{R} (1 - e^{-t/\tau}) \end{aligned}$$
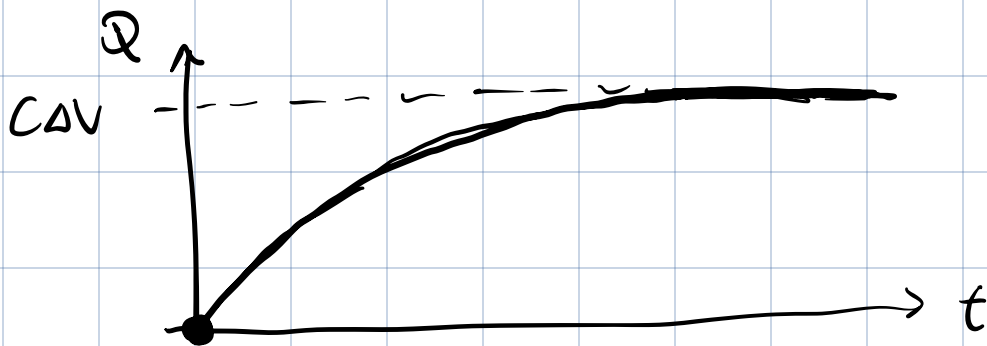
$$\therefore Q = C \Delta V (1 - e^{-t/\tau})$$



$$I = \frac{dQ}{dt} = \frac{d}{dt} (C \Delta V (1 - e^{-t/\tau}))$$

$$= C \Delta V \left[\cancel{\frac{d}{dt} (1)} - \underbrace{\frac{d}{dt} (e^{-t/\tau})}_{-\frac{1}{\tau} e^{-t/\tau}} \right]$$

$$\therefore I = C \Delta V \frac{1}{\tau} e^{-t/\tau}$$

$$= \cancel{C \Delta V} \frac{1}{\cancel{RC}} e^{-t/\tau}$$

$$I = I_0 e^{-t/\tau}$$

current in RC
circuit.

