

PHYS 121

March 8, 2024

- ✓ Complete PrairieLearn HW by today @ 23:59
- ✓ Complete Pre-Lab #6 before the start of Lab #6
- ✓ Quiz #2 will be on Wednesday, March 20  
⇒ See course website for details.

Last Time:

$$I = env_d A$$

$$J = \frac{I}{A} = env_d$$

Ohmic materials obey  $\vec{J} = \sigma \vec{E}$   
↓  
 $\Delta V = IR$


where  $R = \frac{1}{\sigma} \frac{L}{A} = \rho \frac{L}{A}$

Today: When is  $\Delta V$  across a resistor positive  
& when is it negative?

Rule of Thumb:

- If you cross a resistor in the dir'n of the current I, the voltage change is negative
- If you cross a resistor in opposite dir'n of current I, the voltage change is positive.

CASE 1

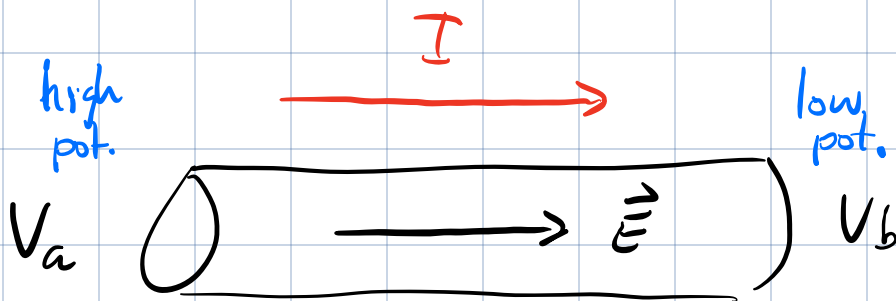

cross resistor in dir'n of I  $\rightarrow$

Track changes in voltage.

$$V_a + \underbrace{\Delta V_R}_{\text{negative}} = V_b$$


Voltage diff.  
across resistor

$$\therefore \Delta V_R = V_b - V_a < 0 \text{ (neg.)}$$

$\uparrow$              $\uparrow$   
low            high

$$\therefore \Delta V_R = -IR \text{ when cross resistor in dir'n of } I.$$

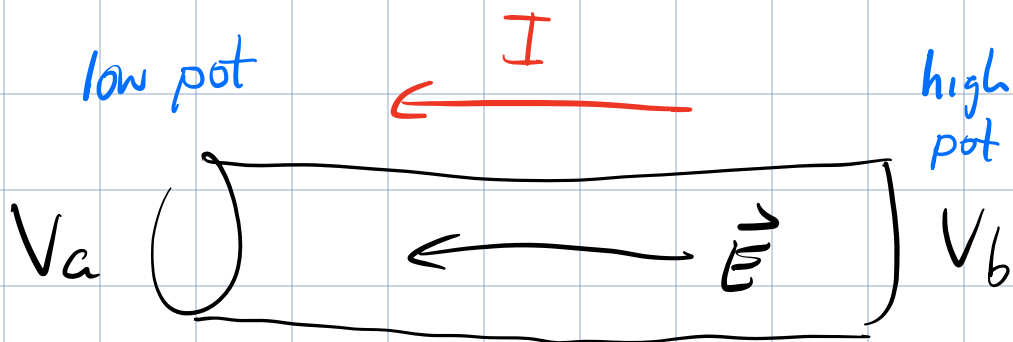CASE 2: Cross R antiparallel to current I



cross R in opp. dir'n of I  $\rightarrow$

$$V_a + \Delta V_R = V_b$$

$$\therefore \Delta V_R = V_b - V_a > 0 \text{ (pos.)}$$

$\uparrow$              $\uparrow$   
high            low

When cross  $R$  in dir'n opp. of the current:

$$\Delta V_R = +IR$$

## Power Dissipated by a Resistor


(OSUPV2 Sec. 9.5)

Recall that power is defined as:

$$P = \frac{\text{change in energy}}{\text{time interval}}$$

$$[P] = \frac{\text{J}}{\text{s}} = \text{W} \quad (\pm \text{Watt})$$

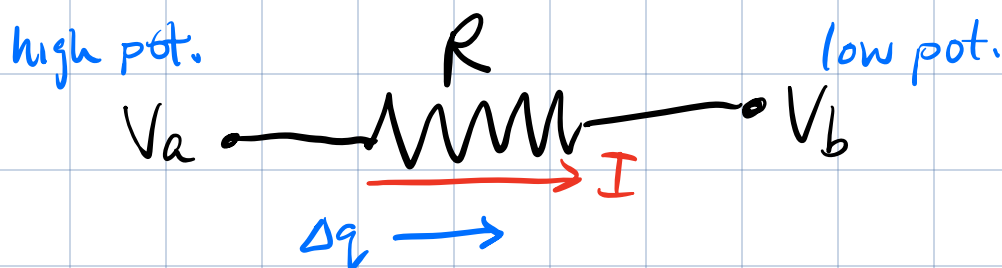Consider an amount of charge  $\Delta q > 0$  that crosses a resistor  $R$  in time  $\Delta t$ .



The charge  $\Delta q$  loses pot.  $\Delta V_R$  when it crosses  $R$ .

The corresponding loss of P.E. of the charge is :

$$\Delta U = \Delta q \Delta V_R$$

If time to cross  $R$  is  $\Delta t$ , then the dissipated power is :


$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta q \Delta V_R}{\Delta t} = \frac{\Delta q}{\Delta t} \Delta V_R$$

$\underbrace{\hspace{1.5cm}}_I$

Power dissipated by resistor is  $P = I \Delta V_R$

The dissipated is transformed into heat.

We know  $\Delta V_R = \underline{IR}$

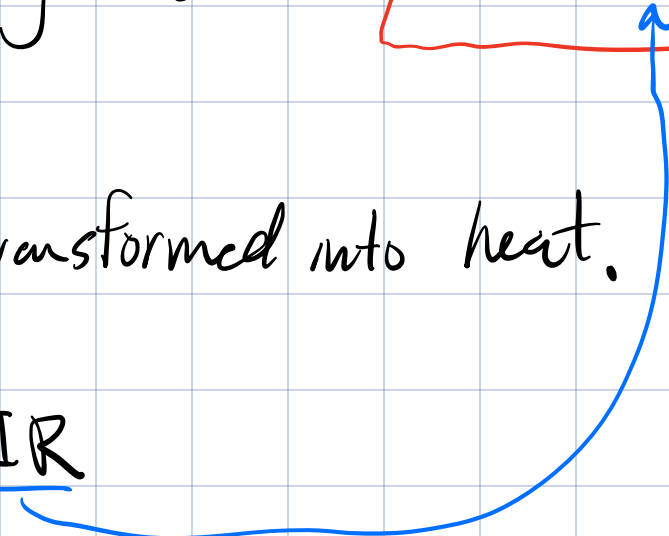

$$P = I(IR) = I^2R$$


$$I = \frac{\Delta V_R}{R}$$

$$P = \left(\frac{\Delta V_R}{R}\right)^2 R = \frac{(\Delta V_R)^2}{R}$$

Power dissipated by a resistor :

$$P = I \Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$

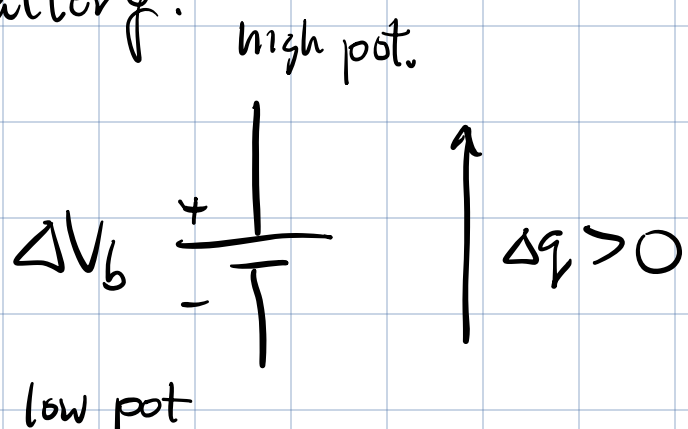In a similar way, we can determine the power supplied by a voltage source, such as a battery.



Charge  $\Delta q > 0$  crosses batt. from neg. to pos. terminal in time  $\Delta t$ .

$\Delta q$  gains pot.  $\Delta V_b$   $\{$  P.E. of  $\Delta U = \Delta q \Delta V_b$

$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta q}{\Delta t} \Delta V_b = \boxed{I \Delta V_b}$$

$\nearrow$  power supplied by battery

power supplied by battery.

Eg. The nichrome wire in a toaster has a resistance of  $24 \Omega$ . If the outlet in the wall supplies  $120 \text{ V}$ , find:

- resulting current in toaster
- The power dissipated by resistor (nichrome wire)
- Power supplied by outlet.

$$(a) \quad I = \frac{\Delta V}{R} = \frac{120 \text{ V}}{24 \Omega} = 5 \text{ A}$$

$$(b) \quad P = I^2 R = 600 \text{ W}$$

} dissipated power

$$P = I \Delta V = 600 \text{ W}$$

$$P = \frac{(\Delta V)^2}{R} = 600 \text{ W}$$

(c)  $P_{\text{supplied}} = I \Delta V = 600 \text{ W}.$

Energy conservation.

The dissipated power heats the nichrome wire to about  $500^\circ\text{C}$ . The wire heats the surrounding air to about  $150^\circ$  which toasts the bread.

---

Recall Kirchhoff Voltage Loop Rule


sum of  
voltage changes  
around a  
closed loop

$$\sum_i \Delta V_i = 0$$

$\Rightarrow$  Conservation of energy.



# Kirchhoff Junction Rule.

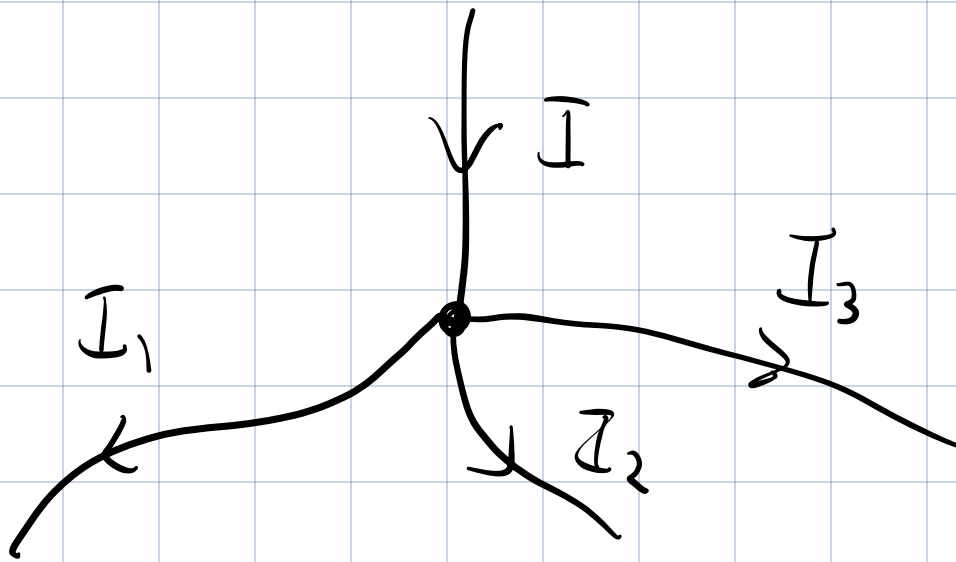

When a current encounters a junction, some takes path 1, some takes path 2, & some takes path 3. However, the net current into the junction must equal net current leaving the junction. There can be no charge created or destroyed at junction.


⇒ Conservation of charge.

Junction Rule:

current in = current out

In our example:  $I = I_1 + I_2 + I_3$

Eg.

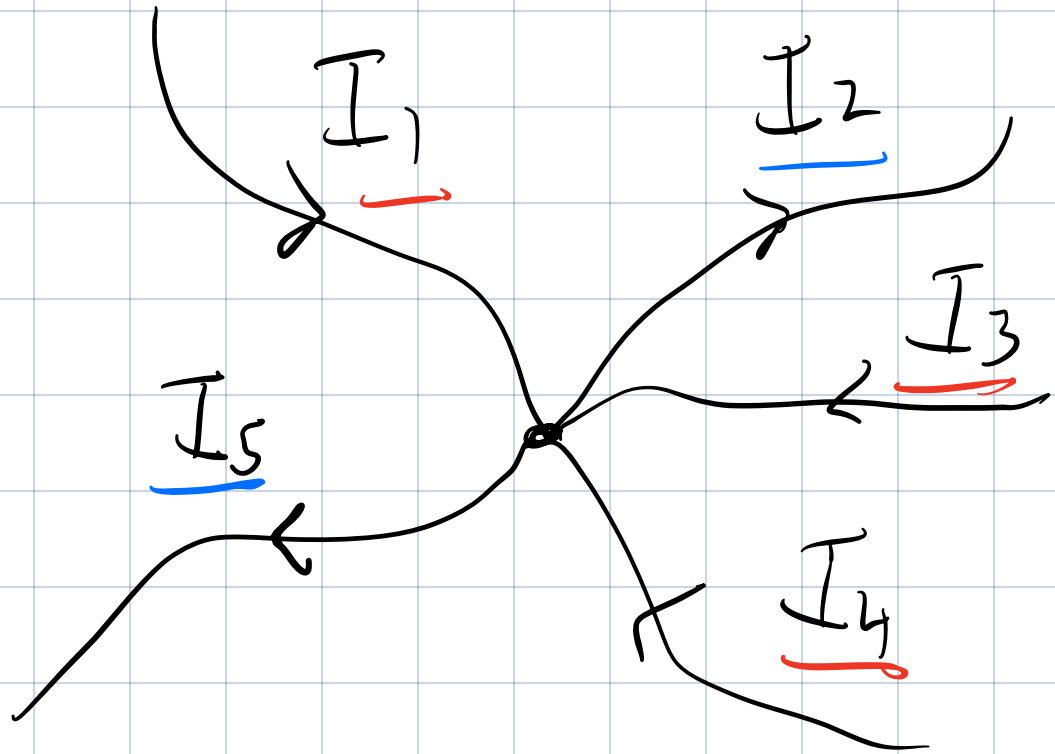

$$\underbrace{I_1 + I_3 + I_4}_{\text{current in}} = \underbrace{I_2 + I_5}_{\text{current out.}}$$