

PHYS 121

March 11, 2024

- ✓ - Complete Prairie Learn HW by Friday @ 23:59
- ✓ - Complete Pre-Lab #6 before the start of Lab #6
- ✓ - Quiz #2 will be on Wednesday, March 20  
⇒ See course website for details.

Recall Kirchhoff Rules:

1. Loop Rule - sum of voltage changes around a closed loop is zero

$$\sum_i \Delta V_i = 0$$


2. Junction Rule - total current into a junction equals total current leaving the junction

$$I_{\text{tot, in}} = I_{\text{tot, out}}$$

Last Time:

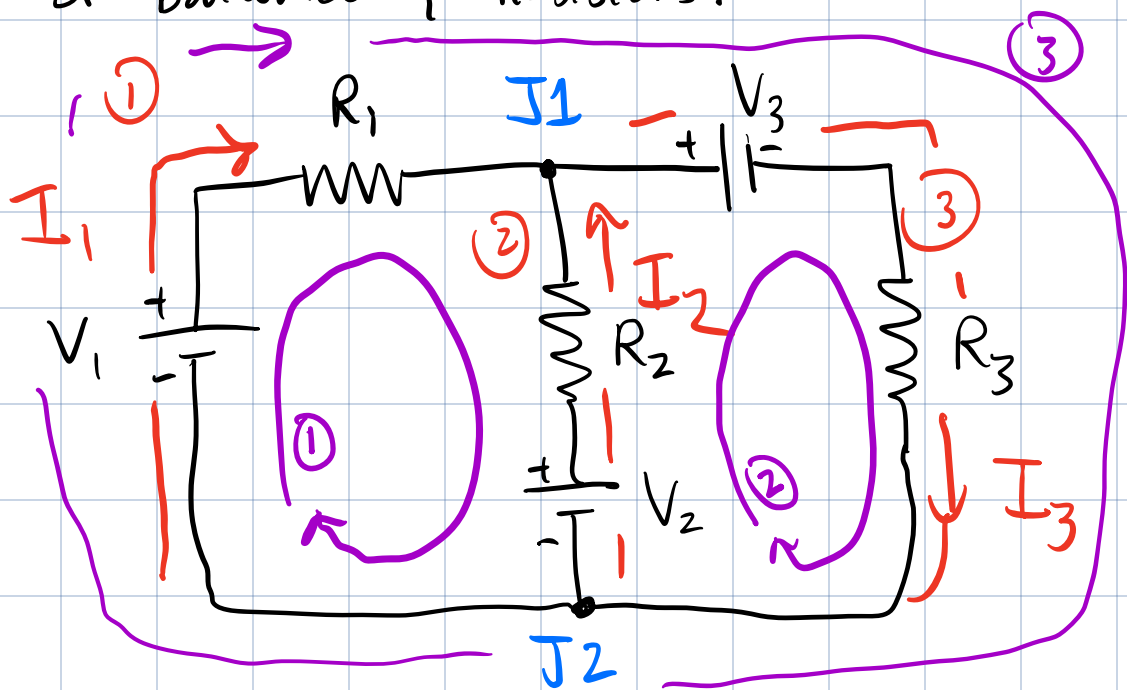1. If cross resistor in dir'n of current  $\Rightarrow \Delta V_R = -IR$ .
2. If cross resistor in dir'n opposite of current  $\Rightarrow \Delta V_R = +IR$ .

Eg. Consider the following circuit consisting of batteries & resistors.



Typically in a circuit like this will have some unknowns to solve for (currents, battery voltage, resistor values)

Step a system of  $N$  eqns to solve for  $N$  unknowns.

Eq. In the circuit above find the current in each branch of circuit (current in each resistor).

Step 1: Assign a current to each branch of circuit. Label currents & pick a dir'n.

If at the end of the problem we calc. a neg. value for a current, it just means we chose the wrong dir'n. All other calc. quantities will be correct.

Step 2: Identify the unknowns.

In this example, assume battery voltages and resistor values are known.

Unknowns are:  $I_1$ ,  $I_2$ ,  $I_3$ .

To solve for 3 unknowns, need to construct a system of 3 indep. equations involving the 3 unknowns.

Step 3: Apply the junction to start building our system of eq'ns.

Eq. J1:  $I_{in} = I_{out}$

$$\boxed{I_1 + I_2 = I_3}$$

$\underbrace{\hspace{10em}}_{I_{in}} \qquad \underbrace{\hspace{10em}}_{I_{out}}$

Ⓐ

J2:  $I_3 = I_1 + I_2$

$\underbrace{\hspace{10em}}_{I_{in}} \qquad \underbrace{\hspace{10em}}_{I_{out}}$

Same result from J1 (no new information).

Step 4: Use the loop rule to find the other two required eq'ns.

$$\text{Loop ①: } 0 = +V_1 - I_1 R_1 + I_2 R_2 - V_2$$

neg-to-pos terminal      in the dir'n of  $I_1$       opp. dir'n of  $I_2$       pos. to neg. term

$$\text{Loop ②: } 0 = +V_2 - I_2 R_2 - V_3 - I_3 R_3$$

$$\text{Loop ③: } 0 = +V_1 - I_1 R_1 - V_3 - I_3 R_3$$

3 loop eq'ns. Claim that there are only 2 independent eq'ns.

Consider (Loop ①) + (Loop ②)

$$\Rightarrow (+V_1 - I_1 R_1 + \cancel{I_2 R_2} - \cancel{V_2})$$
$$+ (\cancel{V_2} - \cancel{I_2 R_2} - V_3 - I_3 R_3) = 0 + 0$$

$$\therefore V_1 - I_1 R_1 - V_3 - I_3 R_3 = 0$$

(Loop ③) eq'n.

Since we can construct the third eq'n using the first two, only have two indep. eq'ns.

Step 5: Finalize system of 3 eq'ns.  
→ Use one junction rule  
→ Two loop rule

For the current example:

$$I_1 + I_2 = I_3 \quad \text{(a)}$$

$$V_1 - I_1 R_1 + I_2 R_2 - V_2 = 0 \quad \textcircled{b}$$

$$V_2 - I_2 R_2 - V_3 - I_3 R_3 = 0 \quad \textcircled{c}$$

Step 6: Solve the system of 3 eq'ns for the 3 unknowns (just a math problem).

Eg. Take the circuit drawn above, assume:

$$V_1 = V$$

$$R_1 = R$$

$$V_2 = 2V$$

$$R_2 = 2R$$

$$V_3 = 3V$$

$$R_3 = R$$

System of 3 eq'ns.

$$I_1 + I_2 = I_3 \quad \textcircled{a}$$

$$V - I_1 R + 2I_2 R - 2V = 0$$

$$-\frac{V}{R} - I_1 + 2I_2 = 0 \quad \textcircled{b}$$

$$2V - 2I_2 R - 3V - I_3 R = 0$$

$$-\frac{V}{R} - 2I_2 - I_3 = 0 \quad \textcircled{c}$$

To solve this system, start by using two of the eq'ns to eliminate one of the unknowns.

Sub  $\textcircled{a}$  in  $\textcircled{c}$  to eliminate  $I_3$

$$-\frac{V}{R} - 2I_2 - (I_1 + I_2) = 0$$

$$\therefore -\frac{V}{R} - I_1 - 3I_2 = 0 \quad \textcircled{d}$$

Now, eq'ns  $\textcircled{b}$  &  $\textcircled{d}$  form a system of two eq'ns & two unknowns.

Take  $\textcircled{b} - \textcircled{d}$  to eliminate  $I_1$ .





$$\textcircled{d} \quad -\frac{V}{R} - I_1 - 3(0) = 0$$

$$\therefore I_1 = -\frac{V}{R}$$

Sub known values of  $I_1$  &  $I_2$  into  $\textcircled{a}$

$$I_1 + I_2 = I_3$$
$$-\frac{V}{R} + 0 = I_3$$

$$\Rightarrow \boxed{I_3 = -\frac{V}{R}}$$

b/c  $I_1, I_3$  are neg., these currents run in the opp. dir'n chose at start of the problem.