
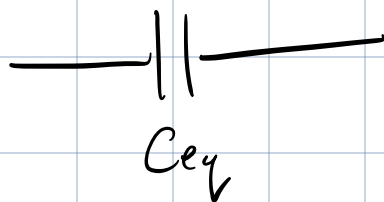


- ✓ - Complete PrairieLearn HW by Friday @ 23:59
- ✓ - Complete Pre-Lab #6 before the start of Lab #6
- ✓ - Quiz #2 will be on Wednesday, March 20
 \Rightarrow See course website for details.


Previously:

Capacitors in Series:

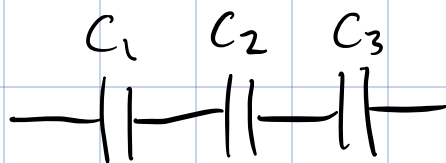

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$




Capacitors in Parallel:

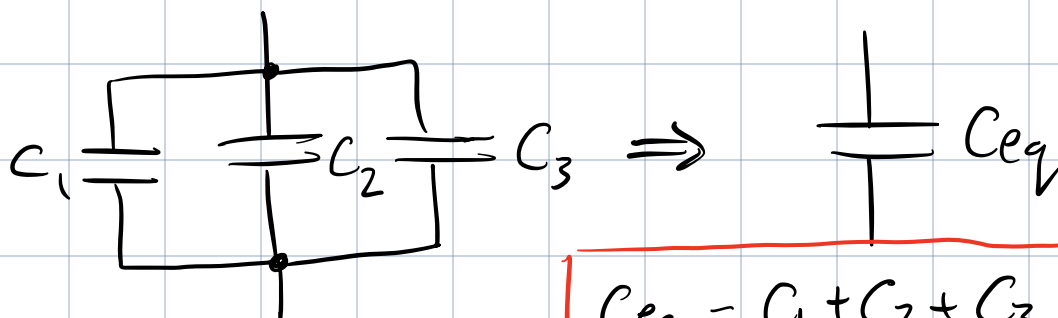

$$C_{eq} = C_1 + C_2 + C_3$$


Today: Will show...

Resistors in series

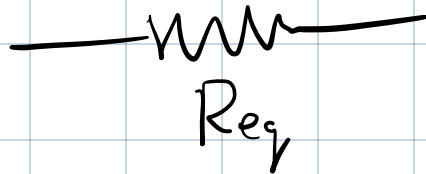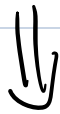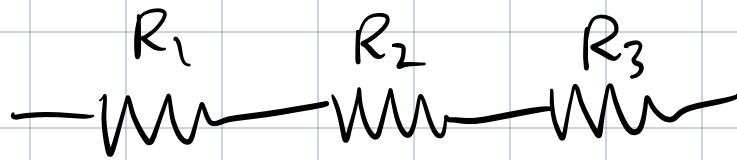



$$R_{eq} = R_1 + R_2 + R_3$$

Resistors in Parallel

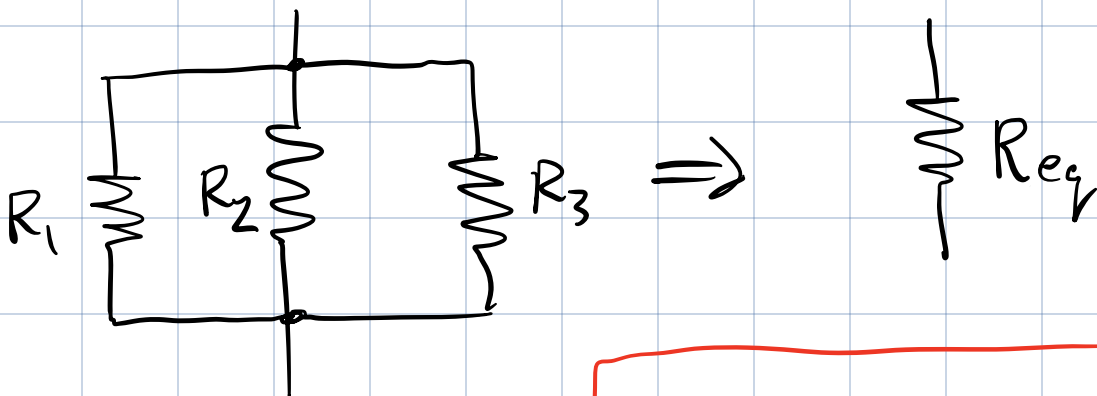


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Resistors in Series (OSUP v2 Sec. 10.2)

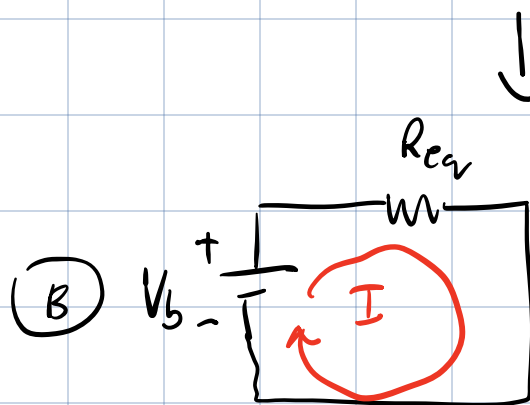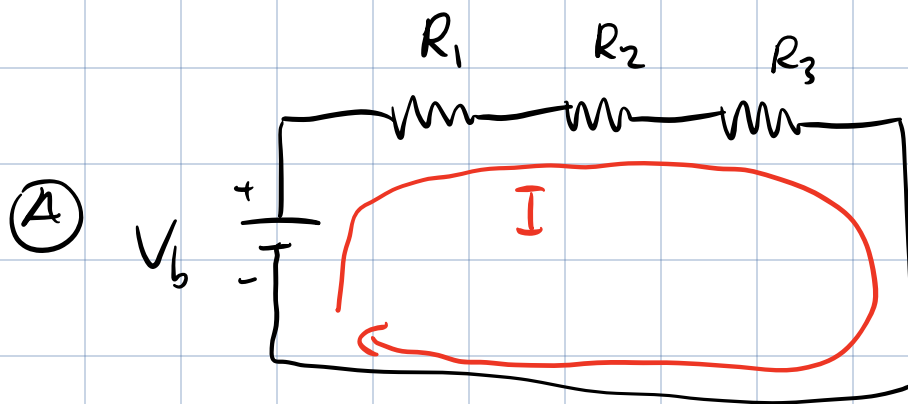

Find R_{eq} that results in the current I in the two circuits.

Consider a small section of circuit (A)

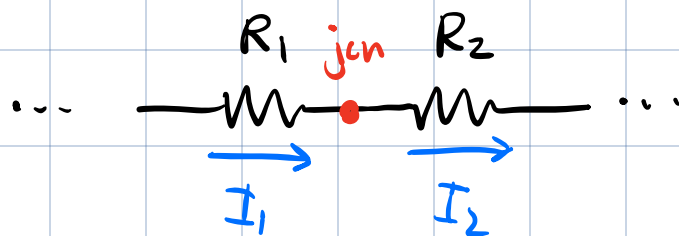

Suppose that resistors R_1 & R_2 could have different currents.

By jcn ($I_{in} = I_{out}$), we require:

$$\begin{array}{ccc} I_1 & = & I_2 \\ \underbrace{\quad} & & \underbrace{\quad} \\ I_{in} & & I_{out} \end{array}$$

⇒ Any components that are in series must have the same current.

⇒ Any components that are in parallel must have the same voltage across them.

Do voltage loop analysis of circuits (A) & (B).

$$(A) \quad V_b - IR_1 - IR_2 - IR_3 = 0$$

$$\therefore V_b = I(R_1 + R_2 + R_3) \quad (i)$$

$$(B) \quad V_b - I R_{eq} = 0$$


$$\therefore V_b = I R_{eq} \quad (ii)$$

$$\text{Require } (i) = (ii)$$

$$\cancel{I}(R_1 + R_2 + R_3) = \cancel{I} R_{eq}$$

$$R_{eq} = R_1 + R_2 + R_3 \quad \text{Resistors in series.}$$

Resistors in Parallel

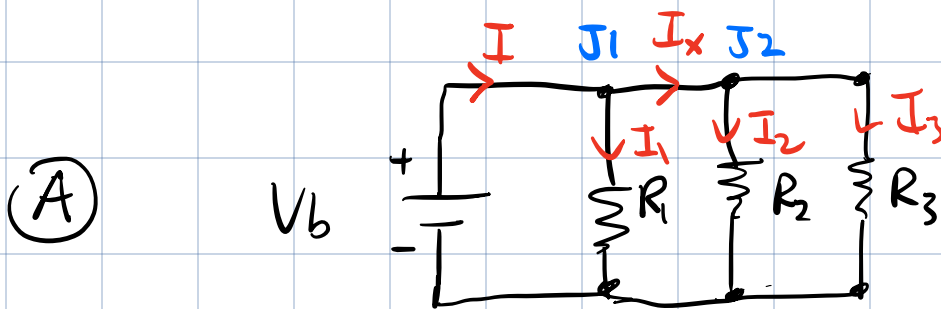

Junction rule @ J_1 :

$$I = I_1 + I_x$$

Junction rule @ J_2 :

$$I_x = I_2 + I_3$$

Combining the two junction rules gives:

$$I = I_1 + I_2 + I_3$$

For R_1 , know $I_1 = \frac{V_1}{R_1}$

" R_2 " $I_2 = \frac{V_2}{R_2}$

" R_3 " $I_3 = \frac{V_3}{R_3}$


$$I = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \quad \textcircled{\times}$$

Since R_1, R_2, R_3, V_b are all in parallel, they must all have the same voltage across them \Rightarrow

$$V_b = V_1 = V_2 = V_3$$

$\therefore \textcircled{\times}$ becomes $I = V_b \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \quad \textcircled{\text{iii}}$

Circuit $\textcircled{\text{B}}$

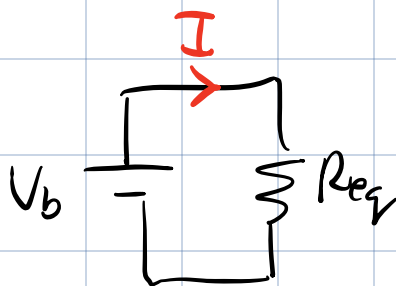

$$I = \frac{V_b}{R_{eq}} \quad \textcircled{\text{iv}}$$

Require (iii) = (iv)


$$\frac{V_b}{R_{eq}} = V_b \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ Resistor in parallel.

————— Cut-off for Quiz #2 —————

OSUPU2 - Chapter 11 (Sec. 11.1 - 11.4)


Imagine a pair of bar magnetic

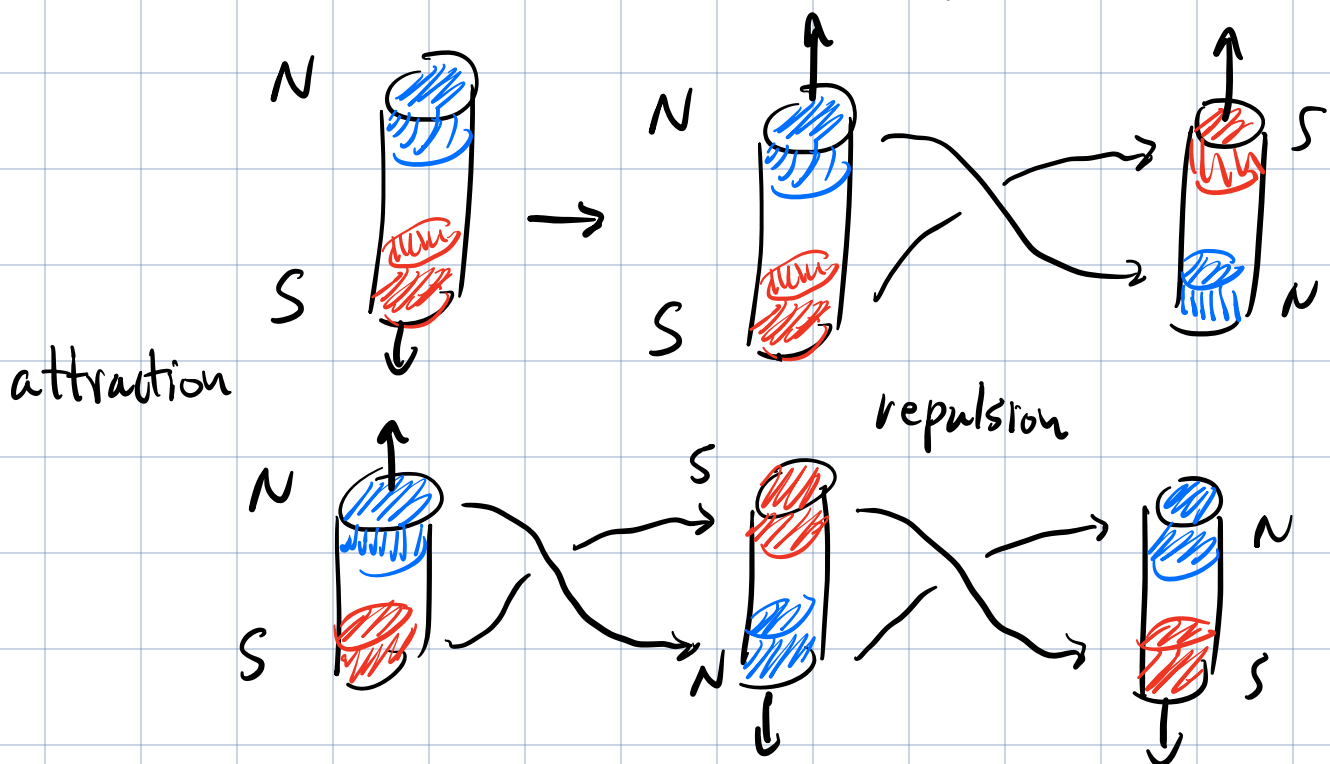


Opposite poles attract } similar to
like poles repel } what we found
for electric charges.

It turns out that, as far as we know, there are no isolated magnetic poles.

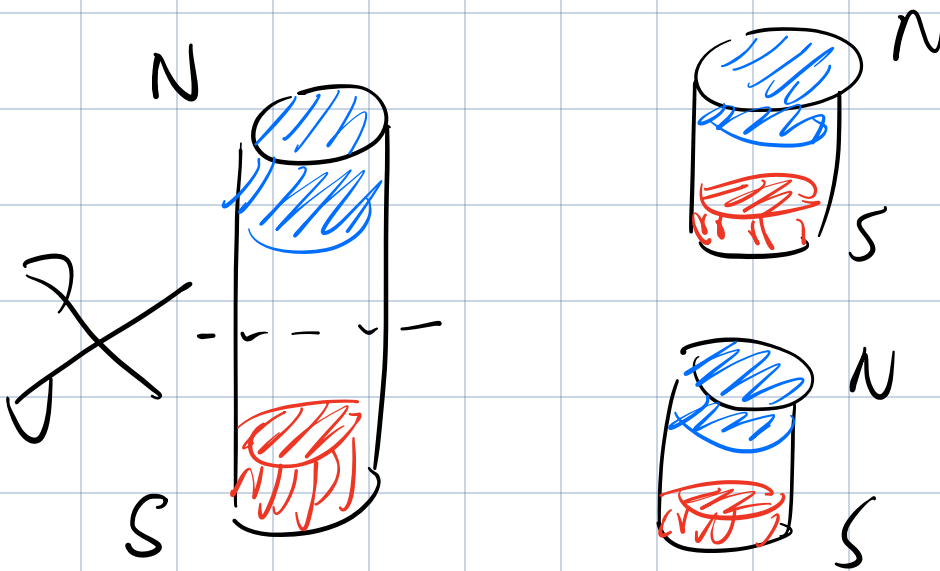
- can't have just a North or just a South poles.
- called monopoles.



Like a water molecule H_2O

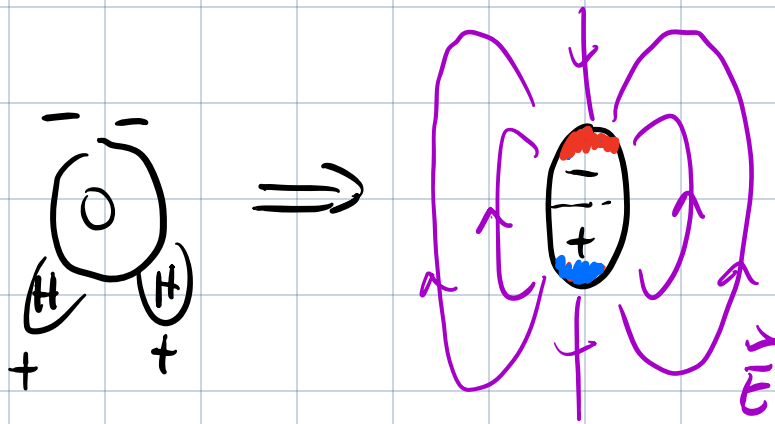

Electric dipole

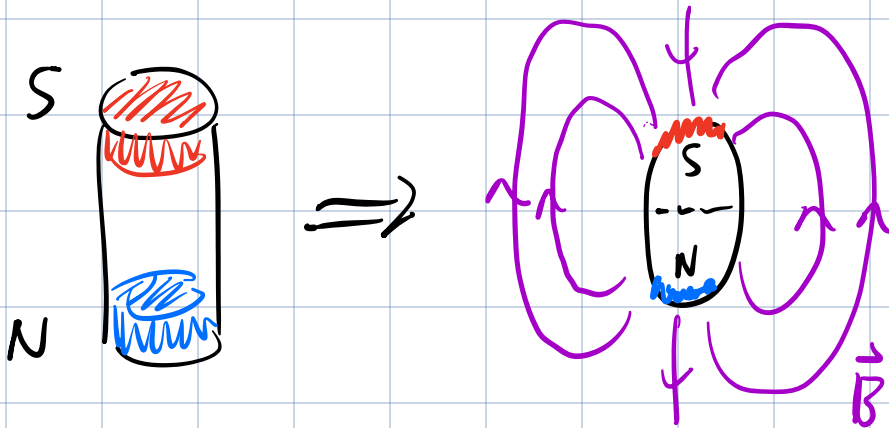

Magnetic dipole

\vec{B} magnetic field lines.


Magnetic fields point away from North poles
& towards south poles

Interaction between charges & magnetic fields.


Imagine placing a compass near a wire.

Compass needle points towards the Earth's North pole due to Earth's magnetic field.

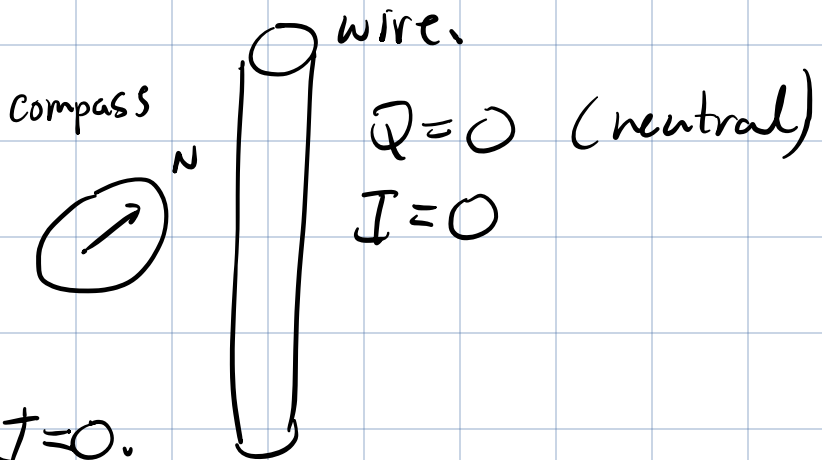
Compass points North. No effect from neutral wire with $I=0$.



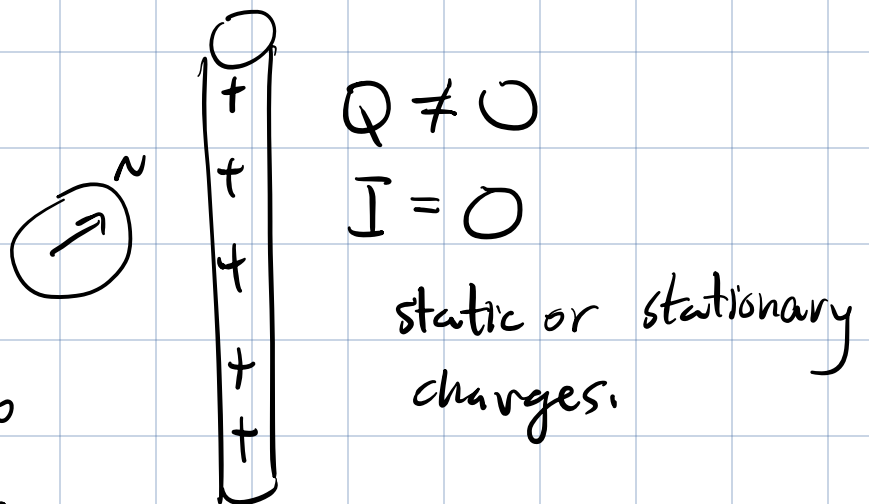With $Q \neq 0$, compass needle still points North. Charged wire has no effect on compass.



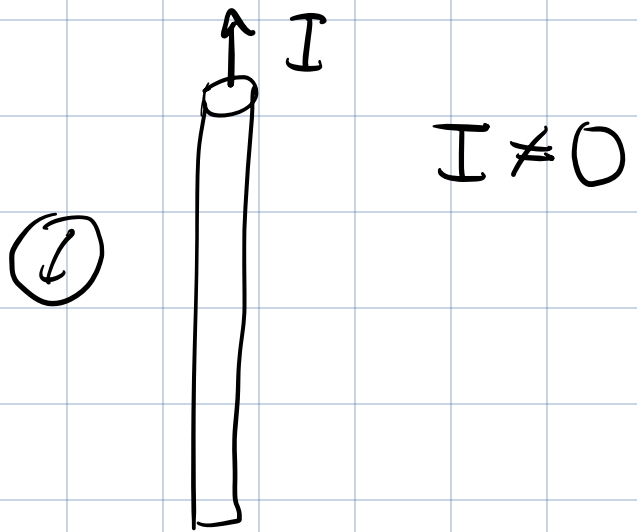with $I \neq 0$
(i.e. the flow of
charge) we observe
that the compass
needle is deflected.



The current in the wire creates a magnetic
field that deflects the compass needle.

Like charge is a source of \vec{E} -fields,
current or moving charges are a source
of \vec{B} -fields.