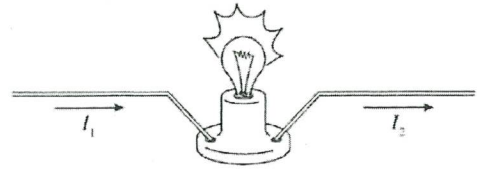


1.

Is I_2 greater than, less than, or equal to I_1 ? Explain.

I_1 & I_2 are in series.
 $\therefore I_1 = I_2$



2.

All wires in this figure are made of the same material and have the same diameter. Rank in order, from largest to smallest, the currents I_1 to I_4 .

Order:


Explanation:

At jcn a $I_1 = I_2 + I_3$

$\therefore I_1 > I_2, I_3$

At jcn b $I_2 + I_3 = I_4$

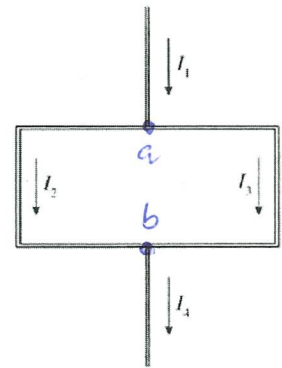$\therefore I_4 > I_2, I_3$ and $I_1 = I_4$



~~Since~~ since wires are same material & same dimensions,
 $I_2 = I_3$. \therefore $I_1 = I_4 > I_2 = I_3$

3.

Metal 1 and metal 2 are each formed into 1-mm-diameter wires. The electric field needed to cause a 1 A current in metal 1 is larger than the electric field needed to cause a 1 A current in metal 2. Which metal has the larger conductivity? Explain.

$J = \sigma E$

$\therefore \frac{I}{A} = \sigma E \Rightarrow \sigma = \frac{I}{AE}$

$I_1 = I_2$
 $A_1 = A_2$

$\therefore \frac{\sigma_1}{\sigma_2} = \frac{E_2}{E_1}$

$E_1 > E_2$

$\therefore \sigma_1 < \sigma_2$

metal 2 has larger conductivity
 \rightarrow requires less \vec{E} to est. the same current.

4. If a metal is heated, does its conductivity increase, decrease, or stay the same? Explain.

as $T \uparrow$, $\sigma \downarrow$.

As temp. increases, get increased thermal vibrations of pos. ions in the metal. This reduces the avg. time τ between e^- scattering events. $\therefore v_d \downarrow$ ~~$\sigma = e^2 n_e v_d$~~
 $\sigma = \frac{e^2 n_e \tau}{m} \downarrow$

5. Wire 1 and wire 2 are made from the same metal. Wire 2 has a larger diameter than wire 1. The electric field strengths E_1 and E_2 in the wires are equal.
 a. Compare the values of the two current densities. Is J_1 greater than, less than, or equal to J_2 ? Explain.

$J = \sigma E$ same metal $\therefore \sigma_1 = \sigma_2$, same $E \therefore E_1 = E_2$
 $\therefore J_1 = J_2$

- b. Compare the values of the currents I_1 and I_2 .

$I = JA$ $A_2 > A_1$ $\therefore I_2 > I_1$


- c. Compare the values of the electron drift speeds $(v_d)_1$ and $(v_d)_2$.

$v_d = \frac{eE}{m} \tau$ $\tau_1 = \tau_2$ (same material)
 $E_1 = E_2 \therefore v_{d,1} = v_{d,2}$

Alternatively, $J = en_e v_d$
 since $J_1 = J_2$, $v_{d,1} = v_{d,2}$

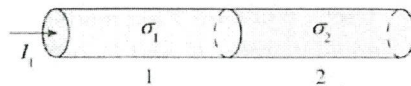6.

A wire consists of two equal-diameter segments. Their conductivities differ, with $\sigma_2 > \sigma_1$. The current in segment 1 is I_1 .



a. Compare the values of the currents in the two segments. Is I_2 greater than, less than, or equal to I_1 ? Explain.

$I_1 = I_2$ the segments are in series.

b. Compare the strengths of the current densities J_1 and J_2 .

$J_1 = J_2$ $J = \frac{I}{A}$ $\left\{ \begin{array}{l} I_1 = I_2 \\ A_1 = A_2 \end{array} \right.$


c. Compare the strengths of the electric fields E_1 and E_2 in the two segments.

$J = \sigma E$ $\therefore E = \frac{J}{\sigma}$ $\therefore \frac{E_1}{E_2} = \frac{\sigma_2}{\sigma_1}$

since $\sigma_2 > \sigma_1$, $E_1 > E_2$

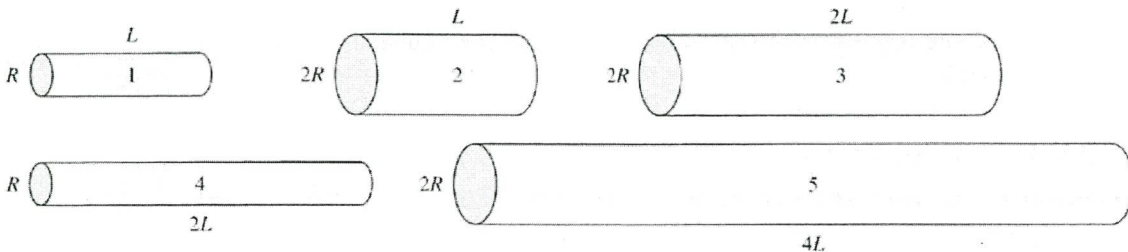7.

The wires below are all made of the same material. Rank in order, from largest to smallest, the resistances R_1 to R_5 of these wires.



Order:

Explanation:


~~$R = \rho \frac{L}{A} = \rho \frac{L}{\pi r^2}$~~ $R = \rho \frac{l}{A} = \rho \frac{l}{\pi r^2} \approx R \propto \frac{l}{r^2}$

$R_1 = \frac{L}{R^2}$ $R_2 = \frac{L}{4R^2}$ $R_3 = \frac{L}{2R^2}$ $R_4 = \frac{2L}{R^2}$ $R_5 = \frac{L}{R^2}$

$R_4 > R_1 = R_5 > R_3 > R_2$

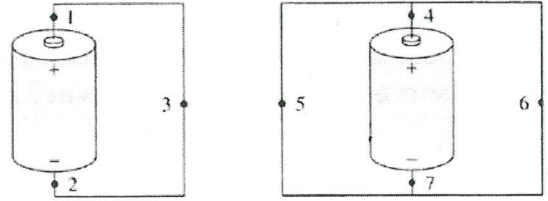8.

The two circuits use identical batteries and wires of equal diameters. Rank in order, from largest to smallest, the currents I_1 to I_7 at points 1 to 7.



Order: $I_1 = I_2 = I_3$ (series)

Explanation: $I_4 = I_7$ (series)

wires 5 & 6 have same geometry $\therefore R_5 = R_6 \Rightarrow I_5 = I_6$

if wire 3 has resistance R , wires 5 & 6 also have resistance R

$\therefore I_3 = I_5 = I_6$ (same ΔV , same R)

$I_4 = I_5 + I_6$ (junct. rule) $\therefore I_4 > I_5, I_6$

$\therefore I_4 = I_7 > I_1 = I_2 = I_3 = I_5 = I_6$

9.

For resistors R_1 to R_2 .

a. Which end (left, right, top, or bottom) is more positive?


R_1 : right R_2 : top

b. In which direction (such as left to right or top to bottom) does the potential decrease?

R_1 : right to left

R_2 : top to btm.

\vec{E} points from high to low pot.

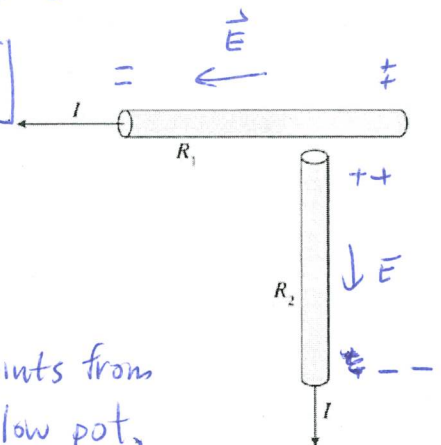

10.

Wire 1 and wire 2 are made from the same metal. Wire 1 has twice the diameter and half the electric field of wire 2. What is the ratio I_1/I_2 ?

$I = JA = \sigma EA$ $\sigma_1 = \sigma_2$ (same material)

$\therefore \frac{I_1}{I_2} = \frac{E_1 A_1}{E_2 A_2} = \frac{E_1}{E_2} \left(\frac{d_1}{d_2}\right)^2$ $A \propto d^2$

$= \frac{1}{2} (2)^2 = 2$

$\therefore I_1 = 2I_2$