

(2pts) 1.

The two circuits use identical batteries and wires of equal diameters. Rank in order, from largest to smallest, the currents I_1 , I_2 , I_3 , and I_4 at points 1 to 4.

Order:

