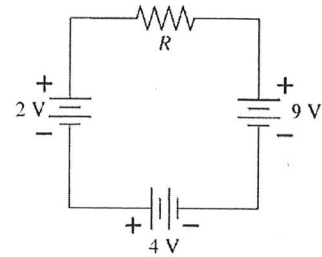



1.

a. In which direction does current flow through resistor R ?


I goes ccw (from right to left through R)



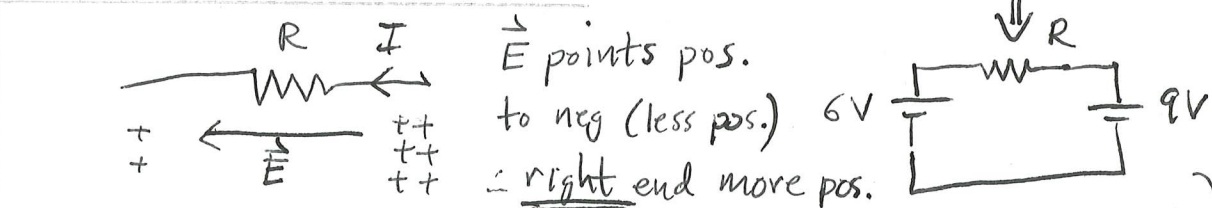
b. Which end of R is more positive? Explain.



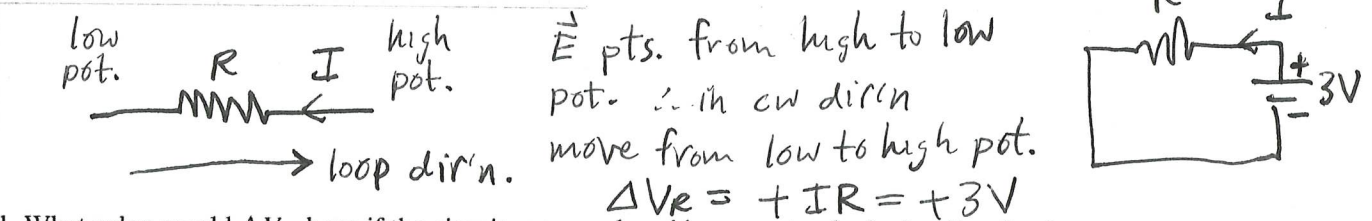c. If this circuit were analyzed in a clockwise direction, what numerical value would you assign to ΔV_{res} ? Why?




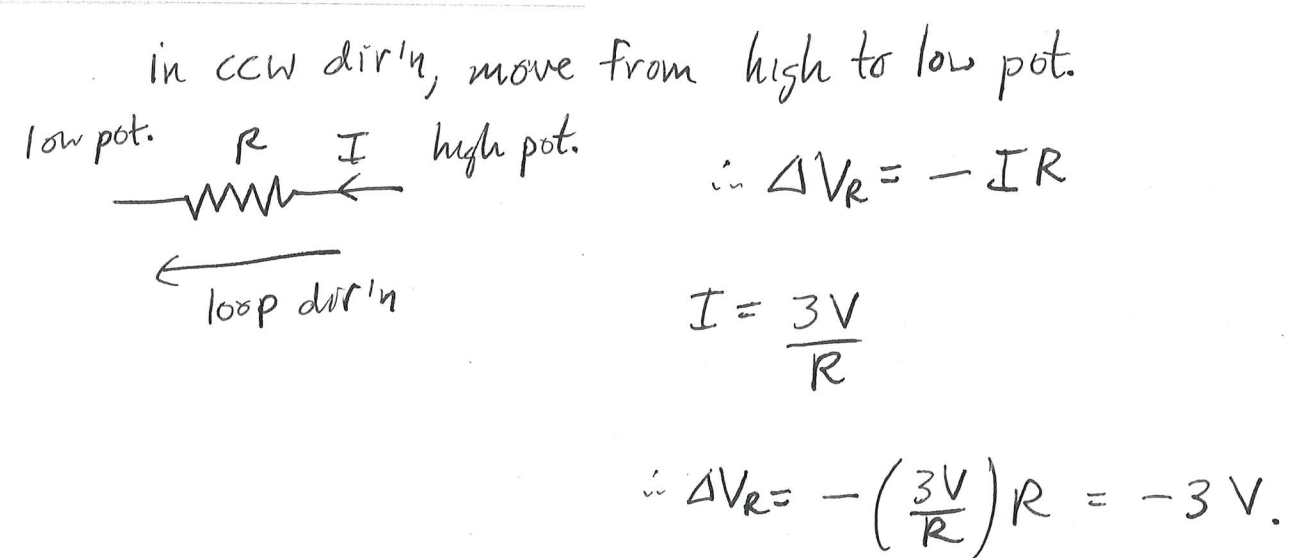d. What value would ΔV_{res} have if the circuit were analyzed in a counterclockwise direction?



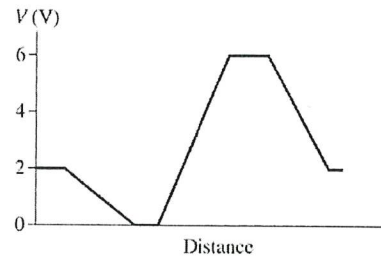
2.

The current in a circuit is 2.0 A. The graph shows how the potential changes when going around the circuit in a clockwise direction, starting from the lower left corner. Draw the circuit diagram.




$$\sum \Delta V_i = -2V + 6V - 4V = 0$$

one possible circuit:

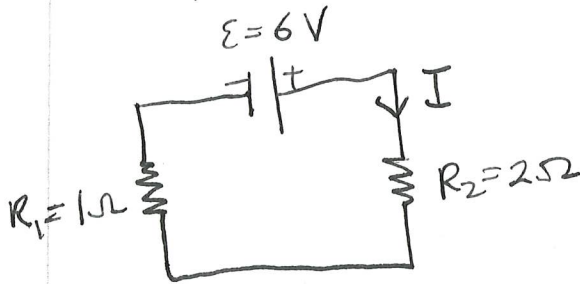

another possibility

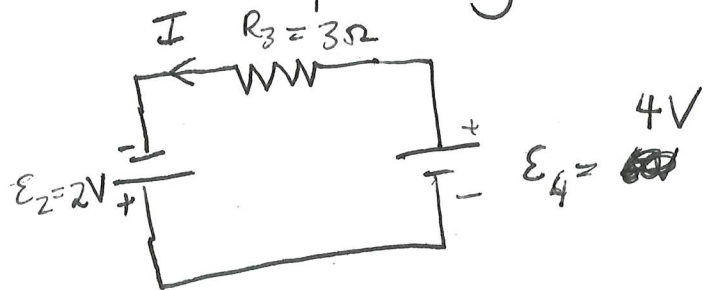


3.

This circuit has two resistors, with $R_1 > R_2$. Which of the two resistors dissipates the larger amount of power? Explain.

$$I_1 = I_2 = I$$


$$P_1 = I^2 R_1 \quad P_2 = I^2 R_2$$

$$R_1 > R_2 \implies P_1 > P_2$$

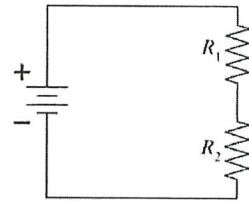


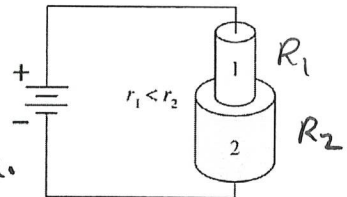4.

Two conductors of equal lengths are connected to a battery by ideal wires. The conductors are made of the same material but have different radii r . Which of the two conductors dissipates the larger amount of power? Explain.



Equiv. circuit is:

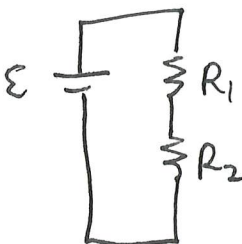

Just like previous problem.


Larger resistor dissipates more power

$$R = \frac{l}{\sigma} \frac{l}{A} \quad A_1 < A_2 \implies R_1 > R_2$$

$\implies R_1$ (wire 1) dissipates more power.

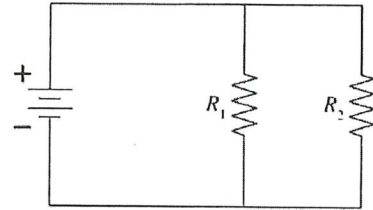5.

The circuit shown has a battery and two resistors, with $R_1 > R_2$. Which of the two resistors dissipates the larger amount of power? Explain your reasoning.



For parallel combo $\Delta V_1 = \Delta V_2 \equiv \Delta V$


$$P_1 = \frac{(\Delta V_1)^2}{R_1} = \frac{(\Delta V)^2}{R_1} \quad P_2 = \frac{(\Delta V)^2}{R_2}$$

$R_1 > R_2 \Rightarrow P_2 > P_1$ R_2 dissipates more power.

6.

The figure shows two circuits. The two ideal batteries are identical and the four resistors all have exactly the same resistance.

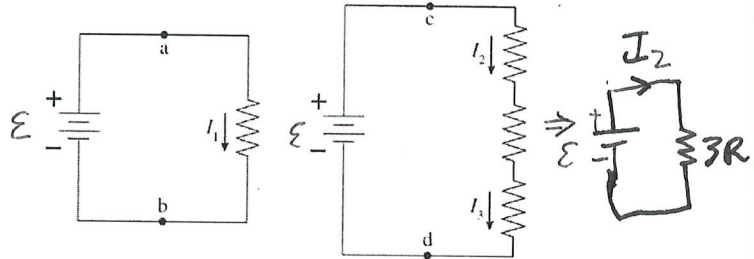a. Is ΔV_{ab} larger than, smaller than, or equal to ΔV_{cd} ? Explain.



$$\Delta V_{ab} = \Delta V_{cd}$$

both across same battery. $\therefore \Delta V_{ab} = \Delta V_{cd} = \epsilon$.

b. Rank in order, from largest to smallest, the currents I_1 , I_2 , and I_3 .

Order:

Explanation:

I_2 in series w/ $I_3 \Rightarrow I_2 = I_3$


$$I_1 = \frac{\epsilon}{R} \quad I_2 = I_3 = \frac{\epsilon}{3R} \quad \therefore I_1 > I_2, I_3$$

$$I_1 > I_2 = I_3$$

7.

What is the equivalent resistance of each group of resistors?

a.

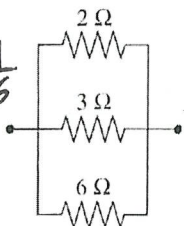


$$R_{eq} = 1\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = \frac{6}{6}$$

$$\therefore R_{eq} = 1\Omega$$

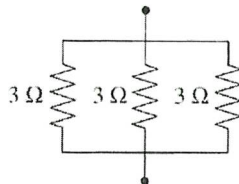
b. $\frac{1}{R_{eq}} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} = \frac{3}{3}$



$$R_{eq} = 1\Omega$$

$$\therefore R_{eq} = 1\Omega$$

c.

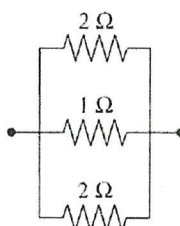

$$R_{eq} = 0.5\Omega$$


$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{1} + \frac{1}{2} = 2$$

$$\therefore R_{eq} = 0.5\Omega$$

8.


a. What fraction of current I goes through the $3\ \Omega$ resistor?

$$\begin{aligned} \Delta V_3 &= \Delta V_9 \\ I_3 R_3 &= I_9 R_9 \\ \therefore I_3 &= I_9 \frac{R_9}{R_3} = 3 I_9 \end{aligned} \quad \left| \begin{aligned} I &= I_3 + I_9 = 4 I_9 \\ \therefore I_9 &= \frac{I}{4} \\ I_3 &= \frac{3}{4} I \end{aligned} \right.$$

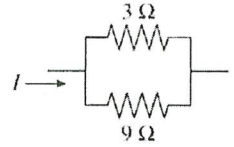

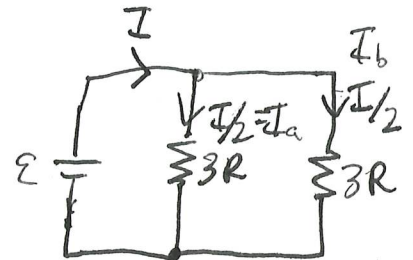b. If the $9\ \Omega$ resistor is replaced with a larger resistor, will the fraction of current going through the $3\ \Omega$ resistor increase, decrease, or stay the same?


increase. More of the current
~~it~~ takes the "low resistance" path.



9.

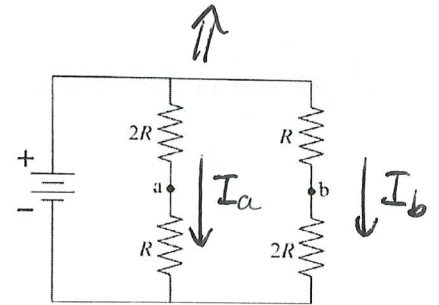
a. Consider the points a and b. Is the potential difference $\Delta V_{ab} = 0$? If so, why? If not, which point is more positive?

$$\begin{aligned} \Delta V_{ab} &\neq 0. \quad I_a = I_b = I/2 \\ &\text{Track changes in volt. from pt. a to b.} \\ &V_a - I_a R + I_b 2R = V_b \\ \therefore V_b - V_a = \Delta V_{ab} &= -\frac{I}{2}R + \frac{I}{2}2R = +\frac{IR}{2} \quad \therefore V_b > V_a \end{aligned}$$



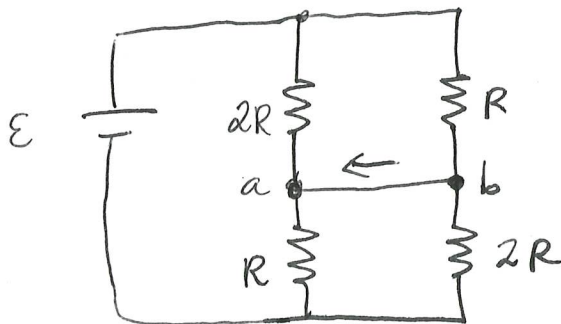b. If a wire is connected between points a and b, does a current flow through it? If so, in which direction—to the right or to the left? Explain.


Yes, current flows from $b \rightarrow a$.



b was at a higher pot.
 than a .
 current flows from high
 to low pot.

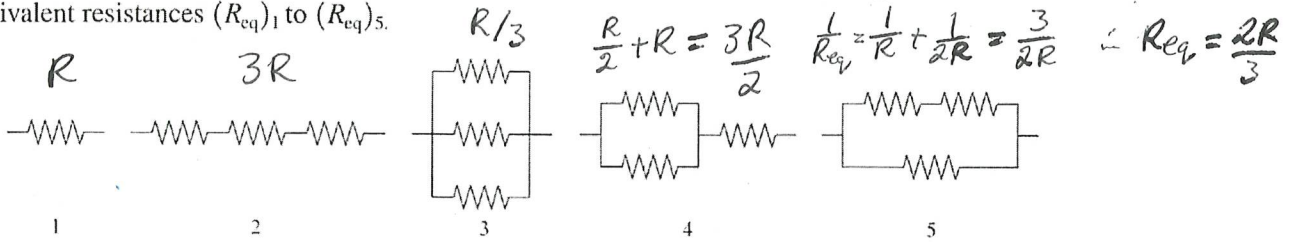10.

The figure shows five combinations of identical resistors. Rank in order, from largest to smallest, the equivalent resistances $(R_{eq})_1$ to $(R_{eq})_5$.



Order:

Explanation: 2, 4, 1, 5, 3


11.

Bulbs A and B are identical. Initially both are glowing.

a. Bulb A is removed from its socket. What happens to bulb B? Does it get brighter, stay the same, get dimmer, or go out? Explain.

B goes out. When A is removed it causes an open circuit.

$$\therefore I \rightarrow 0$$

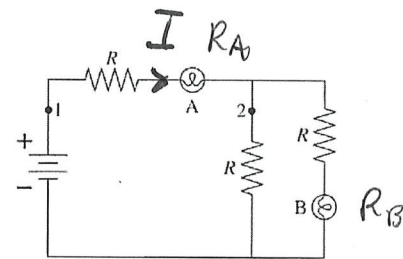

b. Bulb A is replaced. Bulb B is then removed from its socket. What happens to bulb A? Does it get brighter, stay the same, get dimmer, or go out? Explain.

A gets dimmer. When B is in place, have R in parallel with $R + R_B$ which makes a smaller R_{eq} . When B is removed $R_{eq} \rightarrow R$ \therefore current decreases.

c. The circuit is restored to its initial condition. A wire is then connected between points 1 and 2. What happens to the brightness of each bulb?

A goes out.

B gets brighter.

A wire between 1 & 2 short circuits $R + R_A$. \therefore no current through R_A .

Current through R_B increase b/c now don't have series resistance $R + R_A$.