

Conceptual Question 25.01

Part A

If the electric field is zero everywhere inside a region of space, the potential must also be zero in that region.

ANSWER:


- True
 False

Since $E_s = -\frac{dV}{ds}$, if $E=0$ then $\frac{dV}{ds} = 0$
or $V = \text{const.}$

Conceptual Question 25.06

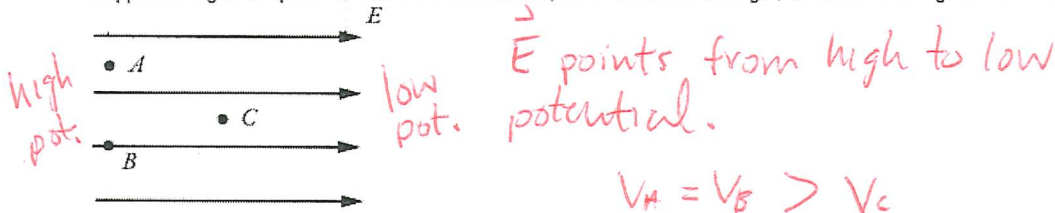Part A

Suppose a region of space has a uniform electric field, directed towards the right, as shown in the figure. Which statement about the electric potential is true?



ANSWER:

- The potential at points A and B are equal, and the potential at point C is higher than the potential at point A .
- The potential at all three locations (A , B , C) is the same because the field is uniform.
- The potential at point A is the highest, the potential at point B is the second highest, and the potential at point C is the lowest.
- The potential at points A and B are equal, and the potential at point C is lower than the potential at point A .

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

For series caps
 $Q_1 = Q_2$.


Conceptual Question 26.11

Part A

When two or more capacitors are connected in series across a potential difference

ANSWER:

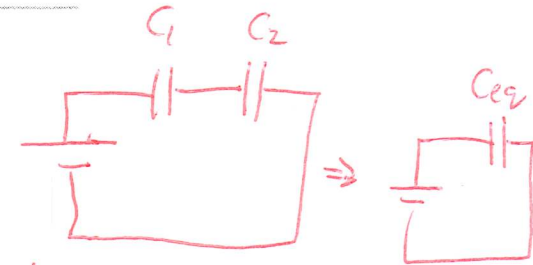- the potential difference across the combination is the algebraic sum of the potential differences across the individual capacitors.
- the equivalent capacitance of the combination is less than the capacitance of any of the capacitors.
- each capacitor carries the same amount of charge.
- All of the above choices are correct.
- None of the above choices are correct.




by loop rule $V_{C1} + V_{C2} = V_{Ceq}$

Problem 26.09

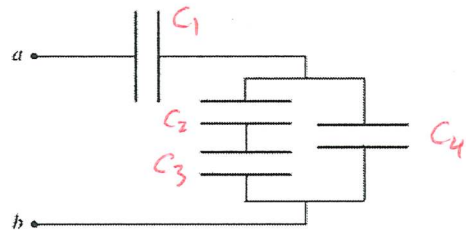Part A


The capacitors in the network shown in the figure all have a capacitance of $5.0 \mu\text{F}$. What is the equivalent capacitance, C_{ab} , of this capacitor network?



ANSWER:


- $20 \mu\text{F}$
- $1.0 \mu\text{F}$
- $3.0 \mu\text{F}$
- $5.0 \mu\text{F}$
- $10 \mu\text{F}$
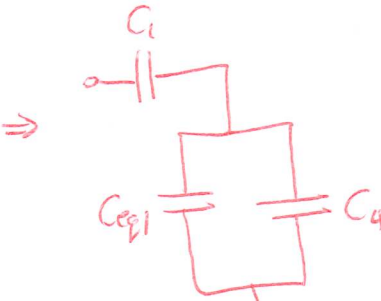
$$\frac{3C}{5} = \frac{3(5\mu\text{F})}{5} = 3\mu\text{F}$$




$$\frac{1}{C_{eq1}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{C} + \frac{1}{C} = \frac{2}{C}$$

$$\therefore C_{eq1} = \frac{C}{2}$$

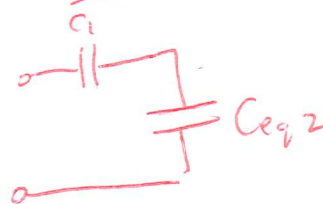
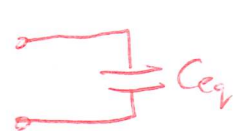
$$C_{eq2} = C_{eq1} + C_4 = \frac{C}{2} + C = \frac{3C}{2}$$




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{eq2}} = \frac{1}{C} + \frac{2}{3C} = \frac{5}{3C}$$

$$C_{eq} = \frac{3C}{5}$$

Conceptual Question 27.01

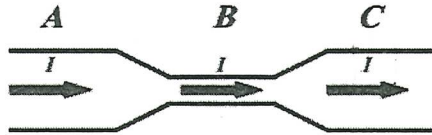Part A

The figure shows a steady electric current passing through a wire with a narrow region. What happens to the drift velocity of the moving charges as they go from region *A* to region *B* and then to region *C*?



ANSWER:

- The drift velocity remains constant.
- The drift velocity increases from A to B and decreases from B to C.
- The drift velocity increases all the time.
- The drift velocity decreases from A to B and increases from B to C.
- The drift velocity decreases all the time.

$$J = \frac{I}{A} = qnV_d$$

$$I_A = I_B = I_C$$

$$J_A = J_C < J_B$$

$$\therefore V_{dA} = V_{dC} < V_{dB}$$

Problem 27.20

Part A

A 2.0 mm diameter wire of length 20 m has a resistance of 0.25 Ω . What is the resistivity of the wire?

ANSWER:


- 0.25 $\Omega \cdot m$
- $4.0 \times 10^{-7} \Omega \cdot m$
- $3.9 \times 10^{-8} \Omega \cdot m$
- $16 \times 10^{-3} \Omega \cdot m$
- $5.0 \times 10^{-7} \Omega \cdot m$

$$R = \rho \frac{L}{A} \quad \therefore \rho = \frac{A}{L} R = \frac{\pi \left(\frac{d}{2}\right)^2}{L} R = 3.93 \times 10^{-8} \Omega m$$

Conceptual Question 28.03

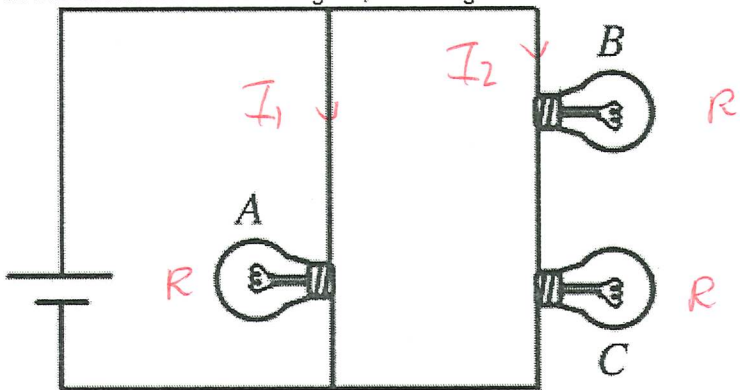Part A

In the circuit shown in the figure, all the lightbulbs are identical. Which of the following is the correct ranking of the brightness of the bulbs?



Greatest current through A

A brightest

B & C equally bright



ANSWER:

- A is brightest, C is dimmest, and B is in between.
- A and B have equal brightness, and C is the dimmest.
- A is the brightest, and B and C have equal brightness but less than A.
- B and C have equal brightness, and A is the dimmest.
- All three bulbs have the same brightness.

Problem 28.24

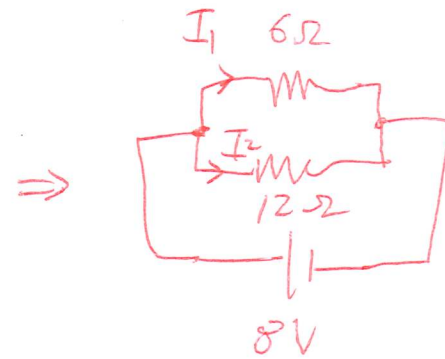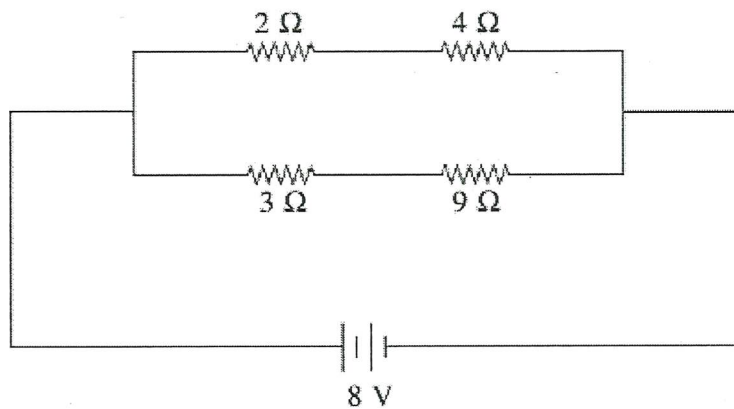Part A

Four resistors are connected across an 8-V DC battery as shown in the figure. The current through the 9- Ω resistor is closest to



by loop rule $8V - 12I_2 = 0$

$$\therefore I_2 = \frac{8V}{12\Omega} = 0.67A$$

current through 3 Ω & 9 Ω resistors is 0.67A.


ANSWER:

- 0.5 A.
- 2 A.
- 0.7 A.
- 1 A.
- 0.9 A.

Problem 28.27

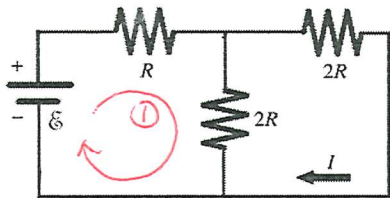
Part A

For the circuit shown in the figure, $I = 0.50 \text{ A}$ and $R = 12 \Omega$. What is the value of the emf \mathcal{E} ?



ANSWER:

- 48 V
- 12 V
- 6.0 V
- 18 V
- 24 V

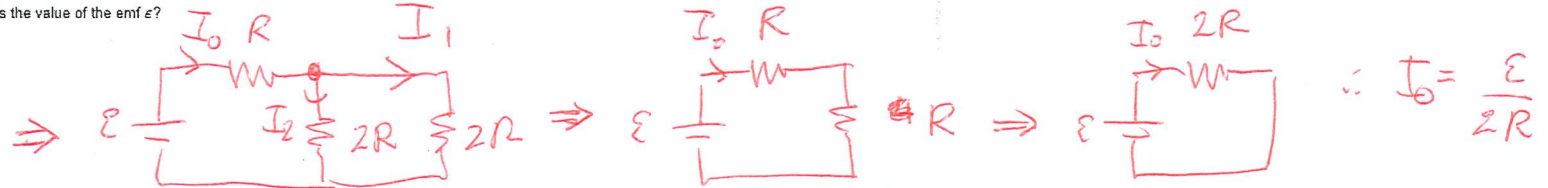

by symmetry $I_1 = I_2 \equiv I$

by junction rule $I_0 = I_1 + I_2 = 2I$

$$\mathcal{E} = 4IR = 4(0.50 \text{ A})(12 \Omega) = 24 \text{ V}$$

$$\therefore I = \frac{I_0}{2} = \frac{\mathcal{E}}{4R}$$

By loop rule ① (check)

$$\mathcal{E} - I_0 R - I(2R) = 0$$

$$\mathcal{E} - \frac{\mathcal{E}}{2} - \frac{\mathcal{E}}{2} = 0 \quad \checkmark$$

Conceptual Question 26.16

Part A

An ideal parallel-plate capacitor consists of a set of two parallel plates of area A separated by a very small distance d . When the capacitor plates carry charges $+Q$ and $-Q$, the capacitor stores energy U_0 . If the separation between the plates is doubled, how much electrical energy is stored in the capacitor?

ANSWER:

- U_0
- $2U_0$
- $U_0/2$
- $U_0/4$
- $4U_0$

$$U_0 = \frac{Q^2}{2C}$$

$$C = \epsilon_0 \frac{A}{d}$$

$$U_0 = \frac{Q^2 d}{2\epsilon_0 A}$$

$$U_1 = \frac{Q^2 (2d)}{2\epsilon_0 A}$$

$$\therefore \frac{U_1}{U_0} = 2$$

$$\Rightarrow U_1 = 2U_0$$