

### Conceptual Question 25.01

#### Part A

If the electric field is zero everywhere inside a region of space, the potential must also be zero in that region.


ANSWER:

- True
- False

### Conceptual Question 25.06
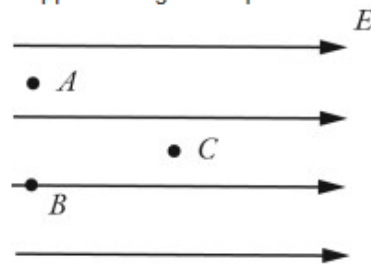
#### Part A

Suppose a region of space has a uniform electric field, directed towards the right, as shown in the figure. Which statement about the electric potential is true?



ANSWER:

- The potential at points  $A$  and  $B$  are equal, and the potential at point  $C$  is higher than the potential at point  $A$ .
- The potential at all three locations ( $A$ ,  $B$ ,  $C$ ) is the same because the field is uniform.
- The potential at point  $A$  is the highest, the potential at point  $B$  is the second highest, and the potential at point  $C$  is the lowest.
- The potential at points  $A$  and  $B$  are equal, and the potential at point  $C$  is lower than the potential at point  $A$ .

## Conceptual Question 26.11

### Part A

When two or more capacitors are connected in series across a potential difference


ANSWER:

- the potential difference across the combination is the algebraic sum of the potential differences across the individual capacitors.
- the equivalent capacitance of the combination is less than the capacitance of any of the capacitors.
- each capacitor carries the same amount of charge.
- All of the above choices are correct.
- None of the above choices are correct.

## Problem 26.09
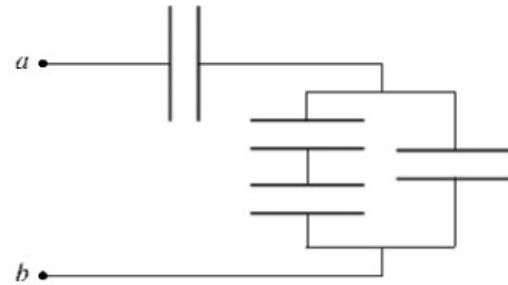
### Part A

The capacitors in the network shown in the figure all have a capacitance of  $5.0 \mu\text{F}$ . What is the equivalent capacitance,  $C_{ab}$ , of this capacitor network?




ANSWER:

- $20 \mu\text{F}$
- $1.0 \mu\text{F}$
- $3.0 \mu\text{F}$
- $5.0 \mu\text{F}$
- $10 \mu\text{F}$

## Conceptual Question 27.01
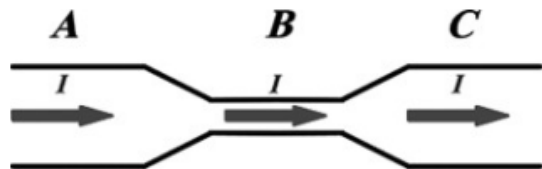
### Part A

The figure shows a steady electric current passing through a wire with a narrow region. What happens to the drift velocity of the moving charges as they go from region *A* to region *B* and then to region *C*?



ANSWER:

- The drift velocity remains constant.
- The drift velocity increases from A to B and decreases from B to C.
- The drift velocity increases all the time.
- The drift velocity decreases from A to B and increases from B to C.
- The drift velocity decreases all the time.

## Problem 27.20

### Part A

A 2.0 mm diameter wire of length 20 m has a resistance of  $0.25 \Omega$ . What is the resistivity of the wire?


ANSWER:

- $0.25 \Omega \cdot \text{m}$
- $4.0 \times 10^{-7} \Omega \cdot \text{m}$
- $3.9 \times 10^{-8} \Omega \cdot \text{m}$
- $16 \times 10^{-8} \Omega \cdot \text{m}$
- $5.0 \times 10^{-7} \Omega \cdot \text{m}$

## Conceptual Question 28.03
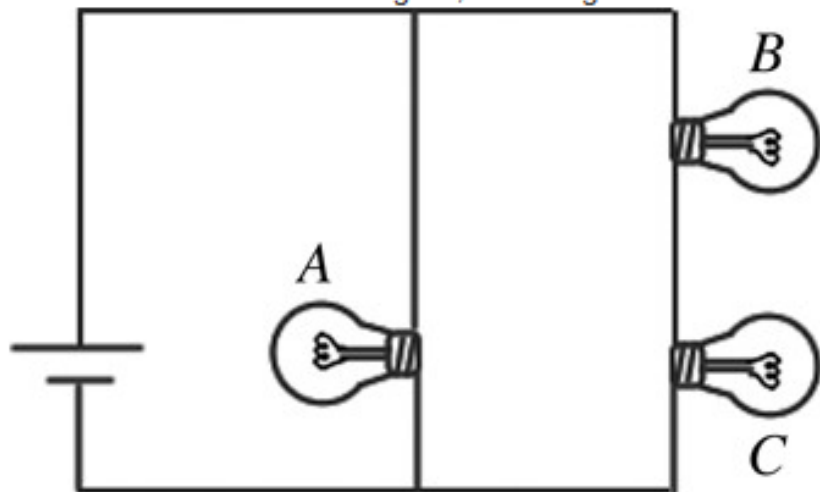
### Part A

In the circuit shown in the figure, all the lightbulbs are identical. Which of the following is the correct ranking of the brightness of the bulbs?




ANSWER:

- A* is brightest, *C* is dimmest, and *B* is in between.
- A* and *B* have equal brightness, and *C* is the dimmest.
- A* is the brightest, and *B* and *C* have equal brightness but less than *A*.
- B* and *C* have equal brightness, and *A* is the dimmest.
- All three bulbs have the same brightness.

## Problem 28.24
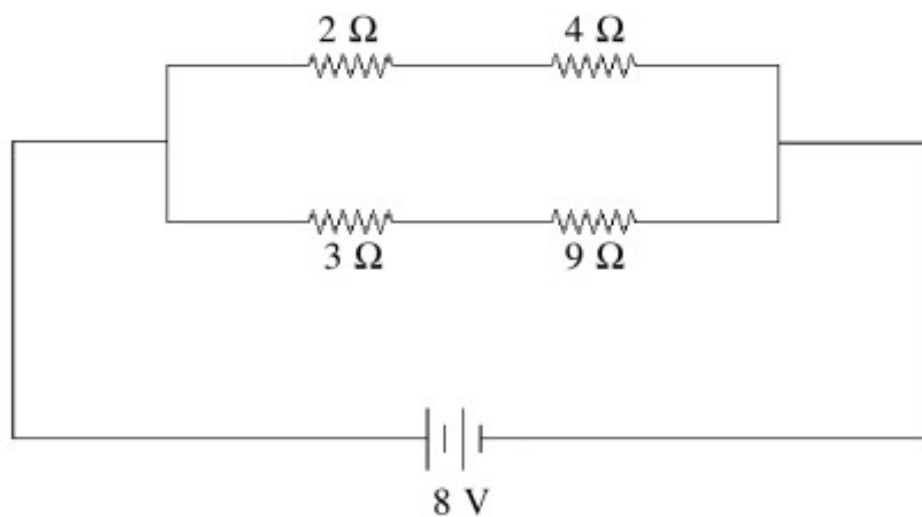
### Part A

Four resistors are connected across an 8-V DC battery as shown in the figure. The current through the 9- $\Omega$  resistor is closest to




ANSWER:

- 0.5 A.
- 2 A.
- 0.7 A.
- 1 A.
- 0.9 A.

Problem 28.27

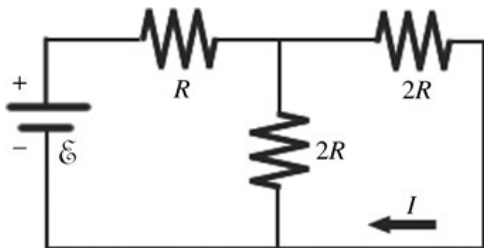Part A

For the circuit shown in the figure,  $I = 0.50 \text{ A}$  and  $R = 12 \Omega$ . What is the value of the emf  $\mathcal{E}$ ?



ANSWER:

- 48 V
- 12 V
- 6.0 V
- 18 V
- 24 V

Conceptual Question 26.16

Part A

An ideal parallel-plate capacitor consists of a set of two parallel plates of area  $A$  separated by a very small distance  $d$ . When the capacitor plates carry charges  $+Q$  and  $-Q$ , the capacitor stores energy  $U_0$ . If the separation between the plates is doubled, how much electrical energy is stored in the capacitor?

ANSWER:

- $U_0$
- $2U_0$
- $U_0/2$
- $U_0/4$
- $4U_0$