
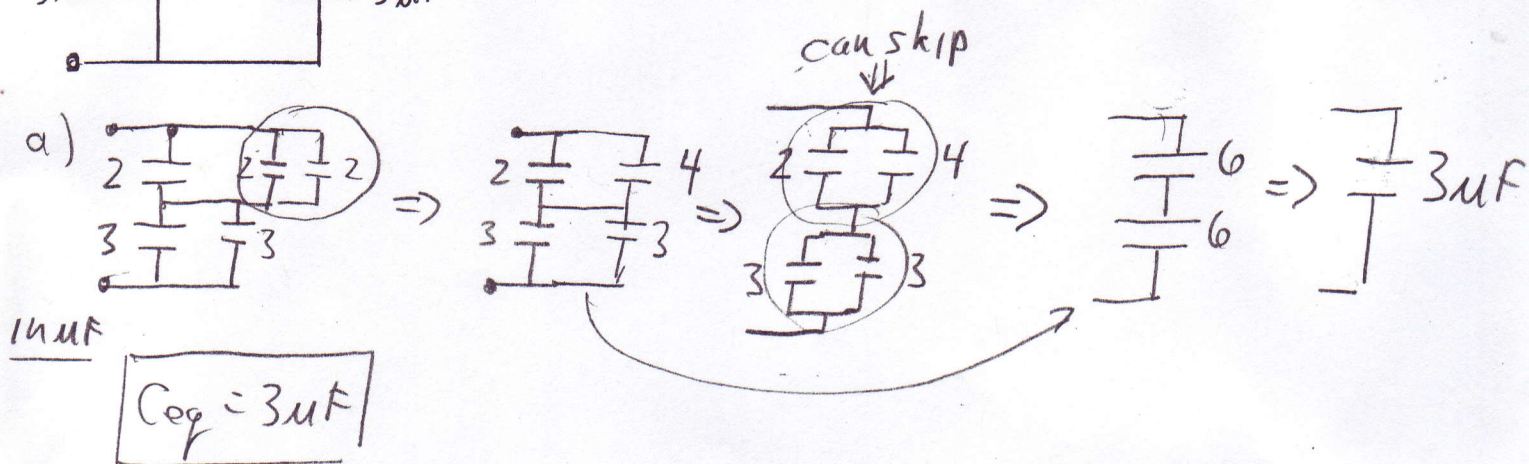
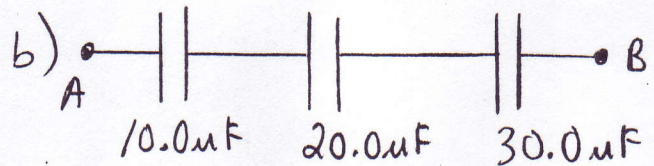


2a) Find the equivalent capacitance of the system of capacitors shown below in figure (a). (4)

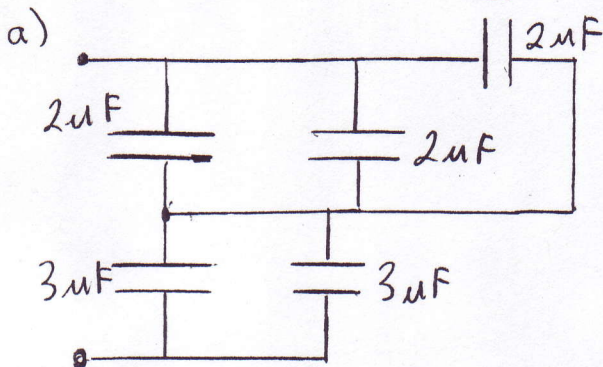b) Consider the capacitors shown in figure (b) below. If none of the capacitors can withstand a potential difference of more than 100 V without failure, what is the maximum potential difference that can be applied across points A and B without inducing a failure? (4 marks)



b)

$$\frac{1}{C_{eq}} = \frac{1}{10.0} + \frac{1}{20.0} + \frac{1}{30.0} \Rightarrow C_{eq} = 5.45 \mu F$$

$$Q = C \Delta V = (5.45 \times 10^{-6}) V_{applied} \Rightarrow Q = 5.45 \times 10^{-6} V_{applied}$$

Since the capacitors are in series each capacitor has the charge. From $\Delta V = Q/C$ the 10.0 μF capacitor will have the highest voltage.

$$100 = \frac{5.45 \times 10^{-6} V_{applied}}{10^{-5}} \Rightarrow V_{applied} = 184 V$$