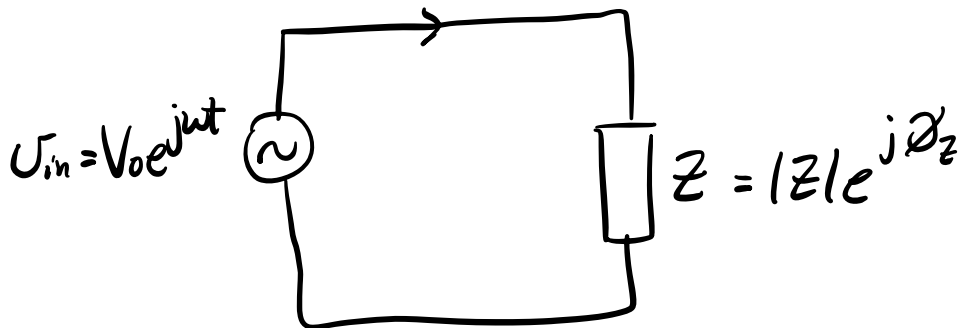


PHYS 231 - Oct. 25, 2023

Last Time: For any circuit of the form:

$$i = I_0 e^{j(\omega t + \phi)}$$




$$I_0 = \frac{V_0}{|Z|} \quad \phi = -\phi_Z = -\tan^{-1} \left(\frac{\text{Im}[Z]}{\text{Re}[Z]} \right)$$

For a capacitor $Z_C = \frac{1}{j\omega C}$

For an inductor $Z_L = j\omega L$

Series LRC circuit

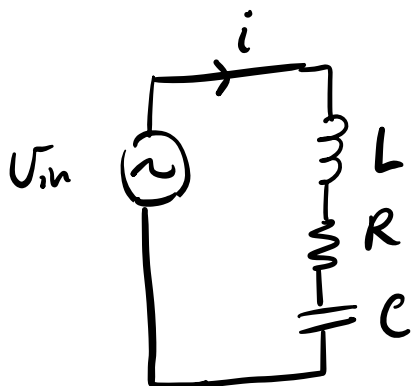

$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \quad \tan \phi_Z = \frac{\omega L}{R} - \frac{1}{\omega RC}$$

$$\Rightarrow I_0 = \frac{V_0 / R}{\sqrt{1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2}}$$

$$\phi = \tan^{-1} \left(\frac{1}{\omega RC} - \omega \frac{L}{R} \right)$$

In Exp. #4 day 2, you will meas. the volt. across the resistor as a fun of the signal generator freq. f ($\omega = 2\pi f$).

$$V_R = iR$$

Amplitude of V_R is just $V_R = I_0 R$

$$V_R = \frac{V_0}{\sqrt{1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2}}$$

the phase of the resistor voltage is the

same as the current phase

$$\phi = \tan^{-1} \left(\frac{1}{\omega RC} - \omega \frac{L}{R} \right)$$

In Exp #4 day 2, you will complete an analysis of

$$\frac{V_R}{V_0} \text{ vs } \omega$$

in the provided Jupyter notebook.

Expect $\frac{V_R}{V_0} = \frac{1}{\sqrt{1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC} \right)^2}}$

$$\phi = \tan^{-1} \left(\frac{1}{\omega RC} - \omega \frac{L}{R} \right)$$

Check limiting behaviours...

1. $\omega \rightarrow 0$ (small)

$$\omega \frac{L}{R} - \frac{1}{\omega RC} \approx -\frac{1}{\omega RC}$$

$$1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC} \right)^2 \approx \left(\frac{1}{\omega RC} \right)^2$$

$$\frac{V_R}{V_0} \approx \frac{1}{\frac{1}{\omega RC}} \approx \omega RC \rightarrow \text{linear}$$

$$\phi \approx \tan^{-1}\left(\frac{1}{\omega RC}\right) \rightarrow \tan^{-1}(\infty)$$



$\therefore \phi \rightarrow +\frac{\pi}{2}$ at low freq.

2. $\omega \rightarrow \infty$ (large) $\frac{\omega L}{R} - \frac{1}{\omega RC} \approx \frac{\omega L}{R}$

$$1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2 \approx \left(\frac{\omega L}{R}\right)^2$$

$$\frac{V_R}{V_0} \approx \frac{1}{\frac{\omega L}{R}} = \frac{1}{\omega} \frac{R}{L} \propto \frac{1}{\omega}$$
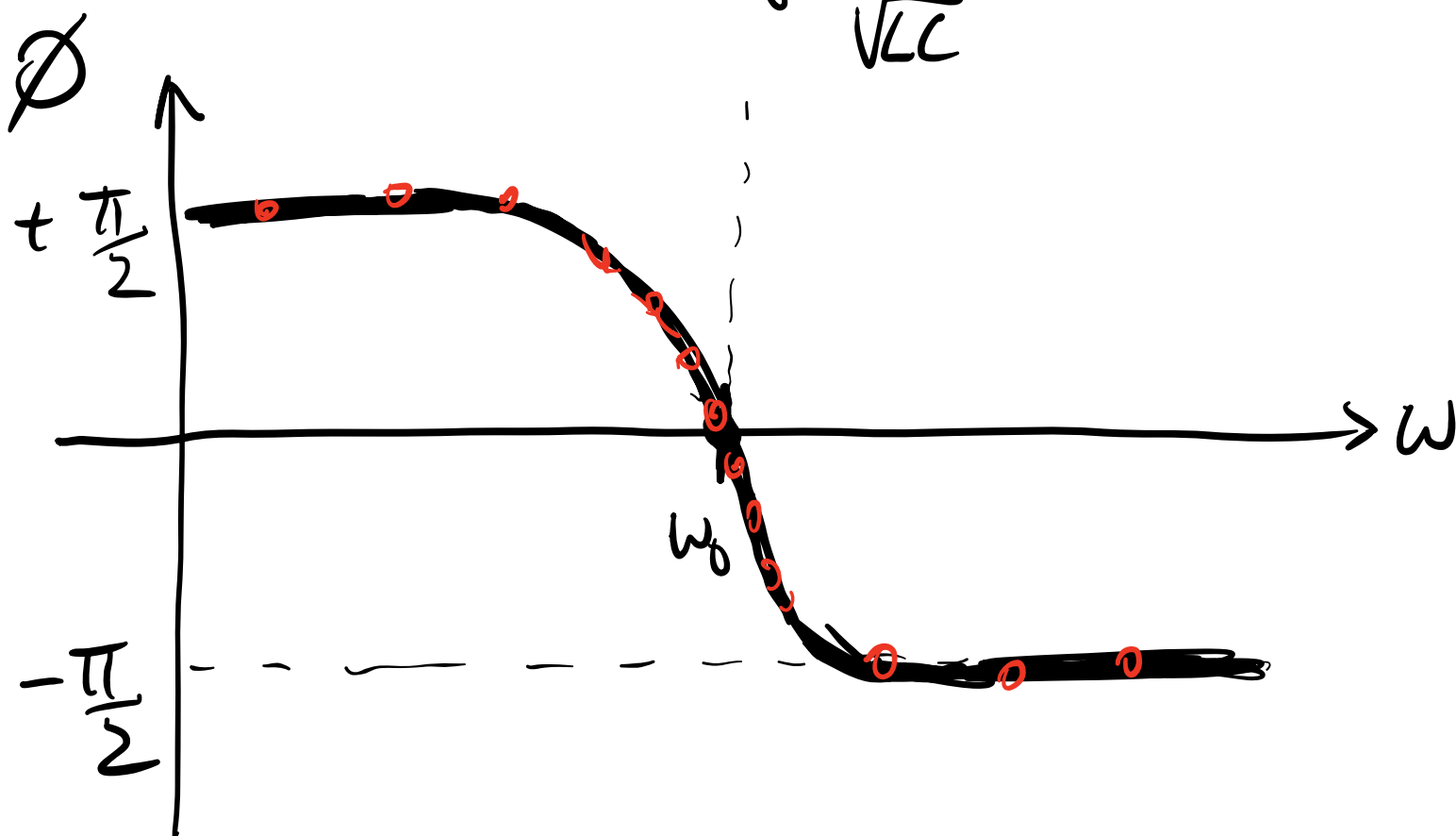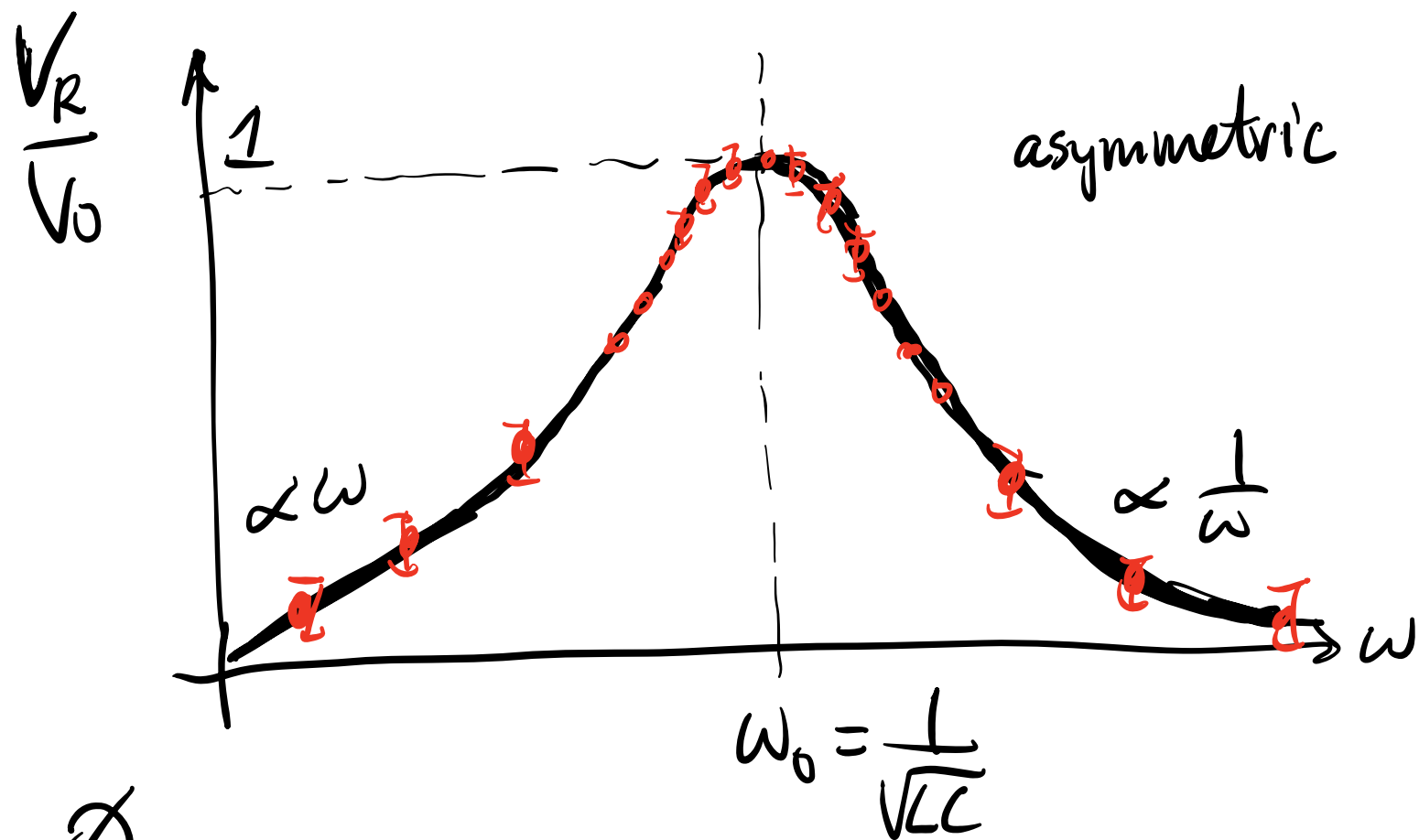
$$\phi \approx \tan^{-1}\left(-\omega \frac{L}{R}\right) \rightarrow -\frac{\pi}{2} \text{ at high freq.}$$



Resonance Frequency.

$$\frac{V_R}{V_0} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}} \quad \text{is a}$$

maximum when $\omega = \omega_0$ s.t.

$$\omega_0 \frac{L}{R} - \frac{1}{\omega_0 RC} = 0$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \Rightarrow$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{When } \omega = \omega_0, \quad \frac{V_R}{V_0} = 1$$

Phase at $\omega = \omega_0$:

$$\phi = \tan^{-1} \left(\frac{L}{\omega_0 RC} - \frac{\omega_0 L}{R} \right)$$

$$= \tan^{-1} \left[\frac{L}{R} \left(\frac{1}{\omega_0 C} - \omega_0 L \right) \right]$$

$$\frac{1}{\frac{C}{\sqrt{L}}} - \frac{1}{\sqrt{LC}} L$$


$$= \frac{1}{\sqrt{\frac{C}{L}}} - \sqrt{\frac{L}{C}}$$

$$= \sqrt{\frac{L}{C}} - \sqrt{\frac{L}{C}} = 0$$

$$\therefore \phi = \tan^{-1}(0) = 0$$

At resonance ($\omega = \omega_0$), the resistor voltage V_R is in phase ($\phi = 0$) with the output of the signal generator.

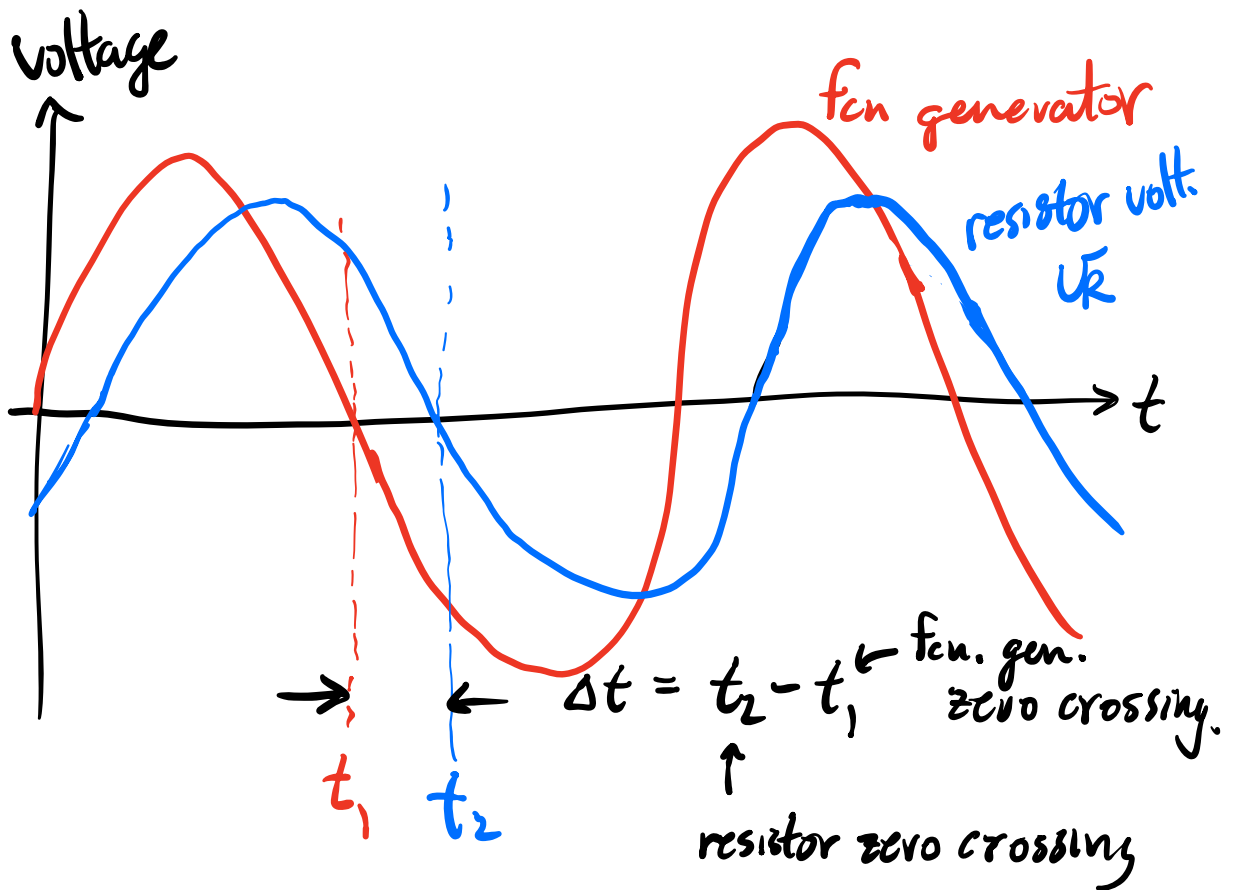Measuring Phase differences using the oscilloscope.



Convert Δt to a phase difference ϕ

$$\frac{\phi}{\Delta t} = -\frac{\pi}{T/2}$$


(half period shift in time corresponds to a phase shift of π)

$$\therefore \phi = -2\pi \frac{\Delta t}{T} = -(2\pi f) \Delta t$$

to determine ϕ , meas. Δt and the calc.

$$\phi = -2\pi f \Delta t$$

Sign of the Phase.

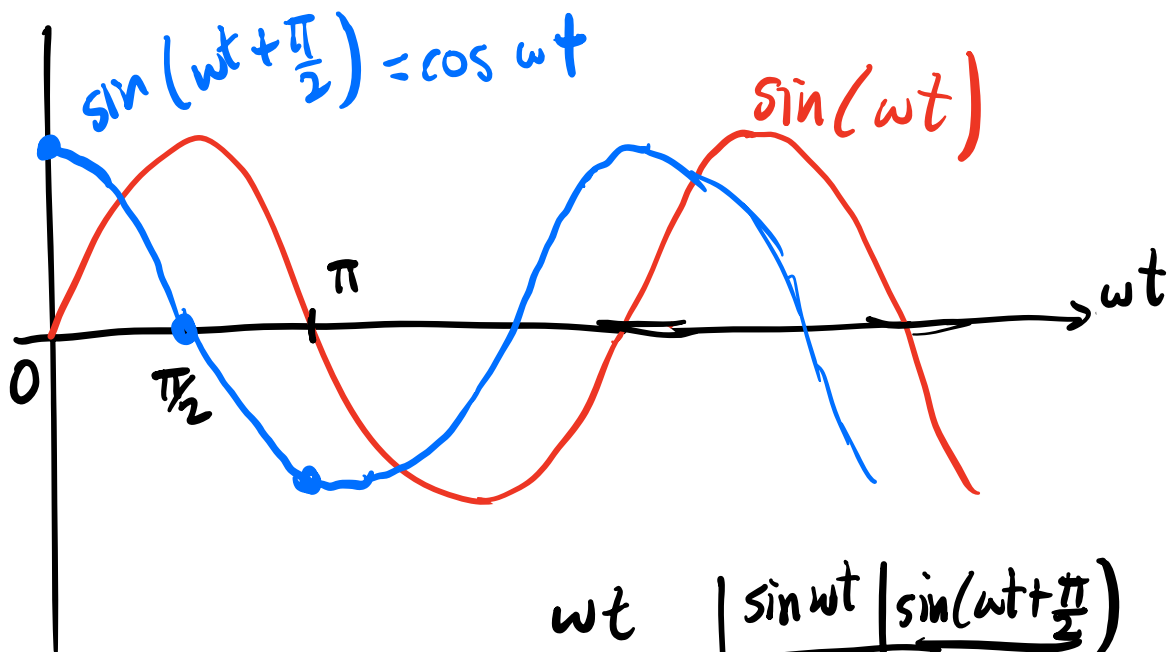

$$f = \sin\left(\omega t + \frac{\pi}{2}\right)$$

ωt	$\sin \omega t$	$\sin\left(\omega t + \frac{\pi}{2}\right)$
0	0	$\sin \frac{\pi}{2} = 1$
$\pi/2$	1	$\sin \pi = 0$
π	0	$\sin \frac{3\pi}{2} = -1$