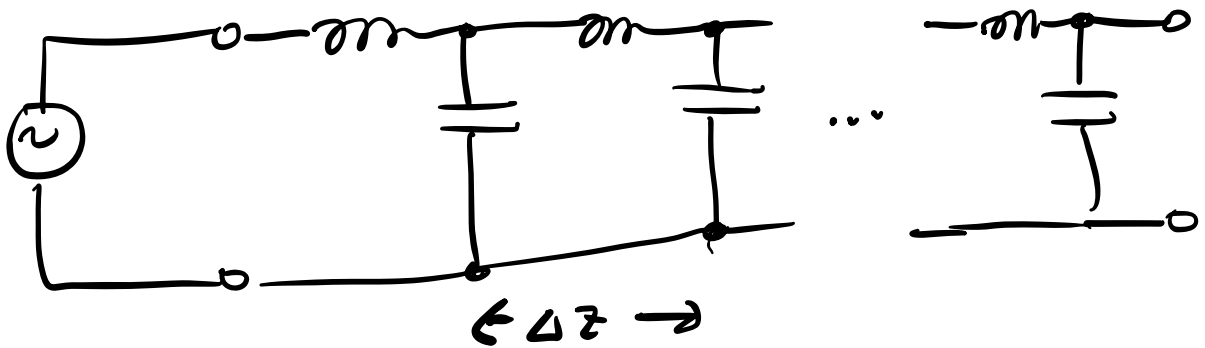


PHYS 331 - Oct. 16, 2023

Last Time



Found $V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$

$$\beta = \omega \sqrt{L_0 C_0}$$


Useful results:

$$\textcircled{\#} \quad \frac{\partial V}{\partial z} = -j\omega L_1 I$$

$$\textcircled{*} \quad \frac{\partial V}{\partial z} = -j\beta V_+ e^{-j\beta z} + j\beta V_- e^{j\beta z}$$

Full time-dep. voltage on trans. line is:
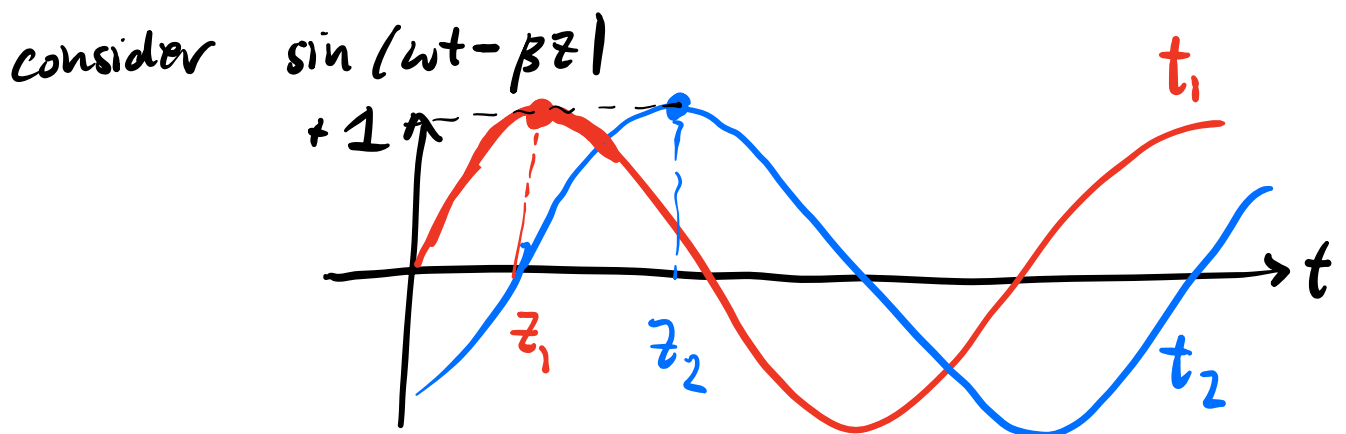
$$\begin{aligned} V(z, t) &= V(z) e^{j\omega t} \\ &= (V_+ e^{-j\beta z} + V_- e^{j\beta z}) e^{j\omega t} \\ &= V_+ e^{j(\omega t - \beta z)} + V_- e^{j(\omega t + \beta z)} \end{aligned}$$



Require $\sin(\omega t_1 - \beta z_1) = \sin(\omega t_2 - \beta z_2)$

\Downarrow

$$\omega t_1 - \beta z_1 = \omega t_2 - \beta z_2$$

$$\underbrace{\omega(t_2 - t_1)}_{\Delta t} = \beta \underbrace{(z_2 - z_1)}_{\Delta z}$$

$$\therefore \frac{\omega}{\beta} = \underbrace{\frac{\Delta z}{\Delta t}}$$

S the speed of the signal.

$$S = \frac{\omega}{\beta} \quad \text{know } \beta = \omega \sqrt{L_1 C_1}$$

$$\therefore S = \frac{\omega^1}{\omega \sqrt{L_1 C_1}}$$

$$\therefore S = \frac{1}{\sqrt{L_1 C_1}}$$

For parallel conductors of radius a ,
we had
$$L_e = \frac{\mu_0 \ln\left(\frac{d}{a}\right)}{\pi}$$

$$C_e = \frac{\pi \epsilon_0}{\ln\left(\frac{d}{a}\right)}$$

$$\therefore L_e C_e = \mu_0 \epsilon_0 = \frac{1}{c^2}$$

\therefore signal speed in transmission
line is

$$S = \frac{1}{\sqrt{L_e C_e}} = c \quad \text{the speed of light.}$$

If our parallel wires were in a
medium with relative permittivity ϵ_r
& permeability μ_r , then we would
find:

$$S = \frac{c}{\sqrt{\epsilon_r \mu_r}} = \frac{c}{n} \quad \text{where } n \text{ is the refractive index.}$$

If we analyze the $\omega t + \beta z$ term, we would find the same result w/ a negative sign. $S = -\frac{1}{\sqrt{L_0 C_0}} = -c$

$e^{j(\omega t - \beta z)}$: forward travelling wave

$e^{j(\omega t + \beta z)}$: backwards travelling wave. can only be due to reflections from the end of the trans. line.

What is the physical interpretation of β ?

$$S = \frac{\omega}{\beta} = f\lambda = \frac{(2\pi f)\lambda}{2\pi}$$

$$\therefore \frac{\omega}{\beta} = \omega \frac{\lambda}{2\pi}$$

$$\beta = \frac{2\pi}{\lambda} \quad \text{called propagation const. or wave number}$$

Return to useful results (⊗) & (⊙)

— two expressions for dV/dz which must be equal to one another.

$$-j\beta V_+ e^{-j\beta z} + j\beta V_- e^{j\beta z} = -j\omega L_e I$$

solve for $I(z)$.

$$I(z) = \frac{+\beta \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]}{+\omega L_e}$$

$$= \frac{\beta}{\omega L_e} \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

$$\beta = \omega \sqrt{L_e C_e}$$

$$\therefore \frac{\beta}{\omega L_e} = \frac{\cancel{\omega} \sqrt{L_e C_e}}{\cancel{\omega} L_e} = \sqrt{\frac{C_e}{L_e}}$$

$$\therefore I(z) = \sqrt{\frac{C_e}{L_e}} \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

the factor $\sqrt{\frac{C_e}{L_e}}$ must have units of Ω^{-1} !

Define $\sqrt{\frac{L\ell}{C\ell}}$ as the "characteristic impedance"


Z_0 of the transmission line. $Z_0 = \sqrt{\frac{L\ell}{C\ell}}$

Summary: For a trans. line driven by a harmonic signal, the volt. & current amplitudes along length of trans. line are given by:

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

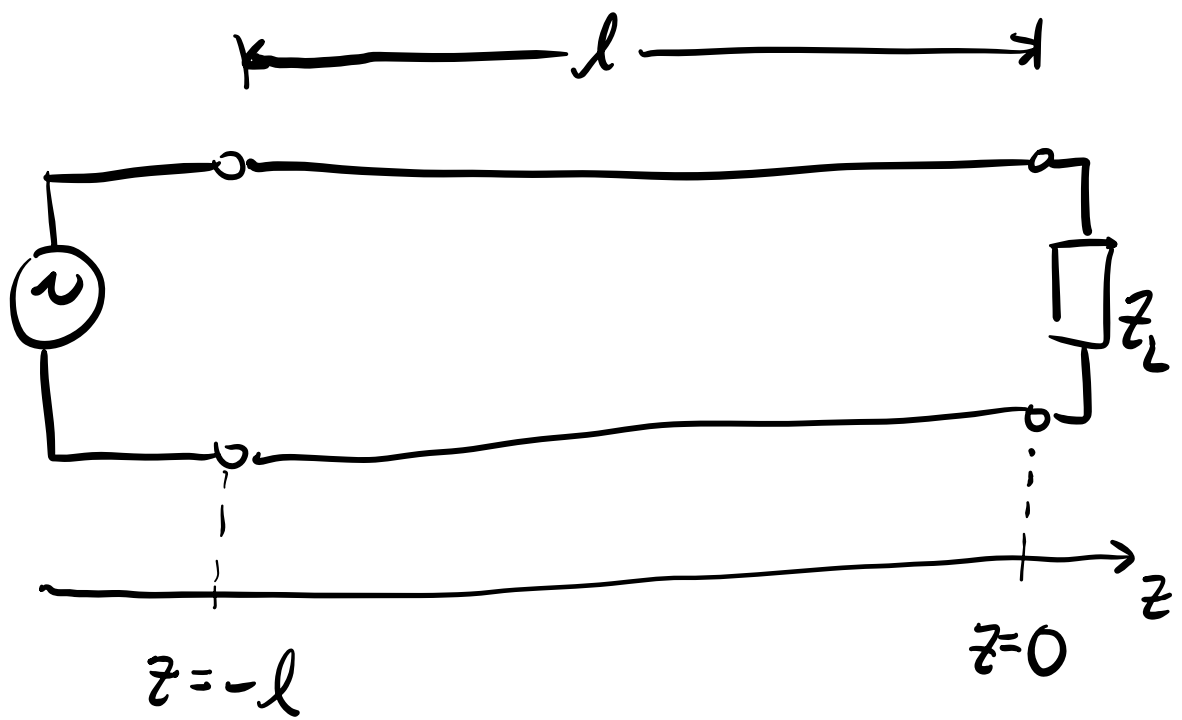Consider a trans. line of length l terminated by a "load" impedance Z_L at its end.



With the chose coord. system, the voltage & current amp. at the pos. of Z_L ($z=0$) are given by:

$$V(0) = V_+ + V_-$$

$$I(0) = \frac{1}{Z_0} [V_+ - V_-]$$

The ration $\frac{V(0)}{I(0)}$ must be equal to the load impedance Z_L at $z=0$

$$\frac{V(z)}{I(z)} = Z_L = Z_0 \left[\frac{V_+ + V_-}{V_+ - V_-} \right]$$



rearrange to express V_-
in terms of V_+ , Z_0 , Z_L .



Find

$$V_- = V_+ \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right)$$

amp. of
backwards travelling
wave

amp. of forward
travelling wave

reflection
coefficient.

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

transmission line
reflection coefficient.

$$\hookrightarrow V_- = \Gamma V_+$$


Special cases:

① $Z_L = 0$ (short circuit)

$$\Gamma = \frac{0 - Z_0}{0 + Z_0} = -1$$

↑ signal is inverted upon reflection (phase shift of 180°).

$$|\Gamma| = 1 \Rightarrow \text{perfect reflection}$$

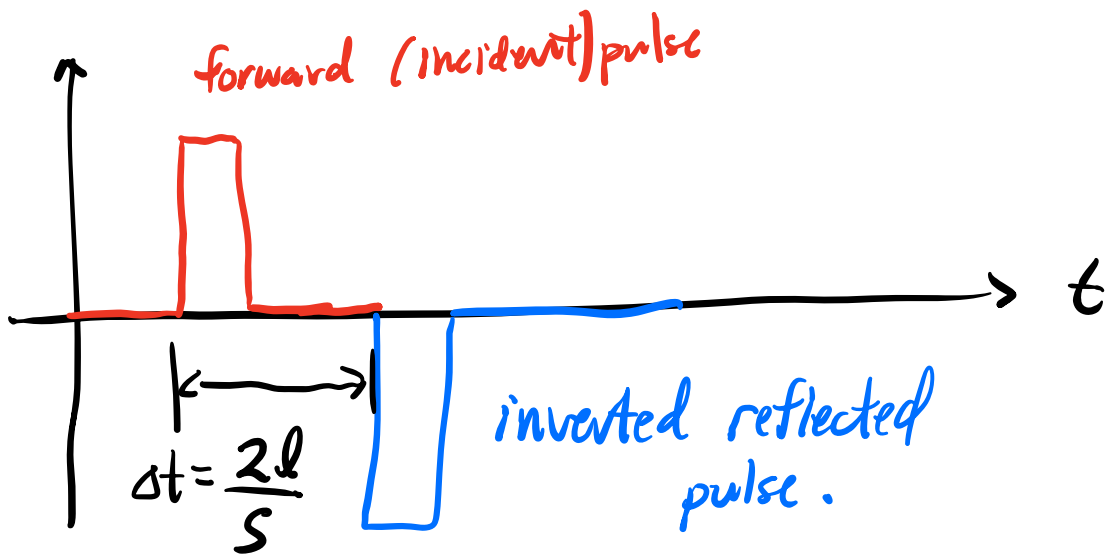


time for pulse to travel to end of trans. line & back again.

② $Z_L \rightarrow \infty$ (open circuit)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \approx \frac{Z_L}{Z_L} = +1$$

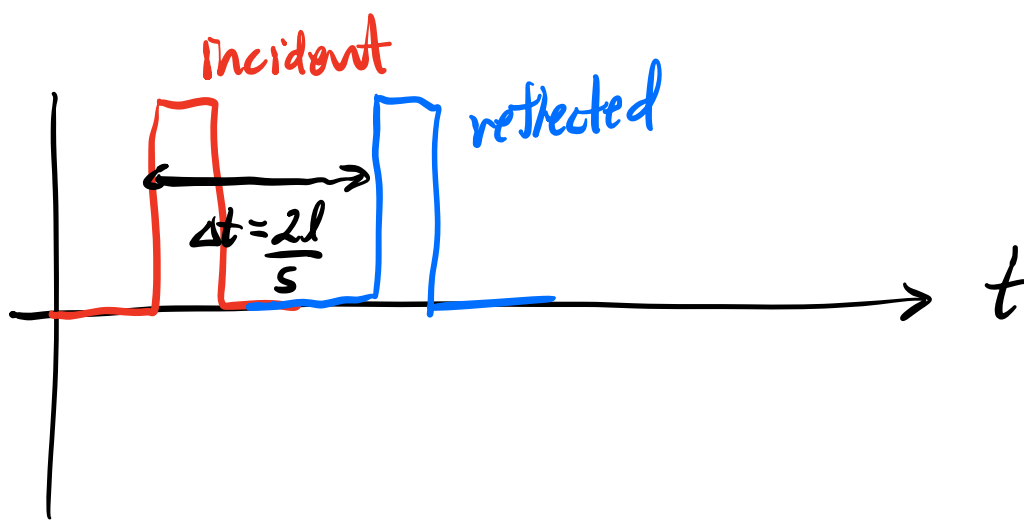another perfect reflection. No inversion.



③ $Z_L = Z_0$ (impedance matching)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - Z_0}{2Z_0} = 0$$

no reflection.

All signal absorbed
by load impedance Z_L .

$$\lambda f = c$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{60 \frac{1}{s}} = 0.5 \times 10^7 \text{ m}$$

$$= \cancel{5} \times 10^6 \text{ m}$$