

PHYS 331 - Oct. 23, 2023

Last Time:


Trans. line reflection coefficient $\Gamma = \frac{z_L - z_0}{z_L + z_0}$

Useful results:

volt. amp. $V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$


current amp. $I(z) = \frac{1}{z_0} [V_+ e^{-j\beta z} - V_- e^{j\beta z}]$

$$z_0 = \sqrt{\frac{L_1}{C_1}}$$

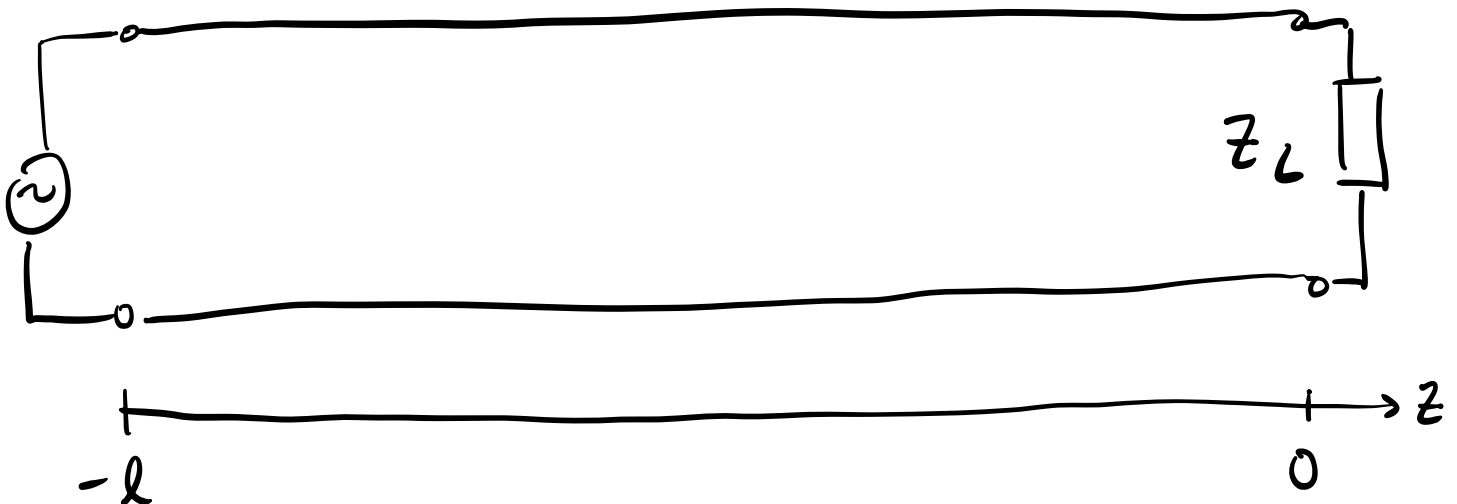

- Today:
- when are trans. line effects important?
 - impedance looking into a trans. line Z_{in} .
 - demo in SCI 239.

When are trans. line effects important?

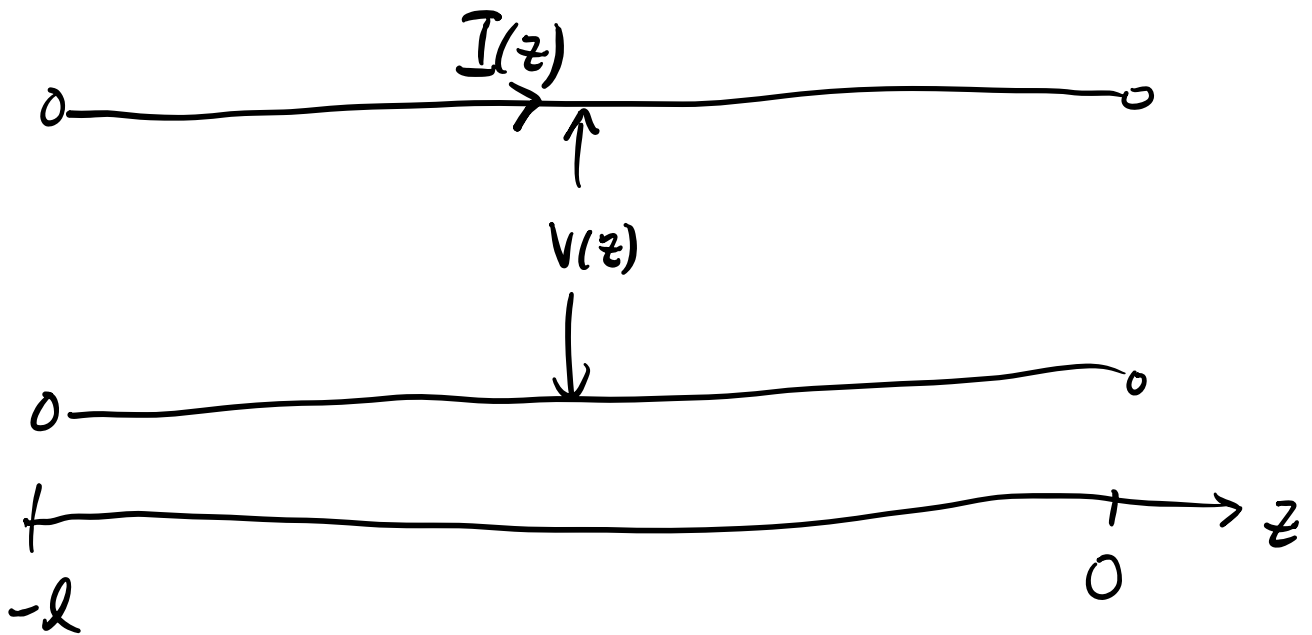

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

$$\beta = \frac{2\pi}{\lambda} = \omega \sqrt{L_l C_l} \quad Z_0 = \sqrt{\frac{L_l}{C_l}}$$

The coaxial cables used in the lab are called RG-58 & designed s.t.

$$\left. \begin{array}{l} C_e \approx 80 \text{ pF/m} \\ L_e \approx 0.20 \mu\text{H/m} \end{array} \right\} Z_0 = \sqrt{\frac{L_e}{C_e}} \approx 50 \Omega.$$

$$\beta = \omega \sqrt{L_e C_e} \quad \text{let's take } \omega = 2\pi(10 \text{ kHz})$$
$$\approx 2.5 \times 10^{-4} \text{ m}^{-1} \ll 1 \text{ m}^{-1}$$

If we take $z = 1 \text{ m}$ (typical)

then

$$\beta z \approx 2.5 \times 10^{-4} \ll 1$$

$$\therefore V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

1 for $\beta z \ll 1$

$$V(z) \approx V_+ + V_- \quad (\text{const}).$$

for current amp., would find

$$I(z) \approx \frac{1}{Z_0} [V_+ - V_-] \quad (\text{const})$$

When $\beta z \ll 1$, current $\{$ volt. amp is uniform along length of trans line $\}$ we can ignore trans line effects.

$$\text{Recall } \beta = \frac{2\pi}{\lambda} \Rightarrow \lambda = \frac{2\pi}{\beta}$$

using $\beta = 2.5 \times 10^{-4} \text{ m}^{-1}$, we get

$$\lambda = 25 \text{ km!}$$

When λ much longer than the trans. line length l , we can ignore these effects.

If, on the other hand, we take

$$\omega = 2\pi (3 \text{ GHz})$$

$$3 \times 10^9 \text{ Hz}$$

$$\text{then } \beta = \omega \sqrt{LlCl} \approx 75 \text{ m}^{-1}$$

In this case, for $z \approx 1 \text{ m}$, the product βz not small.

Cannot approx. $e^{\pm j\beta z} \approx 1$.

Now $V(z)$ & $I(z)$ do vary along length line \Rightarrow trans. line effects are important.

$$\lambda = \frac{2\pi}{\beta} \approx 8 \text{ cm} \ll l.$$

Impedance at an arbitrary pos. z along transmission line.

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

at an arbitrary pt. along trans. line, the impedance $Z(z)$

Impedance \nearrow position \uparrow

$$* Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_+ e^{-j\beta z} + V_- e^{j\beta z}}{V_+ e^{-j\beta z} - V_- e^{j\beta z}}$$



Recall that $V_- = \Gamma V_+$

$$Z(z) = Z_0 \frac{\cancel{V_+} (e^{-j\beta z} + \Gamma e^{j\beta z})}{\cancel{V_+} (e^{-j\beta z} - \Gamma e^{j\beta z})}$$

$$\text{Sub } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z(z) = Z_0 \frac{e^{-j\beta z} + \left(\frac{Z_L - Z_0}{Z_L + Z_0}\right) e^{j\beta z}}{e^{-j\beta z} - \left(\frac{Z_L - Z_0}{Z_L + Z_0}\right) e^{j\beta z}} \quad \begin{array}{l} \text{mult. by} \\ \frac{Z_L + Z_0}{Z_L + Z_0} \end{array}$$

$$Z(z) = z_0 \frac{(z_L + z_0)e^{-j\beta z} + (z_L - z_0)e^{j\beta z}}{(z_L + z_0)e^{-j\beta z} - (z_L - z_0)e^{j\beta z}}$$

collect like terms of z_L & z_0 .

$$Z(z) = z_0 \frac{z_L(e^{-j\beta z} + e^{j\beta z}) + z_0(e^{-j\beta z} - e^{j\beta z})}{z_L(e^{-j\beta z} - e^{j\beta z}) + z_0(e^{-j\beta z} + e^{j\beta z})}$$

Identities: $e^{+j\beta z} + e^{-j\beta z} = 2\cos\beta z$

$$e^{j\beta z} - e^{-j\beta z} = 2j\sin\beta z$$

$$Z(z) = z_0 \frac{\cancel{2}z_L \cos\beta z - \cancel{2}j z_0 \sin\beta z}{-\cancel{2}j z_L \sin\beta z + \cancel{2}z_0 \cos\beta z}$$

divide by $\cos\beta z$

$$Z(z) = z_0 \frac{z_L - jz_0 \tan\beta z}{z_0 - jz_L \tan\beta z}$$

To find the impedance looking into trans. line from its start, sub in

$$z = -l. \quad \text{Recall that } \tan(-\beta l) \\ = -\tan \beta l$$

$$Z_{in} \equiv Z(-l) = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

The impedance of a length of trans. line depends on:

- load impedance Z_L at the end.
- geometry of trans. line which sets value of Z_0
- length l of trans. line
- freq. ω of signal through $\beta = \omega \sqrt{LC}$

Special cases:

① $\beta l = n\pi \rightarrow$ select l s.t. we satisfy $\beta l = n\pi$ where n integer.

$$\frac{2\pi}{\lambda} l = n\pi \Rightarrow l = n \left(\frac{\lambda}{2} \right)$$

Select l to be integer
mult. of $\lambda/2$

$$\tan \beta l = \tan n\pi = 0.$$

$$Z_{in} = \cancel{Z_0} \frac{Z_L}{\cancel{Z_0}} \Rightarrow \boxed{Z_{in} = Z_L}$$

like trans. line is
not there.

$$\textcircled{2} \quad \beta l = n' \left(\frac{\pi}{2} \right) \quad n': \text{ odd } \neq \text{ integer.}$$

$$\frac{2\pi}{\lambda} l = n' \left(\frac{\pi}{2} \right)$$

$$l = n' \left(\frac{\lambda}{4} \right) \quad \begin{array}{l} \text{odd.} \\ \text{mult. of quarter} \\ \text{wavelength} \end{array}$$

$$\tan(\beta l) = \tan\left(n' \frac{\pi}{2}\right) \rightarrow \pm \infty$$

In this case

$$Z_{in} \approx Z_0 \frac{\cancel{j Z_0 \tan \beta l}}{\cancel{j Z_L \tan \beta l}}$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

"transform the impedance".

(3) $Z_L = Z_0$ (impedance matching condition).

$$Z_{in} = Z_0 \frac{\cancel{Z_L}^{Z_0} + j Z_0 \tan \beta l}{Z_0 + j \cancel{Z_L}^{Z_0} \tan \beta l}$$

$$\therefore Z_{in} = Z_0$$