

PHYS 331 - September 11, 2023

## Lock-in Detection

Lock-in detectors are good at meas. the amplitude & phase of small AC signals when the freq. of the desired signal is known.

Recall that we can represent any complex number using:

① mag. & phase

$$z = |z| e^{j\theta} = |z| \underbrace{(\cos\theta + j\sin\theta)}_{e^{j\theta}}$$

② real & imaginary component

$$z = \overset{\uparrow}{x} + j \underset{\text{imaginary}}{y}$$

real

Switch between the two representations:

$$|z| = \sqrt{x^2 + y^2}$$

$$\tan \phi = \frac{y}{x}$$


$$x = |z| \cos \phi$$

$$y = |z| \sin \phi$$

We want to show that a lock-in detector can be used to find the real ( $x$ ) and imaginary ( $y$ ) components of a signal. Thus, we can calc. the signal amp. from  $\sqrt{x^2 + y^2}$  & signal phase from

$$\phi = \tan^{-1}\left(\frac{y}{x}\right).$$

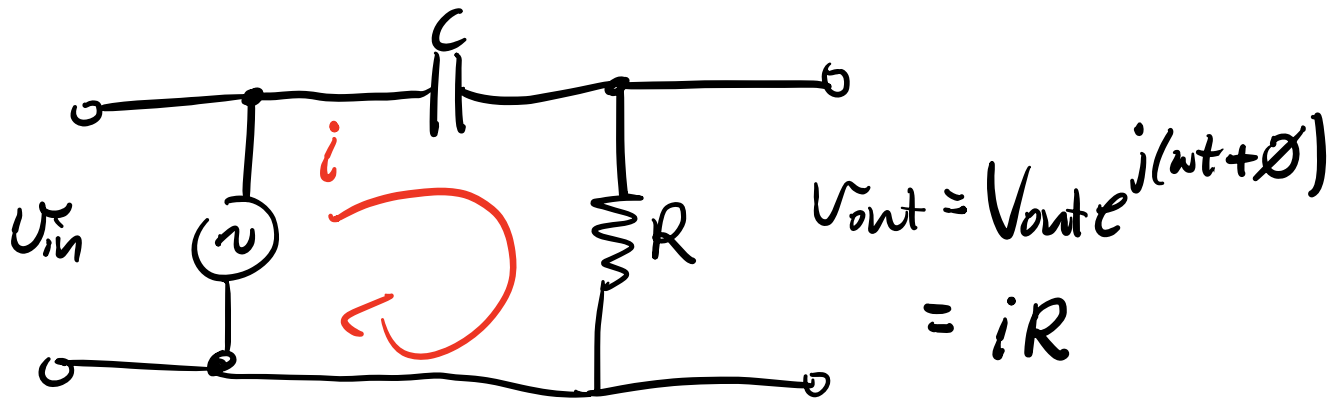To understand the physical meaning of the real & imaginary components of a signal, let's consider an RC circuit.



$$U_{in} = V_{in} e^{j\omega t}$$

$$i = \frac{U_{in}}{Z} \quad Z = R + \underbrace{\frac{1}{j\omega C}}_{Z_C} = \frac{j\omega RC + 1}{j\omega C}$$

$$i = U_{in} \left( \frac{j\omega C}{1 + j\omega RC} \right) \frac{(1 - j\omega RC)}{(1 - j\omega RC)}$$

$$= U_{in} \frac{\omega C (j + \omega RC)}{1 + (\omega RC)^2}$$

$$\underline{V_{out}} = iR = U_{in} \frac{\omega RC (j + \omega RC)}{1 + (\omega RC)^2}$$

Sub in  $V_{in} = V_{in} e^{j\omega t}$

$$V_{out} = V_{out} e^{j(\omega t + \phi)} = V_{out} e^{j\omega t} e^{j\phi}$$

$$V_{out} \cancel{e^{j\omega t}} \underbrace{e^{j\phi}}_{\cos\phi + j\sin\phi} = V_{in} \cancel{e^{j\omega t}} \frac{\omega RC (j + \omega RC)}{1 + (\omega RC)^2}$$

$$V_{out} (\cos\phi + j\sin\phi) = V_{in} \frac{\omega RC (j + \omega RC)}{1 + (\omega RC)^2}$$

set real & imaginary parts equal on left & right sides.

Real:

$$V_{out} \cos\phi = V_{in} \frac{(\omega RC)^2}{1 + (\omega RC)^2} \equiv X$$

Imaginary:  $V_{out} \sin\phi = \frac{V_{in} \omega RC}{1 + (\omega RC)^2} \equiv Y$

X is the "real" component of  $V_{out}$   
Y is the "imaginary" component of  $V_{out}$ .

If we know  $x$  &  $y$ , we can calc. the amp. & phase of  $V_{out}$ .

$$\sqrt{x^2 + y^2} = V_{out} = \sqrt{\frac{V_{in}^2 \left[ (\omega RC)^2 + (\omega RC)^4 \right]}{\left[ 1 + (\omega RC)^2 \right]^2}}$$

$$= V_{in} \omega RC \frac{\sqrt{1 + (\omega RC)^2}}{1 + (\omega RC)^2}$$

$$\therefore V_{out} = V_{in} \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$


high-pass filter.

Phase:  $\tan \phi = \frac{y}{x} = \frac{\cancel{V_{in}} \cancel{\omega RC}}{1 + \cancel{(\omega RC)^2}}$


$$\frac{\cancel{V_{in}} (\omega RC)^2}{1 + \cancel{(\omega RC)^2}}$$

$$\tan \phi = \frac{1}{\omega RC}$$

Interpret  $\phi$ .

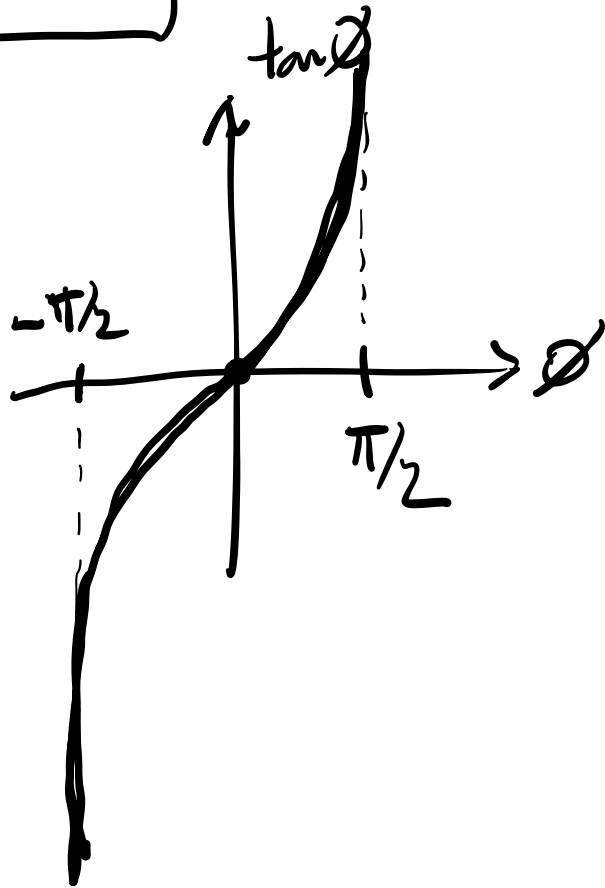
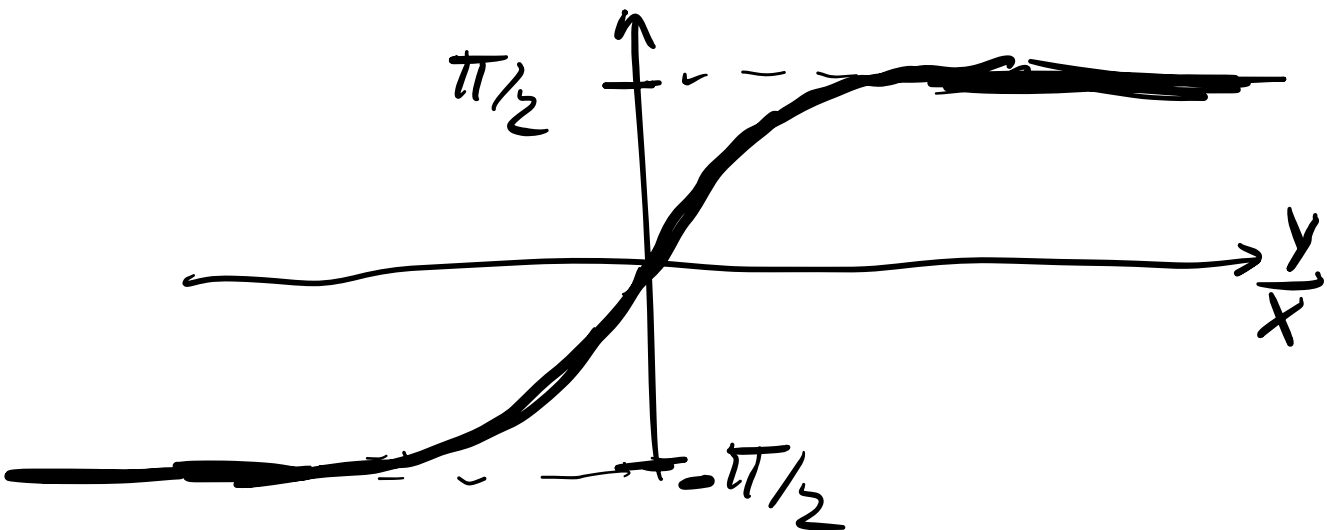
$$\phi = \tan^{-1} \left( \frac{y}{x} \right)$$



Notice if the imaginary component of a signal is zero ( $y=0$ ), then

$$\frac{y}{x} = 0 \quad \& \quad \boxed{\phi = 0.}$$

When an output is shifted in phase relative to an input signal, it implies that the output has both real & imaginary components.