

# Exploring the Non-ideal Characteristics of Transmission Lines

Jake Bobowski



PHYS 331



Thursday, November 20, 2023

University of British Columbia – Okanagan Campus

Kelowna, British Columbia, Canada


<http://physics.ok.ubc.ca/welcome.html>

# Transient response...

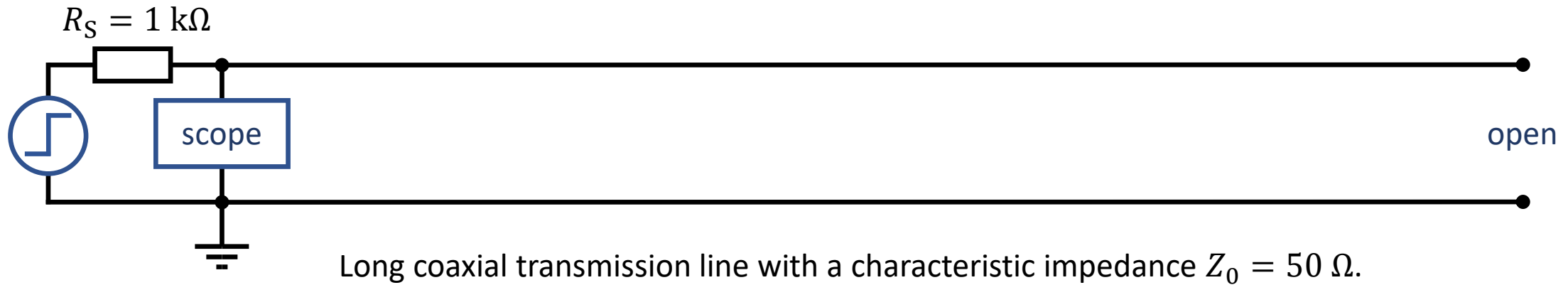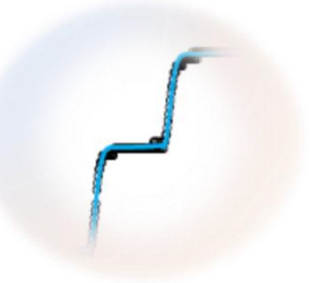

If the output of the signal generator steps instantaneously from zero to  $V_0$ , what is the expected  $v(t)$  measured by an oscilloscope at the transmission line input?

# Transient response...




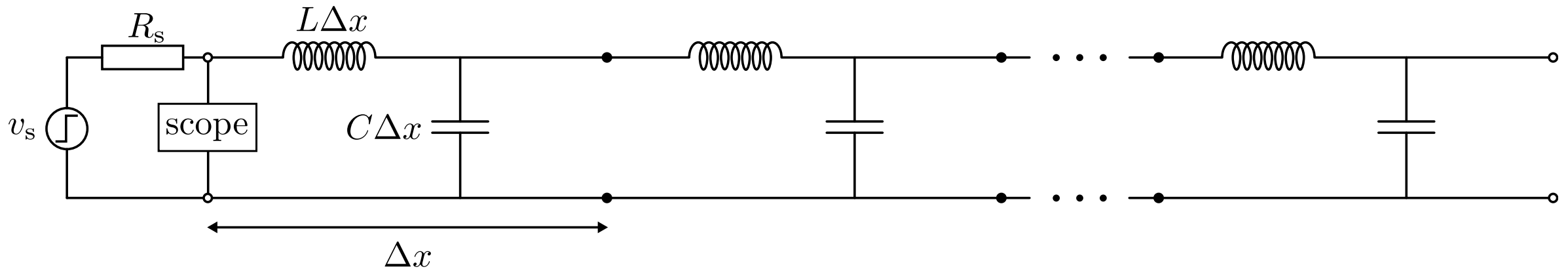


The case of an ideal (lossless) transmission line can be analyzed using a number of different methods:

- So-called “bounce diagrams”  
(Transients on Bounded Transmission Lines - [https://web.mit.edu/6.013\\_book/www/chapter14/14.4.html](https://web.mit.edu/6.013_book/www/chapter14/14.4.html))
- Inverse Fourier transform of the equivalent frequency-domain analysis  
(A Fourier Transform Approach to Transmission-Line Analysis - DOI: [10.1109/TE.1970.4320549](https://doi.org/10.1109/TE.1970.4320549))
- Inverse Laplace transform  
(Modeling and Measuring the Non-ideal Characteristics of Transmission Lines – DOI: [10.1119/10.0001896](https://doi.org/10.1119/10.0001896))



# Transient response...

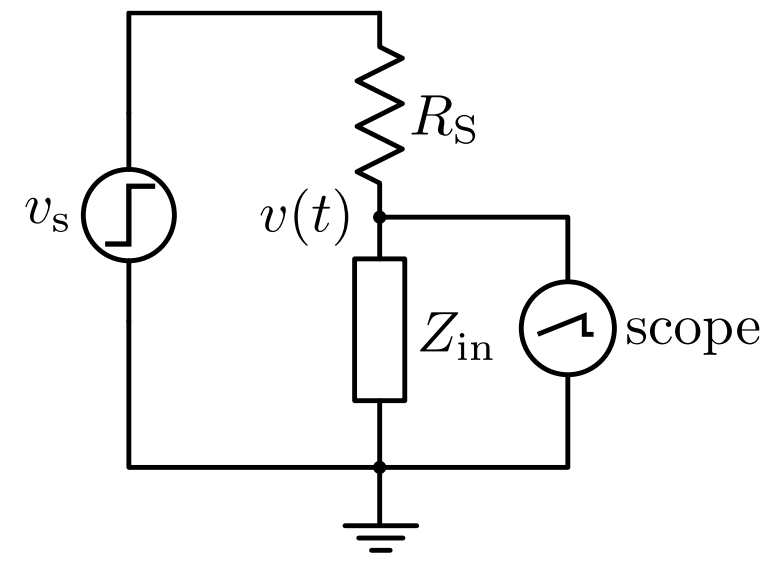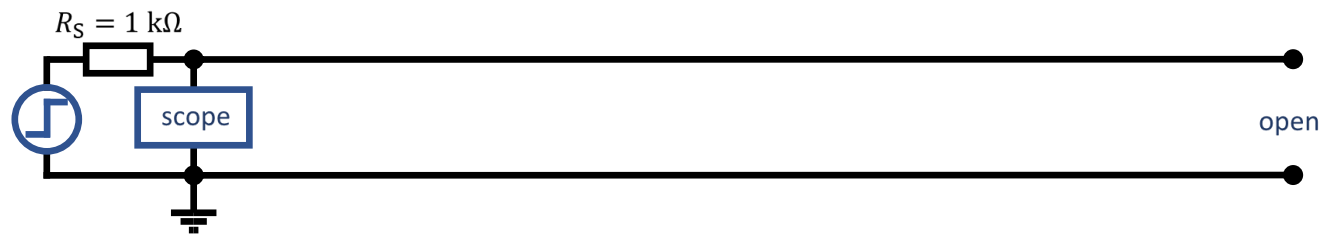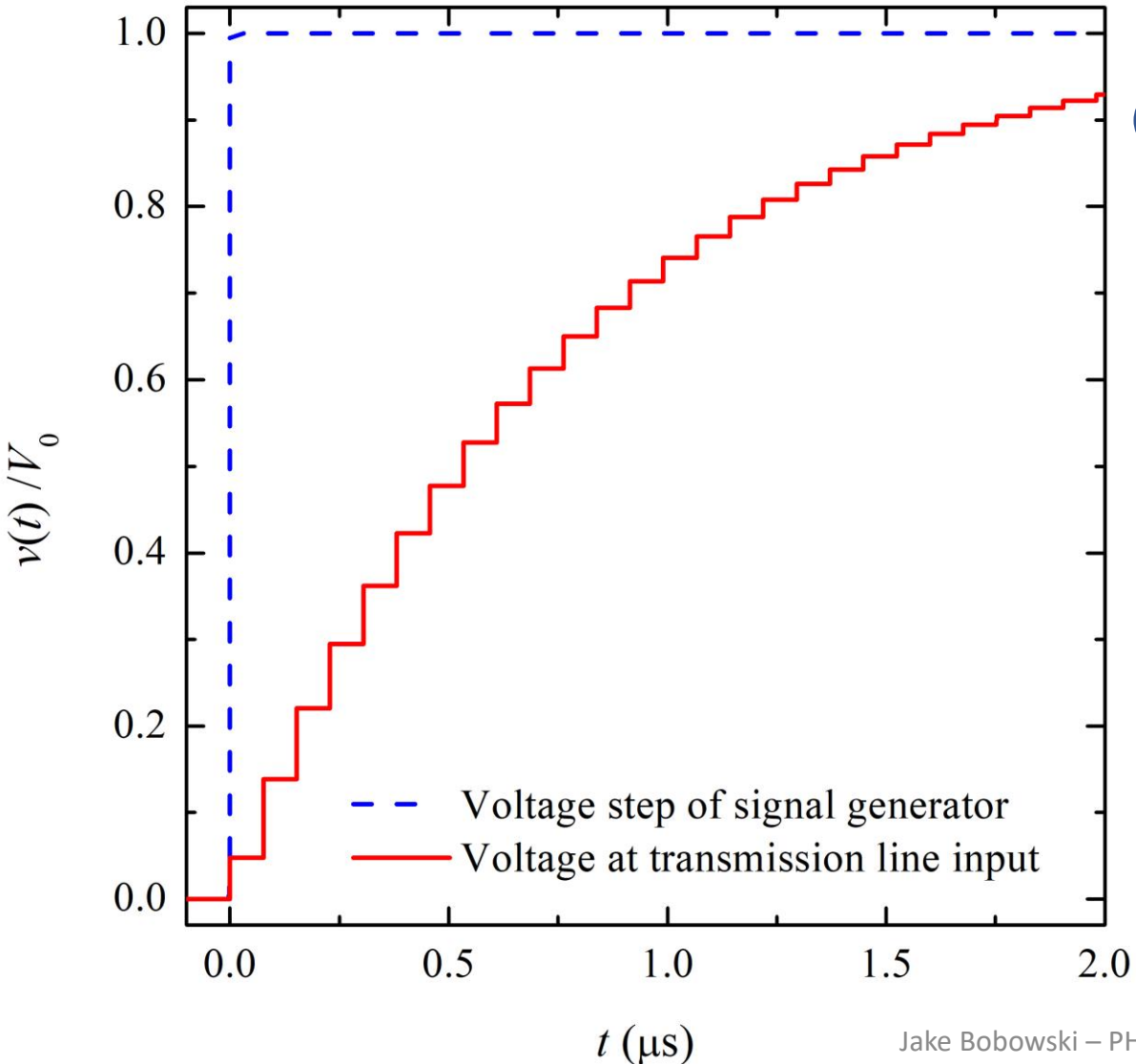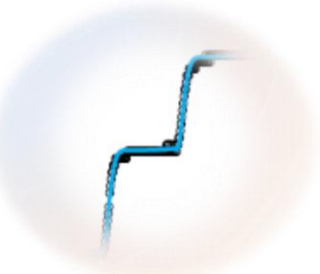


# Transient response...






Pulse generator: HP 8011A

Oscilloscope: Tektronix  
TDS 2002C (70 MHz)

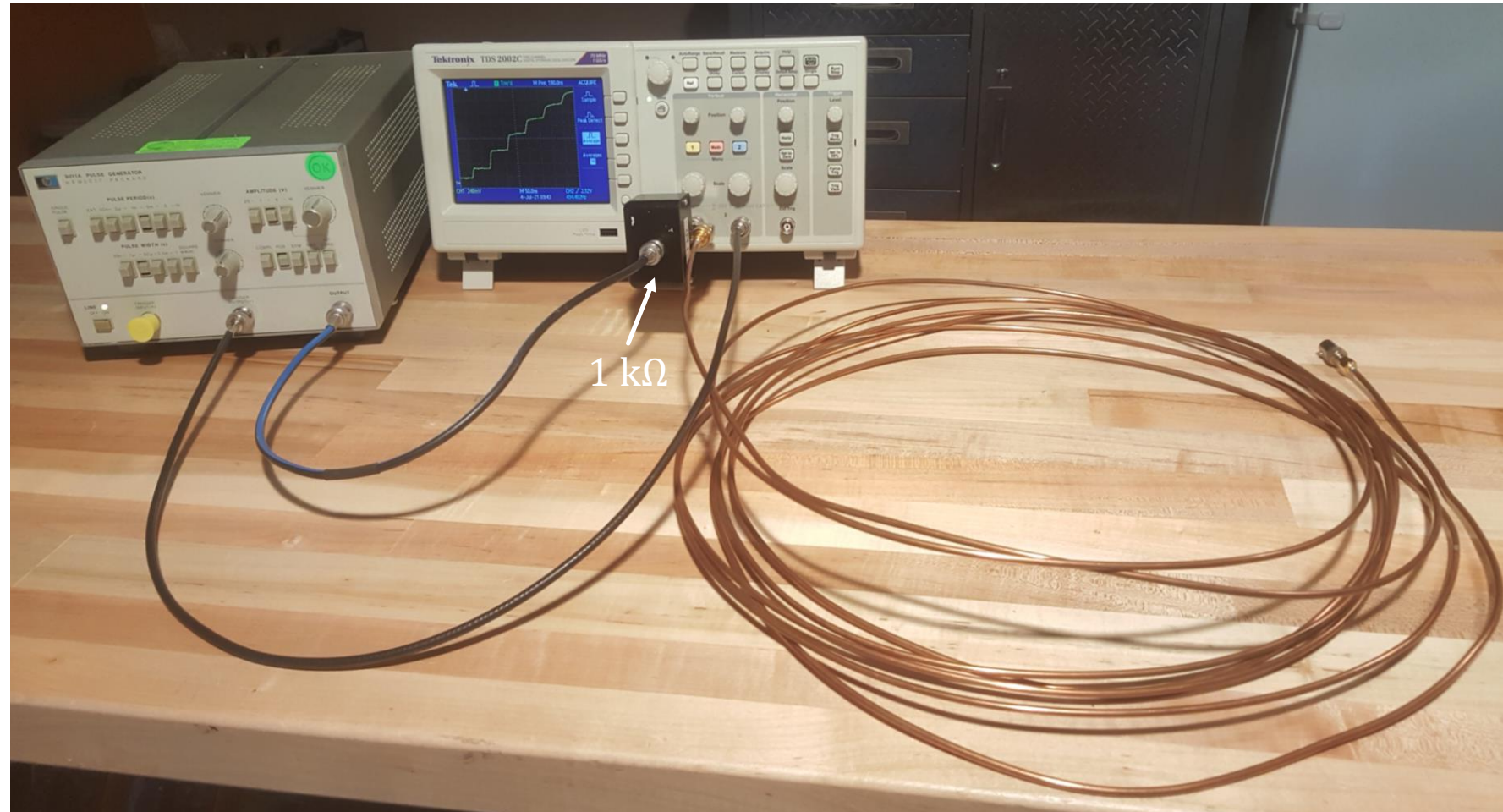
Coax: UT-141 semi-rigid (8-m long)  
copper outer conductor  
SPCW inner conductor



# Transient response...

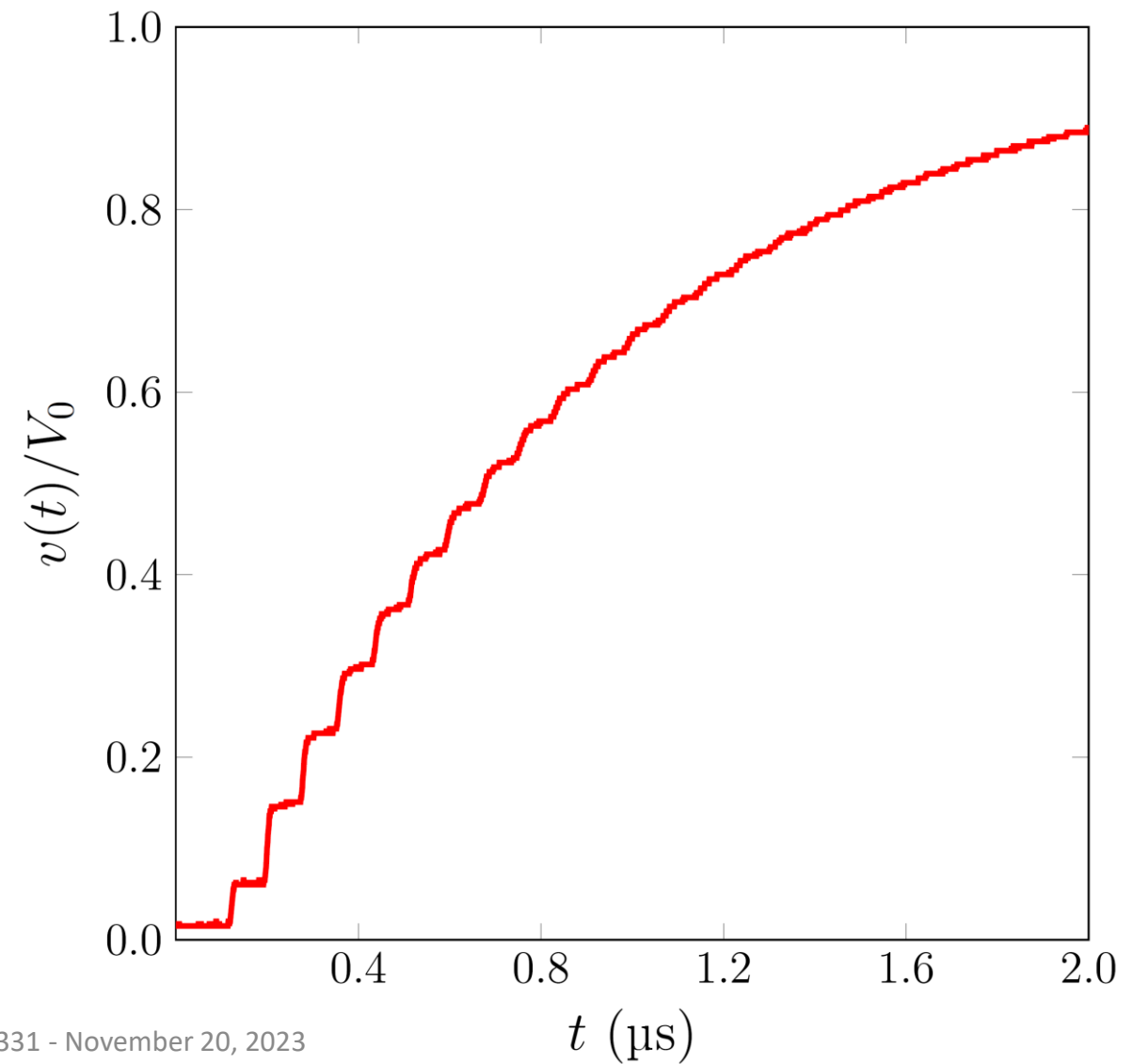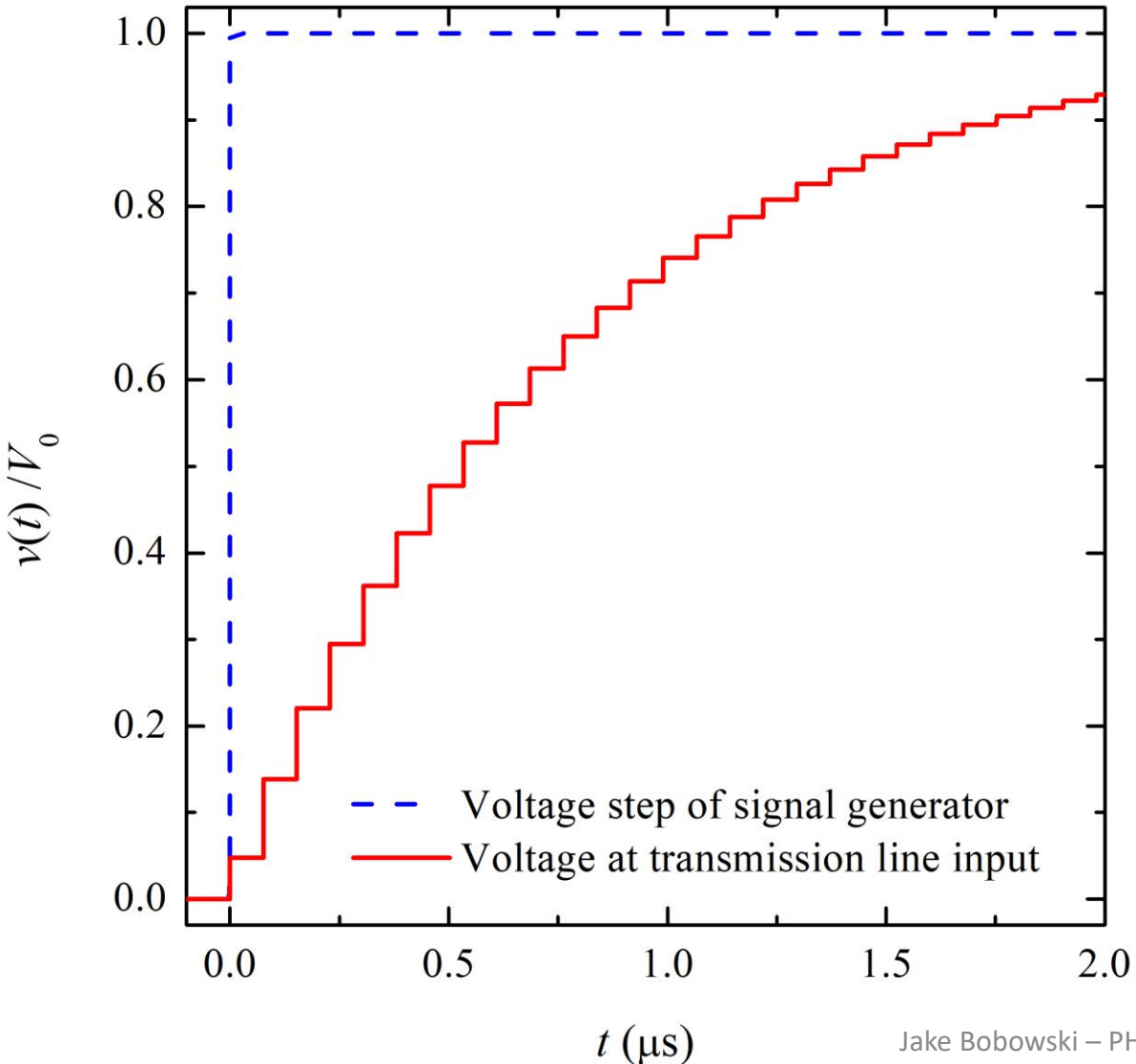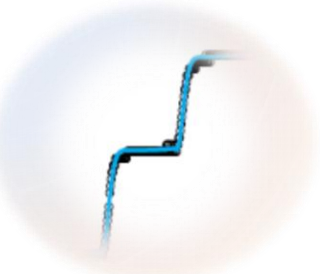



# Transient response...

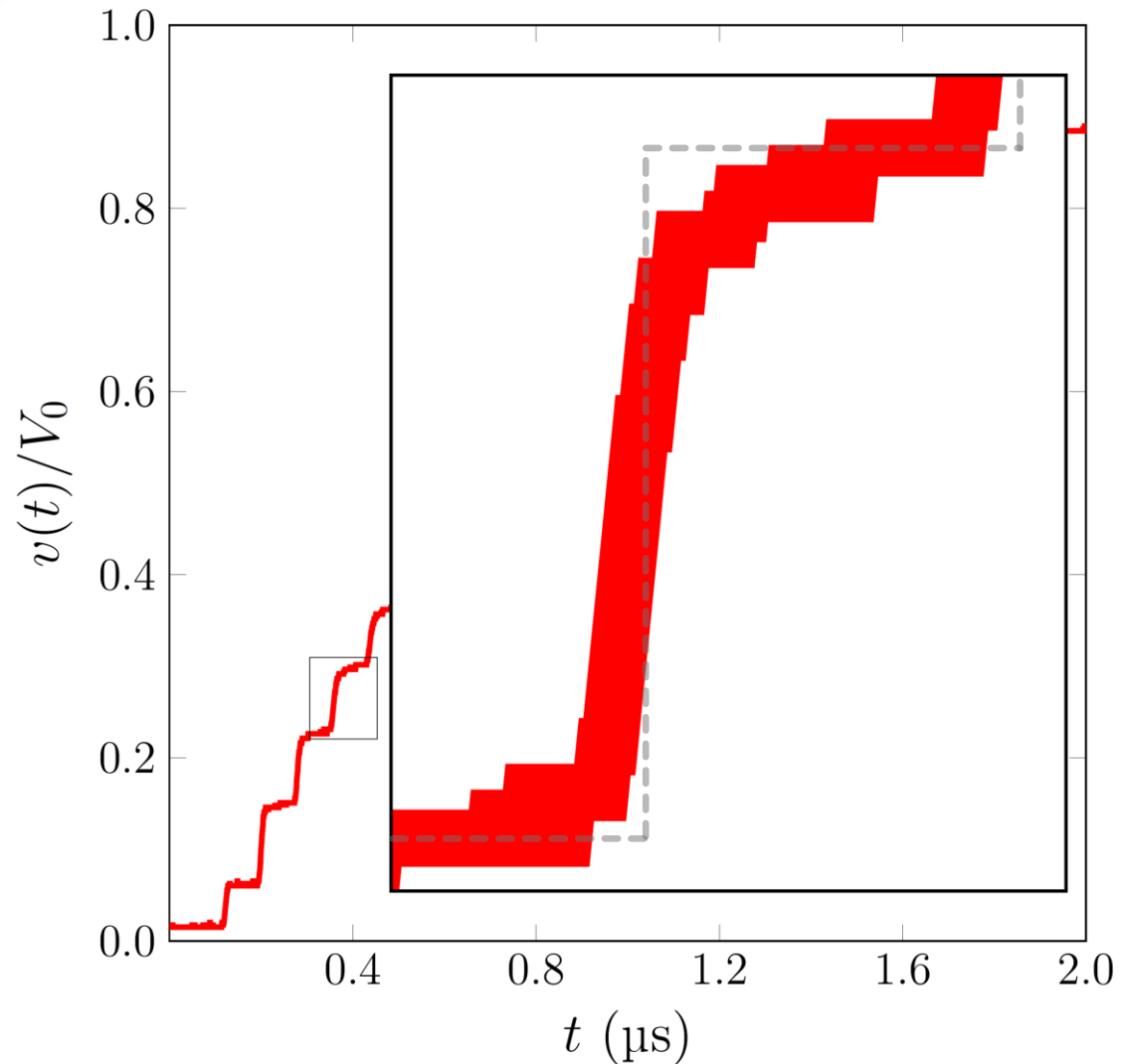

Non-ideal features:




- Finite slope of vertical part of step
- Non-zero slope of horizontal part of the step
- Rounded corners
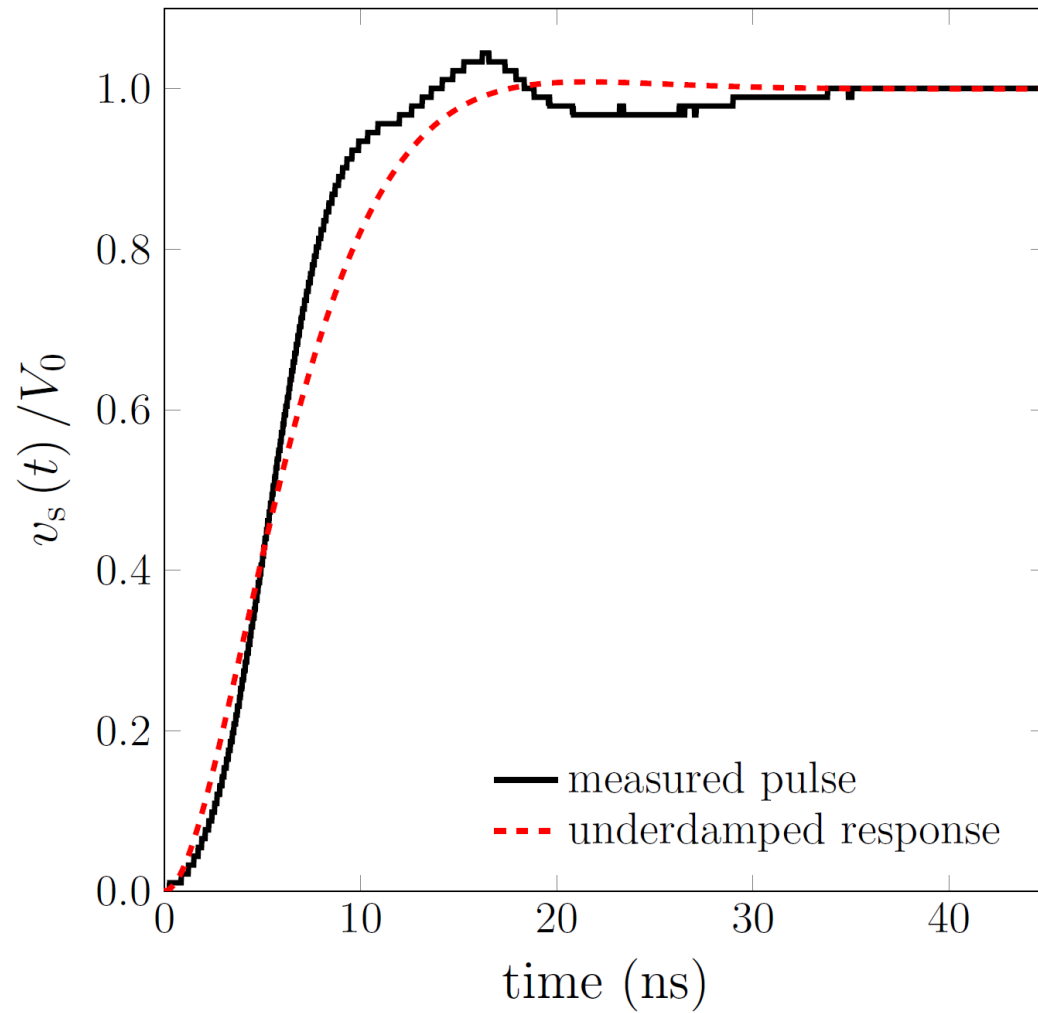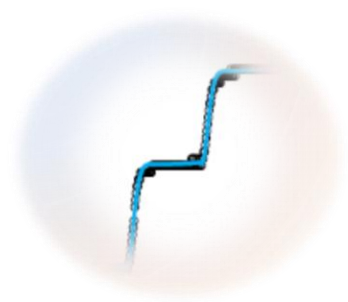
# Transient response with finite rise time...





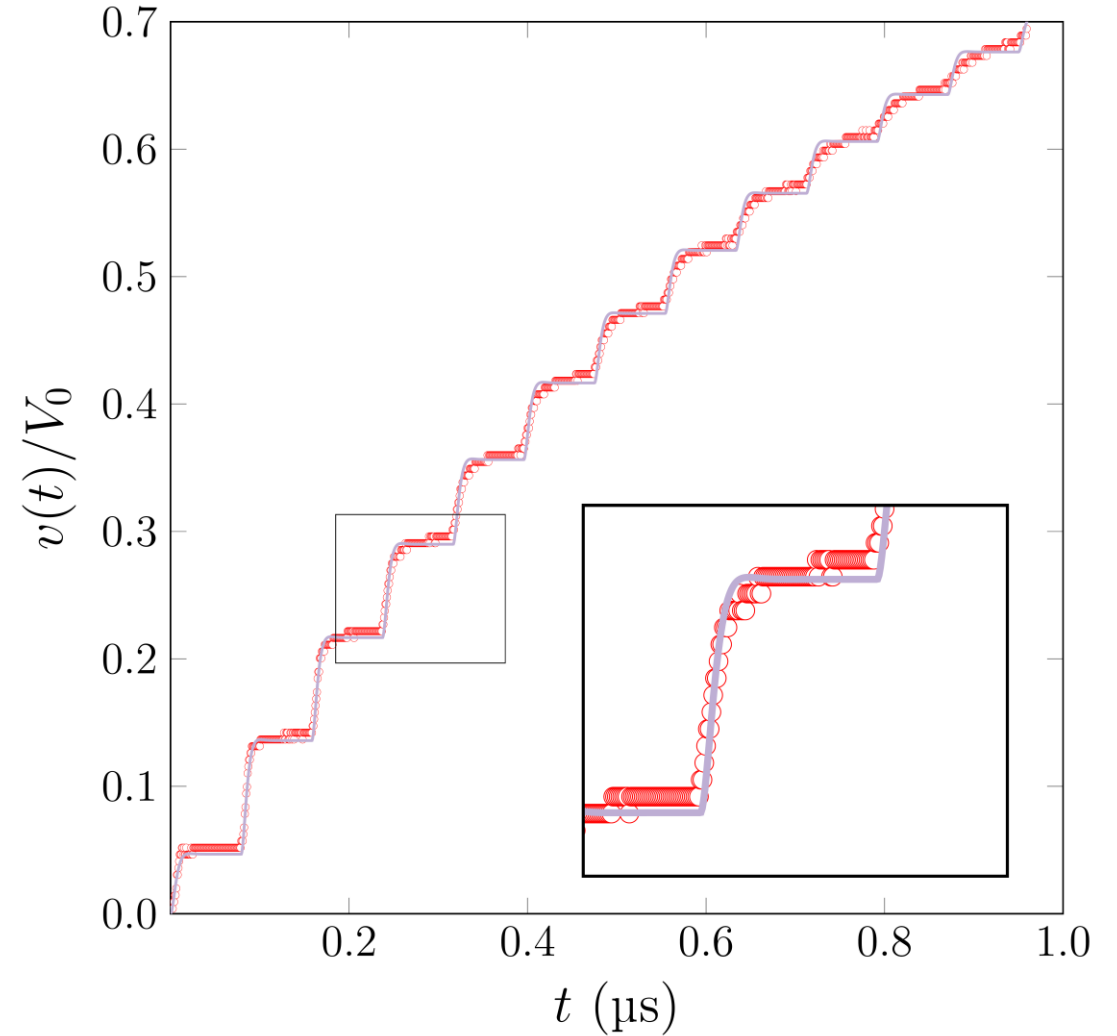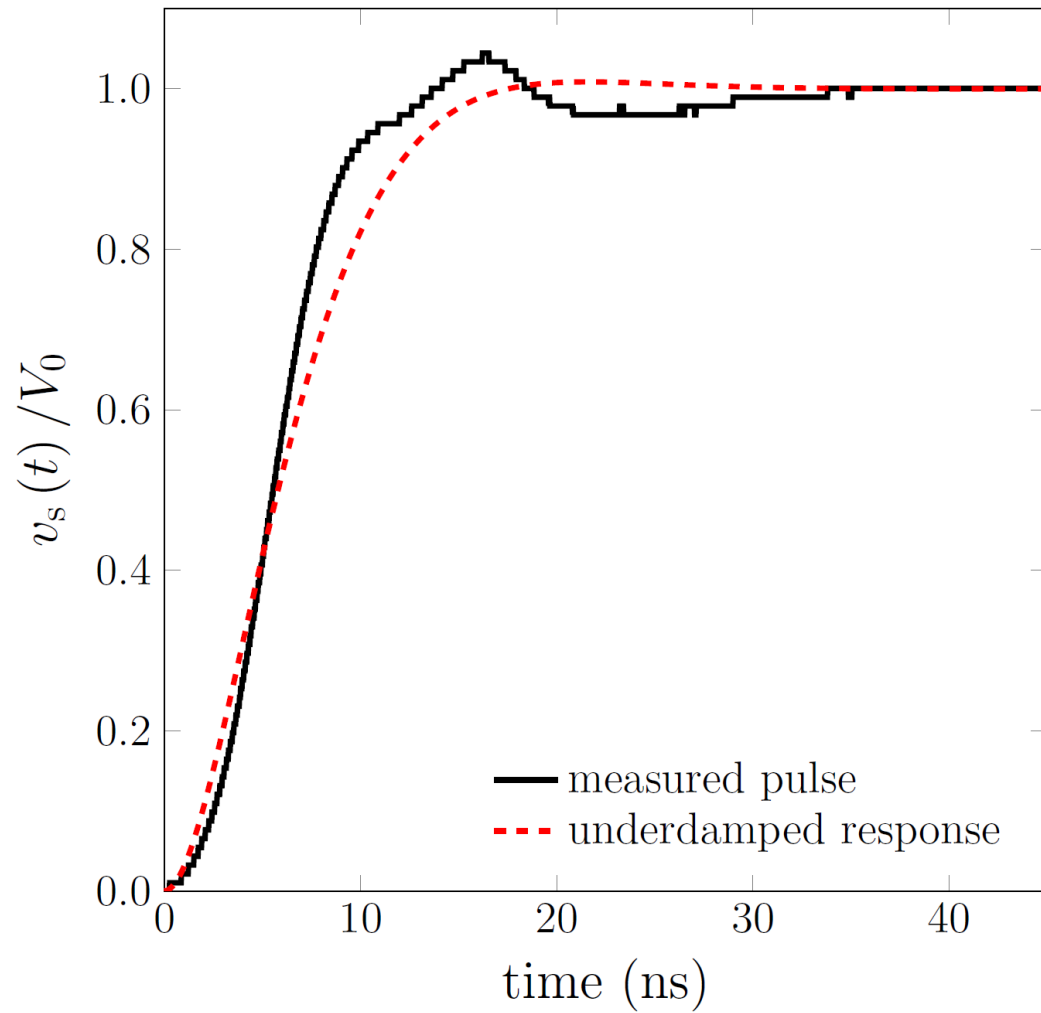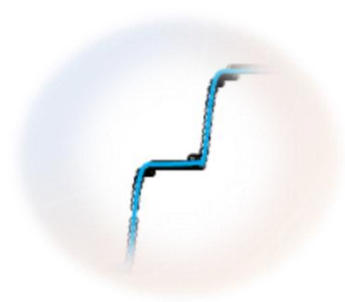
# Transient response with finite rise time...



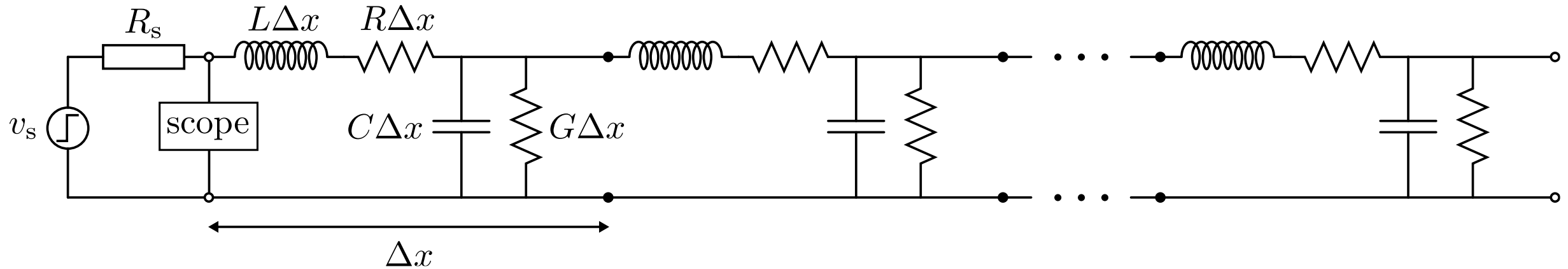
# Transmission line losses...

Model both the dielectric and conductor losses of a coaxial transmission line.  
Include these effects in the calculated transient response.



Modeling and measuring the non-ideal characteristics of transmission lines, Am. J. Phys. **89**, 96–104 (2021).
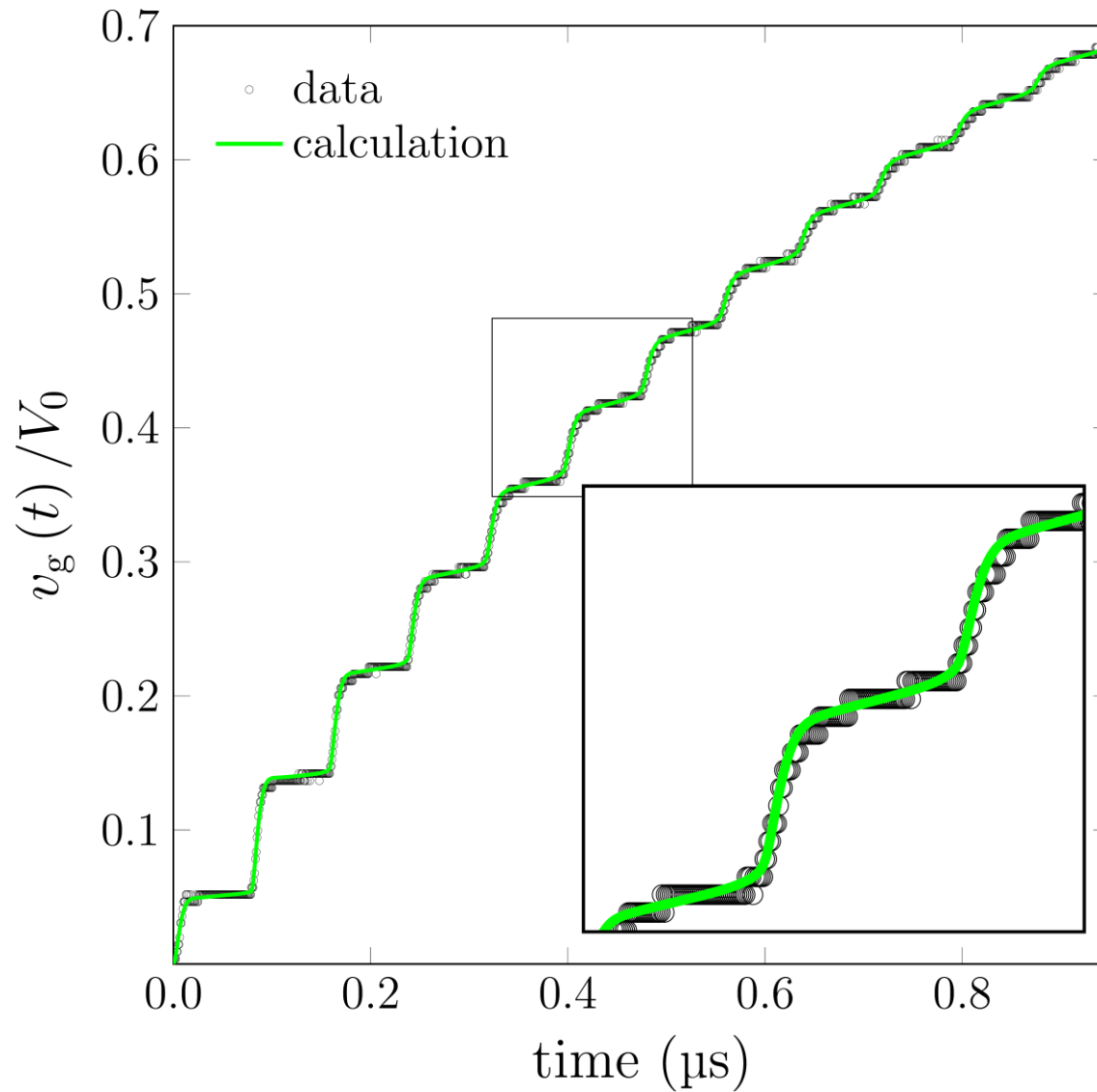
# Transients in a lossy transmission line...




Includes:

- Finite rise time
- Conductor losses
- Dielectric losses had no effect





# Transmission line losses...

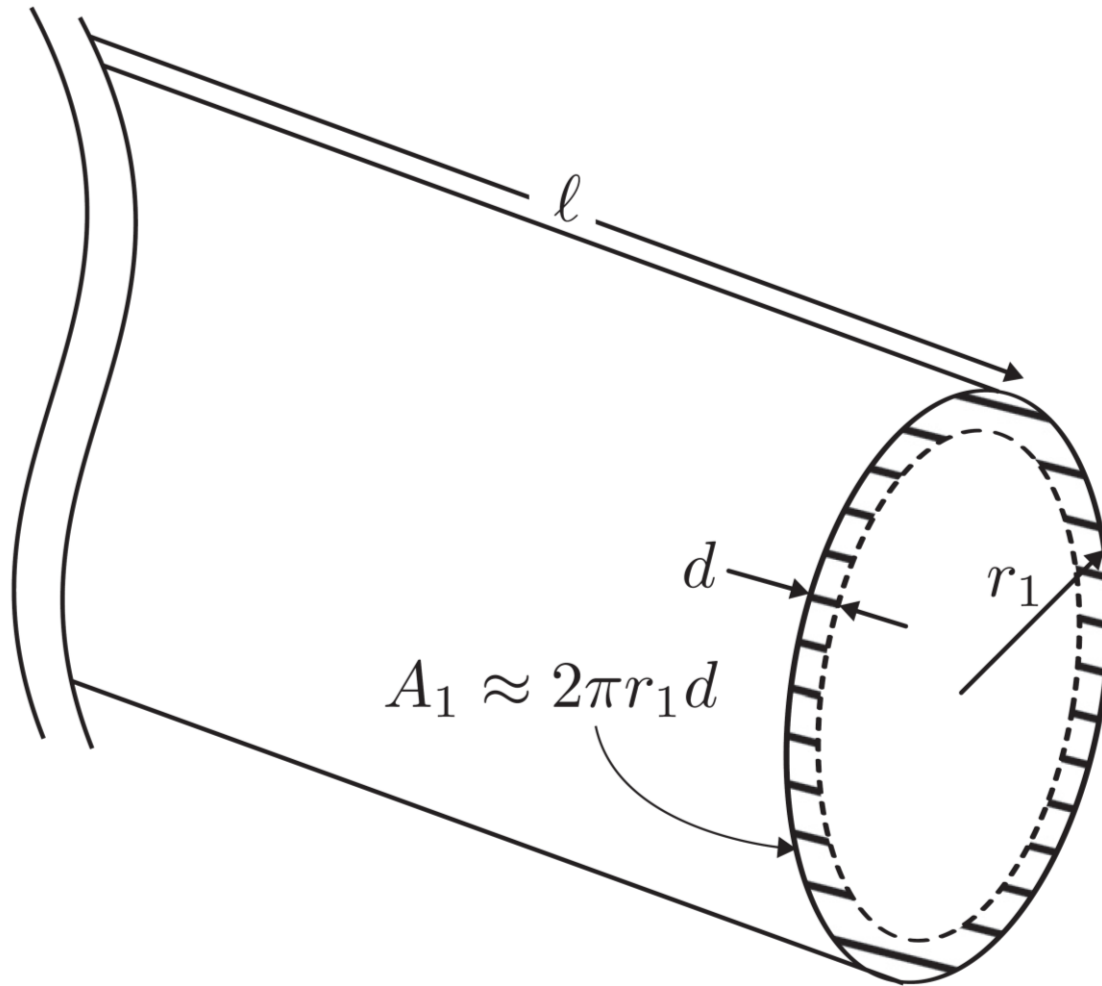

Skin depth:


$$d = \sqrt{\frac{2\rho}{\mu_0\omega}}$$

Resistance per unit length:

$$R = \frac{\rho}{2\pi r_1 d} = \frac{1}{2\pi r_1} \sqrt{\frac{\mu_0 \rho \omega}{2}}$$

Modeling and measuring the non-ideal characteristics of transmission lines, Am. J. Phys. **89**, 96—104 (2021).

# Transmission line losses...

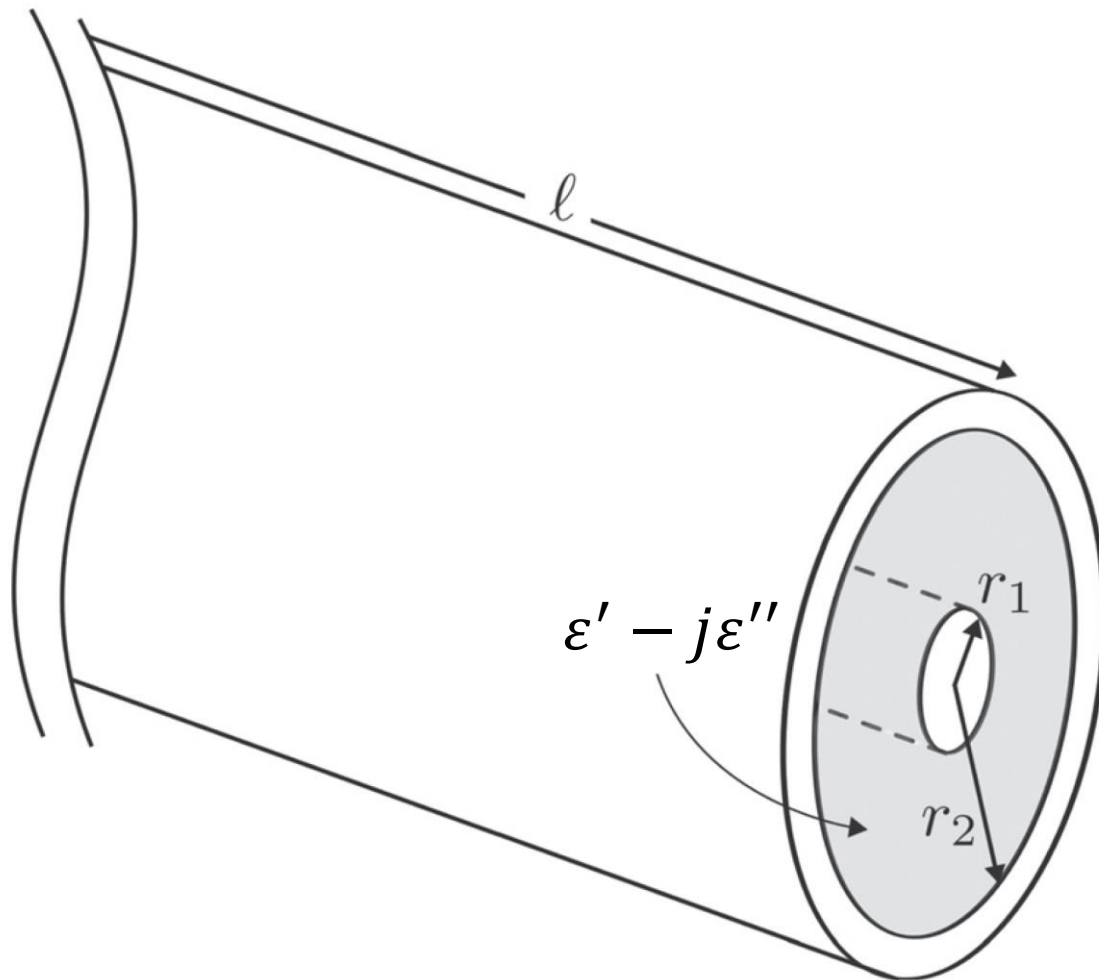

Admittance per unit length:

$$j\omega C = j\omega \left[ \frac{2\pi\epsilon_r\epsilon_0}{\ln(r_2/r_1)} \right]$$

Conductance per unit length:




$$G = \frac{2\pi\omega\epsilon''\epsilon_0}{\ln(r_2/r_1)}$$

Modeling and measuring the non-ideal characteristics of transmission lines, Am. J. Phys. **89**, 96—104 (2021).

# Transmission line losses... cooling to 77 K



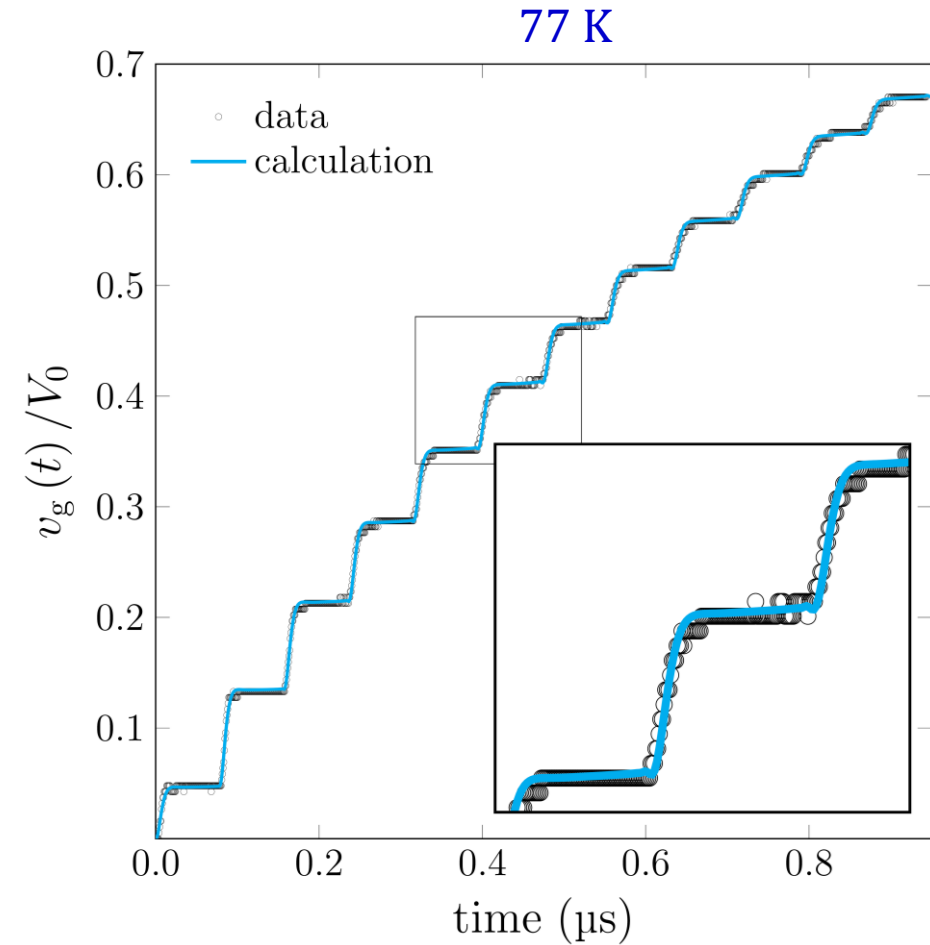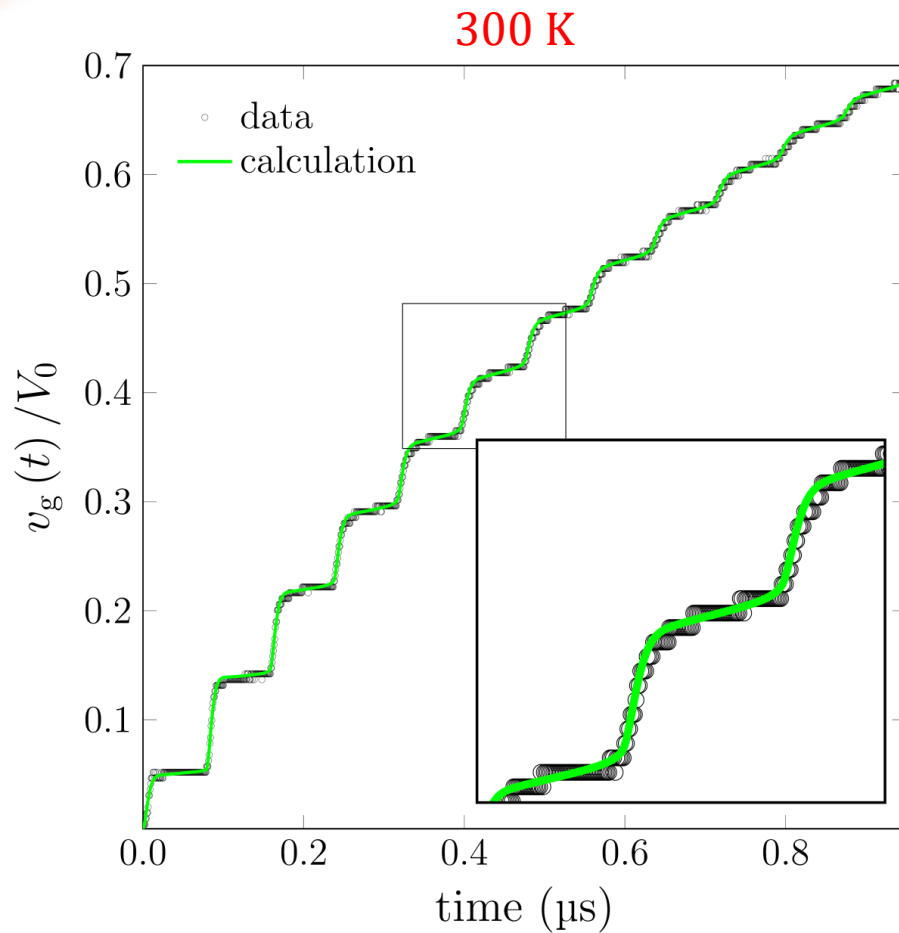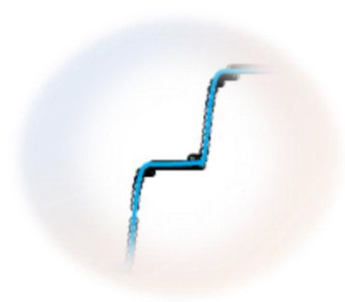
# Transmission line losses... cooling to 77 K



Transients in lossy transmission lines, arXiv:2011.00430.



### Lossy Transmission Line Transients

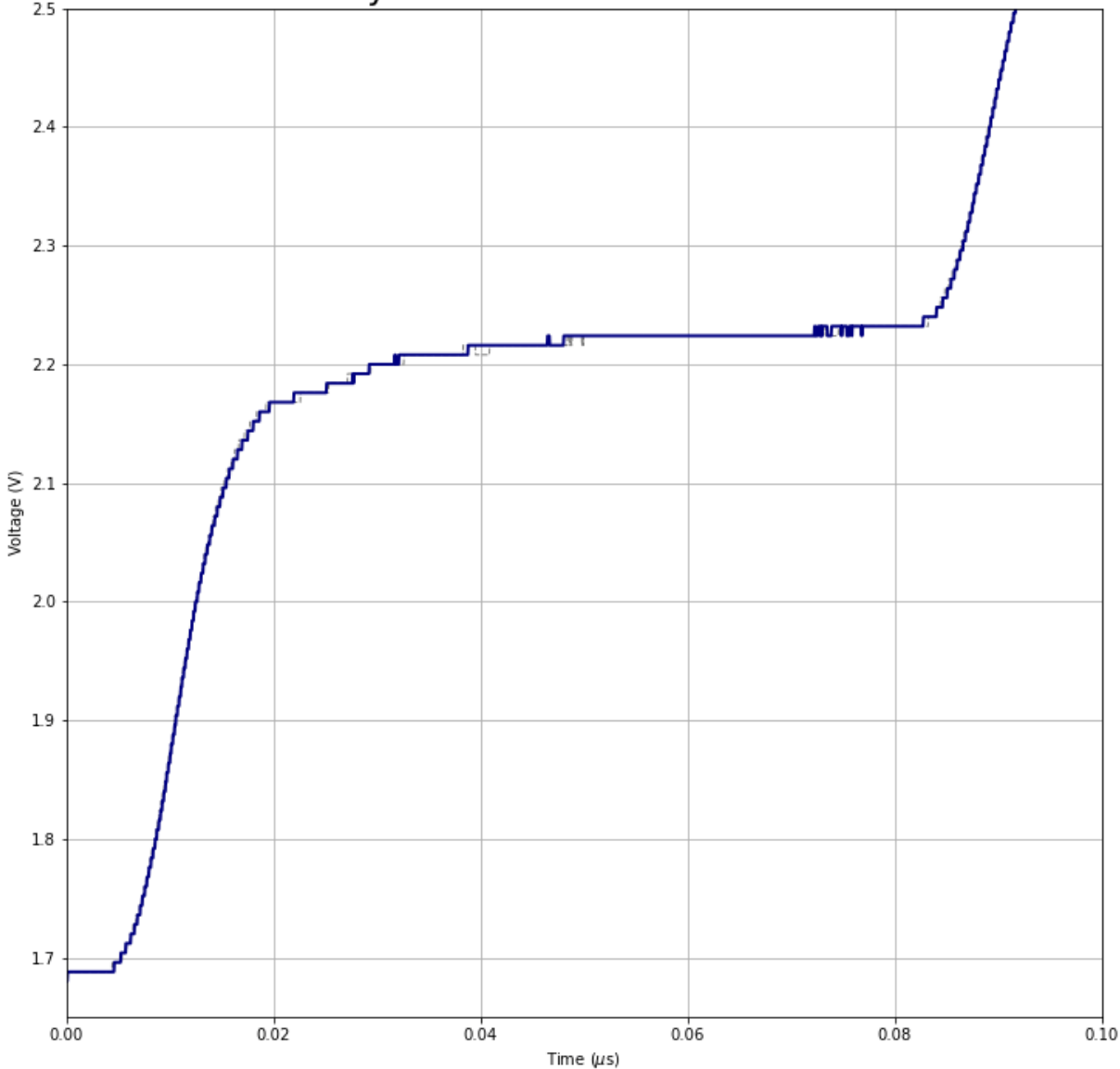

[Link](#) to gif.