

PHYS 331 – Assignment #4

Due Monday, December 4 at 08:00

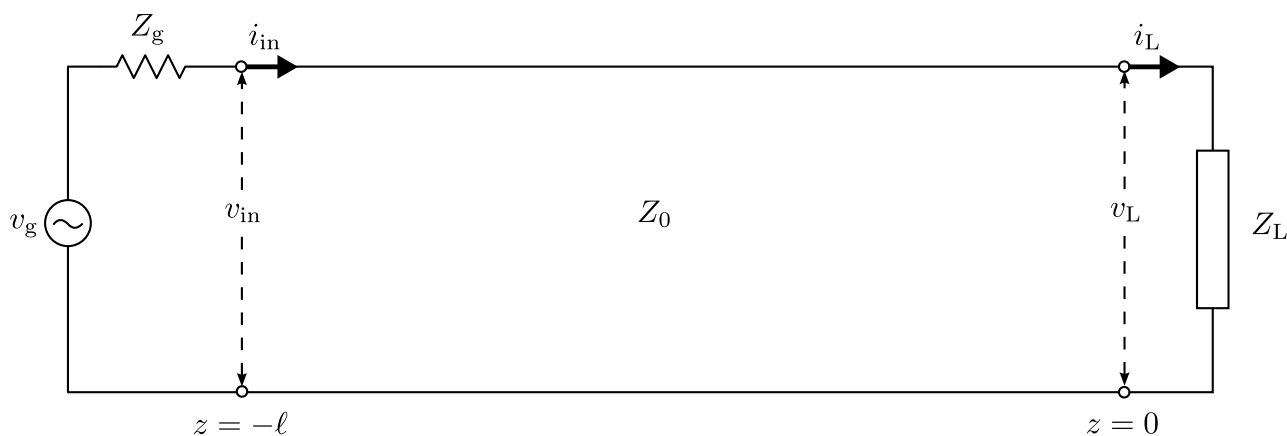


Figure 1: A signal generator with output impedance Z_g drives a transmission line of length ℓ that is terminated with load impedance Z_L .

Figure 1 shows the geometry of the transmission line system that we will use for all parts of this assignment. Assume $\ell = 8$ m, $Z_0 = 50 \Omega$, and that the signal propagation speed is $s = 0.7c$, where c is the vacuum speed of the light. In our discussion of transmission lines we showed that, in the frequency domain:

$$\hat{v}(z, \omega) = V_+ [e^{-j\omega z/s} + \Gamma e^{j\omega z/s}], \quad (1)$$

$$\hat{i}(z, \omega) = \frac{V_+}{Z_0} [e^{-j\omega z/s} - \Gamma e^{j\omega z/s}]. \quad (2)$$

1. For all parts of this first problem, we will assume that the output impedance of the signal generator is matched to the characteristic impedance of the transmission line such that $Z_g = Z_0$. Also assume that the output of the signal generator v_g is a square pulse with a height of 1 V and width 25 ns. In class, we showed that, in this case:

$$V_+ = \frac{\hat{v}_g}{2} e^{-j\omega \ell/s}. \quad (3)$$

We also showed that, in the time domain, the voltage at the input of the transmission line ($z = -\ell$) is given by:

$$v_{\text{in}} = \frac{v_{\text{g}}(t)}{2} + \frac{\Gamma}{2}v_{\text{g}}(t - 2\ell/s). \quad (4)$$

(a) Calculate the current at $i_{\text{in}}(t)$ at the input of the transmission line. For this calculation, assume that Γ is independent of ω .

Plot i_{in} as a function of time for the cases $Z_{\text{L}} = 0, 50\Omega$, and ∞ . You can sketch the current as a function of time by hand or you can plot it in Python using the linked code as a guide. If you sketch your plot by hand, you must include accurate and labeled scales for both the x - and y -axes.

(b) Calculate the voltage at $v_{\text{L}}(t)$ at the load impedance. For this calculation, assume that Γ is independent of ω .

Plot v_{L} as a function of time for the cases $Z_{\text{L}} = 0, 50\Omega$, and ∞ . You can sketch the voltage as a function of time by hand or you can plot it in Python using the linked code as a guide. If you sketch your plot by hand, you must include accurate and labeled scales for both the x - and y -axes.

(c) Calculate the current at $i_{\text{L}}(t)$ at the load impedance. For this calculation, assume that Γ is independent of ω .

Plot i_{L} as a function of time for the cases $Z_{\text{L}} = 0, 50\Omega$, and ∞ . You can sketch the current as a function of time by hand or you can plot it in Python using the linked code as a guide. If you sketch your plot by hand, you must include accurate and labeled scales for both the x - and y -axes.

For this problem, show the details of the calculations of i_{in} , v_{L} , and i_{L} . Writing down only the correct answer will not result in full marks.